

# 10. Eigen Vector (Eigen Excitation) and Eigen Value

---

## 10.1 Eigen vector

The input impedance measured at every port , eg., becomes identical in eigen excitation. This impedance is an eigen value of the impedance matrix of the circuit.

## 10.2 Eigen values and eigen vectors in circuit matrices

When eigen values are obtained for one of circuit matrices, those of remaining matrices are determined. Also, eigen vectors are identical for all matrices in a given circuit.

## 10.3 Method for determination of eigen value and eigen vector

The eigen values and eigen vectors of rotationally symmetric circuit is calculated as an example.

# Eigen Vector and Eigen Value : Definition

Consider the case that the following relation holds. That is, the input impedance measured at every port is identical.


$$\frac{V_1^i}{I_1^i} = \frac{V_2^i}{I_2^i} = \dots = \frac{V_n^i}{I_n^i} = z_i$$

$$[V^i] = [Z][I^i] = z_i[I^i]$$

$$([Z] - z_i[1])[I] = 0$$

$$\det([Z] - z_i[1]) = 0$$

n solutions for  $z_i$   eigen value

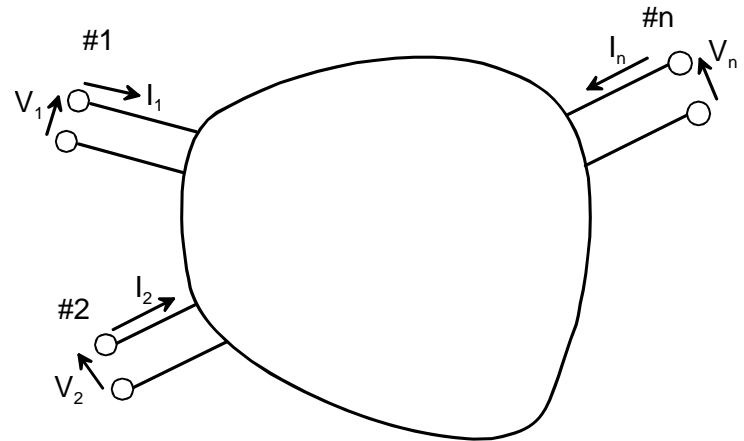

# Eigen Vector and Eigen Value : Example

Symmetric 2 port circuit

$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{12} & Z_{11} \end{bmatrix}$$

$$\det([Z] - z[1]) = 0$$

$$(Z_{11} - z)^2 - Z_{12}^2 = 0$$

$$\therefore z_i = Z_{11} \pm Z_{12}$$

$$(a) \quad z_1 = Z_{11} + Z_{12}$$

$$\begin{bmatrix} -Z_{12} & Z_{12} \\ Z_{12} & -Z_{12} \end{bmatrix} \begin{bmatrix} I_1^1 \\ I_2^1 \end{bmatrix} = 0$$

$$\therefore I_1^1 = I_2^1 \quad (\text{even excitation})$$

$$(b) \quad z_2 = Z_{11} - Z_{12}$$

$$\begin{bmatrix} Z_{12} & Z_{12} \\ Z_{12} & Z_{12} \end{bmatrix} \begin{bmatrix} I_1^2 \\ I_2^2 \end{bmatrix} = 0$$

$$\therefore I_1^2 = -I_2^2 \quad (\text{odd excitation})$$

# Relation between different circuit matrices

Rational function of a square matrix  $[M]$

$$f([M]) = c_0([M] - c_1[1])([M] - c_2[1]) \cdots ([M] - c_{-1}[1])^{-1}([M] - c_{-2}[1])^{-1} \cdots$$

$$[M]\mathbf{E}^i = \lambda_i \mathbf{E}^i$$

$$c_k[1]\mathbf{E}^i = c_k \mathbf{E}^i$$

$$([M] - c_k[1])\mathbf{E}^i = (\lambda_i - c_k)\mathbf{E}^i$$

$$\mathbf{E}^i = (\lambda_i - c_k)([M] - c_k[1])^{-1}\mathbf{E}^i \Rightarrow ([M] - c_k[1])^{-1}\mathbf{E}^i = (\lambda_i - c_k)^{-1}\mathbf{E}^i$$

$$\begin{aligned} f([M])\mathbf{E}^i &= c_0([M] - c_1[1])([M] - c_2[1]) \cdots ([M] - c_{-1}[1])^{-1}([M] - c_{-2}[1])^{-1} \cdots \mathbf{E}^i \\ &= c_0([M] - c_1[1])([M] - c_2[1]) \cdots ([M] - c_{-1}[1])^{-1}(\lambda_i - c_{-2})^{-1} \cdots \mathbf{E}^i \\ &= c_0(\lambda_i - c_1)(\lambda_i - c_2) \cdots (\lambda_i - c_{-1})^{-1}(\lambda_i - c_{-2})^{-1} \cdots \mathbf{E}^i \end{aligned}$$

eigen vector of rational matrix function  $f([M])$  = eigen vector of matrix  $[M]$ .

eigen value of rational matrix function  $f([M])$

$$c_0(\lambda_i - c_1)(\lambda_i - c_2) \cdots (\lambda_i - c_{-1})^{-1}(\lambda_i - c_{-2})^{-1} \cdots$$

# Relation between different matrices

$$[Z][I^i] = z_i[I^i]$$

$$[Y][V^i] = y_i[V^i]$$

Here, the following relation holds.

$$[Y] = f([Z]) = [Z]^{-1} = ([Z] - c_{-1}[1])^{-1} \quad c_{-1} = 0$$

eigen vectors of impedance matrix = eigen vectors of admittance matrix

eigen values of impedance matrix and admittance matrix :

$$y_i = (z_i - c_{-1})^{-1} = z_i^{-1}$$

Scattering matrix and impedance matrix

$$[S] = \left(\frac{1}{R_0}[Z] + 1\right)^{-1} \left(\frac{1}{R_0}[Z] - 1\right) = ([Z] + R_0)^{-1} ([Z] - R_0)$$

$$S_i = (z_i + R_0)^{-1} (z_i - R_0) = \frac{z_i - R_0}{z_i + R_0}$$

# How to find eigen vector and eigen value ?

$$[P]\mathbf{u}^i = p_i\mathbf{u}^i$$

$$[Q][P]\mathbf{u}^i = p_i[Q]\mathbf{u}^i$$

Commutative matrices  $[P]$  and  $[Q]$ :  $[P][Q] = [Q][P]$

$$[Q][P]\mathbf{u}^i = [P][Q]\mathbf{u}^i = [P]([Q]\mathbf{u}^i) = p_i([Q]\mathbf{u}^i)$$

$[Q]\mathbf{u}^i$  is the eigen vector of  $[P]$ , and has the eigen value  $p_i$ .

Therefore,  $[Q]\mathbf{u}^i$  is to be proportional to  $\mathbf{u}^i$

$$\therefore [Q]\mathbf{u}^i = q_i\mathbf{u}^i$$

$\mathbf{u}^i$  is also an eigen vector of matrix  $[Q]$ .


# How to find eigen vector and eigen value ?

rotationally symmetric 3 port circuit

$$[R][Z]\mathbf{i} = [R]\mathbf{v} = \mathbf{v}' = [Z]\mathbf{i}' = [Z][R]\mathbf{i}$$

$$[R] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

$$[R][Z] = [Z][R]$$

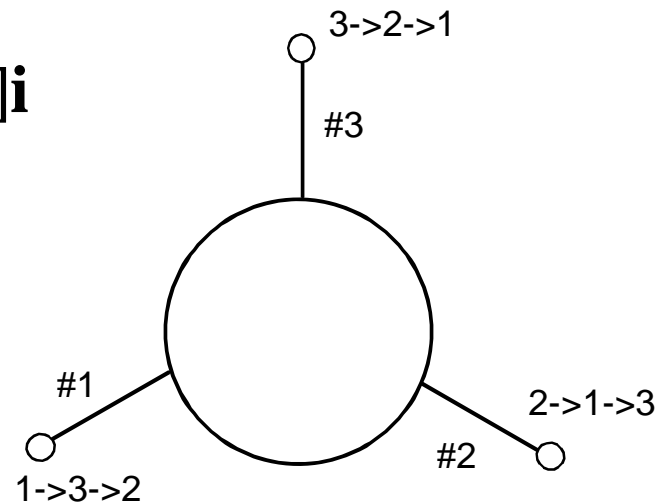

The eigen vector of  $[Z]$  becomes identical to that of  $[R]$ .

$$[R]\mathbf{u}^i = r^i \mathbf{u}^i$$

$$\det([R] - r[1]) = 0$$

$$\det \begin{pmatrix} -r & 0 & 1 \\ 1 & -r & 0 \\ 0 & 1 & -r \end{pmatrix} = 0$$

$$r^3 - 1 = 0$$

$$\therefore r = 1, e^{j\frac{2\pi}{3}}, e^{-j\frac{2\pi}{3}}$$

# How to find eigen vector and eigen value ?

$$(i) r = 1 \quad \begin{pmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix} \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} = \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} \quad \Rightarrow \quad \mathbf{u}^1 = \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix}$$

$$(ii) r = e^{j\frac{2\pi}{3}} \quad \begin{pmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix} \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} = e^{j\frac{2\pi}{3}} \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} \quad \Rightarrow \quad \mathbf{u}^2 = \begin{pmatrix} 1 \\ e^{-j\frac{2\pi}{3}} \\ e^{j\frac{2\pi}{3}} \end{pmatrix}$$

$$(iii) r = e^{-j\frac{2\pi}{3}} \quad \begin{pmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix} \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} = e^{-j\frac{2\pi}{3}} \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} \quad \Rightarrow \quad \mathbf{u}^3 = \begin{pmatrix} 1 \\ e^{j\frac{2\pi}{3}} \\ e^{-j\frac{2\pi}{3}} \end{pmatrix}$$