



Multiplication and Shift Circuits

Shmuel Wimer


Bar Ilan University, Engineering Faculty

Technion, EE Faculty



Shift/Add Unsigned Multiplication Algorithms

 a Multiplicand $a_{k-1}a_{k-2} \cdots a_1a_0$
 x Multiplier $x_{k-1}x_{k-2} \cdots x_1x_0$
 p Product ($a \times x$) $p_{2k-1}p_{2k-2} \cdots p_1p_0$



Shift partial products



In right shift multiplication the partial products $x_j a$, $0 \leq j \leq k-1$, are recursively accumulated from top to bottom.

$$p^{(j+1)} = \underbrace{\left(p^{(j)} + x_j a 2^k \right)}_{\text{add}} \times 2^{-1} \quad \text{with } p^{(0)} = 0 \text{ and } p^{(k)} = p$$

shift right
↓

$x_0 a 2^k$ will be multiplied by 2^{-k} after k iterations. a is pre multiplied by 2^k to offset the effect of right shifts.

After k iteration the recurrence yields $p^{(k)} = ax + p^{(0)} 2^{-k} = ax$

a is aligned to the left (MSB) k bits of a $2k$ -bit .

How to obtain $p = ax + y$? Initialize $p^{(0)}$ to $y 2^k$



(a) Right-shift algorithm

```
=====
a      1 0 1 0
x      1 0 1 1
=====
```

```
p(0)    0 0 0 0
+x0a   1 0 1 0
=====
```

initialize
add partial product aligned to left

```
p(1)    0 1 0 1 0
+x1a   1 0 1 0
=====
```

multiply by 2^{-1} by **right-shift**
add partial product aligned to left

```
p(2)    0 1 1 1 1 0
+x2a   0 1 1 1 1 0
=====
```

multiply by 2^{-1} by **right-shift**
add partial product aligned to left

```
p(3)    0 0 1 1 1 1 0
+x3a   0 0 1 1 1 1 0
=====
```

```
p(4)    0 1 1 0 1 1 1 0
=====
```



In left shift multiplication the partial products $x_{k-1-j}a$, $0 \leq j \leq k-1$, are recursively accumulated from bottom to top.

$$p^{(j+1)} = \underbrace{2p^{(j)} + x_{k-1-j}a}_{\text{add}} \quad \text{with } p^{(0)} = 0 \text{ and } p^{(k)} = p$$

shift left
↓

After k iteration the recurrence yields $p^{(k)} = ax + p^{(0)}2^k = ax$

How to obtain $p = ax + y$? Initialize $p^{(0)}$ to $y2^{-k}$



(b) Left-shift algorithm

a				1	0	1	0
x				1	0	1	1
$p^{(0)}$				0	0	0	0
	0			0	0	0	0
$+x_3a$				1	0	1	0
$p^{(1)}$		0		1	0	1	0
	0	1		0	1	0	0
$+x_2a$				0	0	0	0
$p^{(2)}$		0	1		0	1	0
	0	1	0		1	0	0
$+x_1a$				1	0	1	0
$p^{(3)}$		0	1	1		0	0
	0	1	1	0		0	1
$+x_0a$				1	0	1	0
$p^{(4)}$	0	1	1	0	1	1	1

initialize

multiply by 2 by **left-shift**

add partial product aligned to right

multiply by 2 by **left-shift**

add partial product aligned to right

multiply by 2 by **left-shift**

add partial product aligned to right



Serial multiplication by add and shift entails k additions and k shifts


Right shift is favored since the addition of partial product takes place at the MSB k -bit part of the $2k$ word. In left shift it takes place at the LSB k -bit part and carry can propagate to MSB part.

Left shift algorithm requires therefore $2k$ bit adder, while for right shift k bit suffice.



Hardware of right-shift multipliers (without control)
 
$$p^{(j+1)} = \left(p^{(j)} + x_j a 2^k \right) \times 2^{-1}$$



Shift registers

Next bit of multiplier


Control requires counter

Adder's carry out must be stored

Addition of a partial product requires two clock cycles. One for add and one for a shift.



 
Reducing addition of partial product to one cycle



At each clock cycle adder's carry-out is written to MSB and LSB is used for multiplication (via a MUX)



 Hardware of left-shift multipliers (without control)





Multiplication of Signed Numbers

- **Sign-magnitude** representation requires only XOR-ing of the operands' sign bits.
- In **1's-complement**, a negative operand is complemented and unsigned multiplication takes place. The result is complemented by XOR-ing of operands' sign bits.
- For **2's-complement**, right-shift multiplication is proper for negative multiplicand and positive multiplier.



Right-shift multiplication

a	1	0	1	1	0					
x	0	1	0	1	1					
$p^{(0)}$	0	0	0	0	0					
$+x_0a$	1	0	1	1	0					
$p^{(1)}$	1	1	0	1	1	0				
$+x_1a$	1	0	1	1	0					
$p^{(2)}$	1	1	0	0	0	1	0			
$+x_2a$	0	0	0	0	0					
$p^{(3)}$	1	1	1	0	0	0	1	0		
$+x_3a$	1	0	1	1	0					
$p^{(4)}$	1	1	0	0	1	0	0	1	0	
$+x_4a$	0	0	0	0	0					
$p^{(5)}$	1	1	1	0	0	1	0	0	1	0

Negative multiplicand

Positive multiplier

Negative sign extensions



Negative multiplicand and multiplier

a	1	0	1	1	0				
x	1	0	1	0	1				
$p^{(0)}$	0	0	0	0	0				
$+x_0a$	1	0	1	1	0				
$p^{(1)}$	1	1	0	1	1	0			
$+x_1a$		0	0	0	0	0	0		
$p^{(2)}$	1	1	1	0	1	1	0		
$+x_2a$		1	1	1	0	1	1	0	
$p^{(3)}$	1	1	0	0	1	1	1	0	
$+x_3a$		0	0	0	0	0			
$p^{(4)}$	1	1	1	0	0	1	1	1	0
$+(-x_4a)$		0	1	0	1	0			
$p^{(5)}$		0	0	0	1	1	0	1	1
		0	0	0	1	1	0	1	1

Negative multiplicand

Negative multiplier


Negative sign extensions

Handle correctly by subtracting $x_{k-1}a$ rather than adding

Hardware complements multiplicand and adds 1 via carry-in



 Hardware implementation (control logic not shown)



Bypassed MUX for positive multiplier

Subtracting $x_{k-1}a$
by negation plus 1

Left-shift requires more logic due to sign extension, and is also slower ($2k$ bit adder).



Parallel Multiplication Algorithms

```
  011001 : 2510
× 100111 : 3910
-----
  011001
 011001
 000000
 000000
+011001
-----
001111001111 : 97510
```

multiplicand
multiplier

partial
products

product

$$P = YX = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right)$$
$$= \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$

	y ₅	y ₄	y ₃	y ₂	y ₁	y ₀						
	x ₅	x ₄	x ₃	x ₂	x ₁	x ₀						
							x ₀ y ₅	x ₀ y ₄	x ₀ y ₃	x ₀ y ₂	x ₀ y ₁	x ₀ y ₀
							x ₁ y ₅	x ₁ y ₄	x ₁ y ₃	x ₁ y ₂	x ₁ y ₁	x ₁ y ₀
							x ₂ y ₅	x ₂ y ₄	x ₂ y ₃	x ₂ y ₂	x ₂ y ₁	x ₂ y ₀
							x ₃ y ₅	x ₃ y ₄	x ₃ y ₃	x ₃ y ₂	x ₃ y ₁	x ₃ y ₀
							x ₄ y ₅	x ₄ y ₄	x ₄ y ₃	x ₄ y ₂	x ₄ y ₁	x ₄ y ₀
							x ₅ y ₅	x ₅ y ₄	x ₅ y ₃	x ₅ y ₂	x ₅ y ₁	x ₅ y ₀
p ₁₁	p ₁₀	p ₉	p ₈	p ₇	p ₆	p ₅	p ₄	p ₃	p ₂	p ₁	p ₀	

Multiplicand


Multiplier

Partial
Products

Product




 Dot diagram is convenient to illustrate large array multiplication.





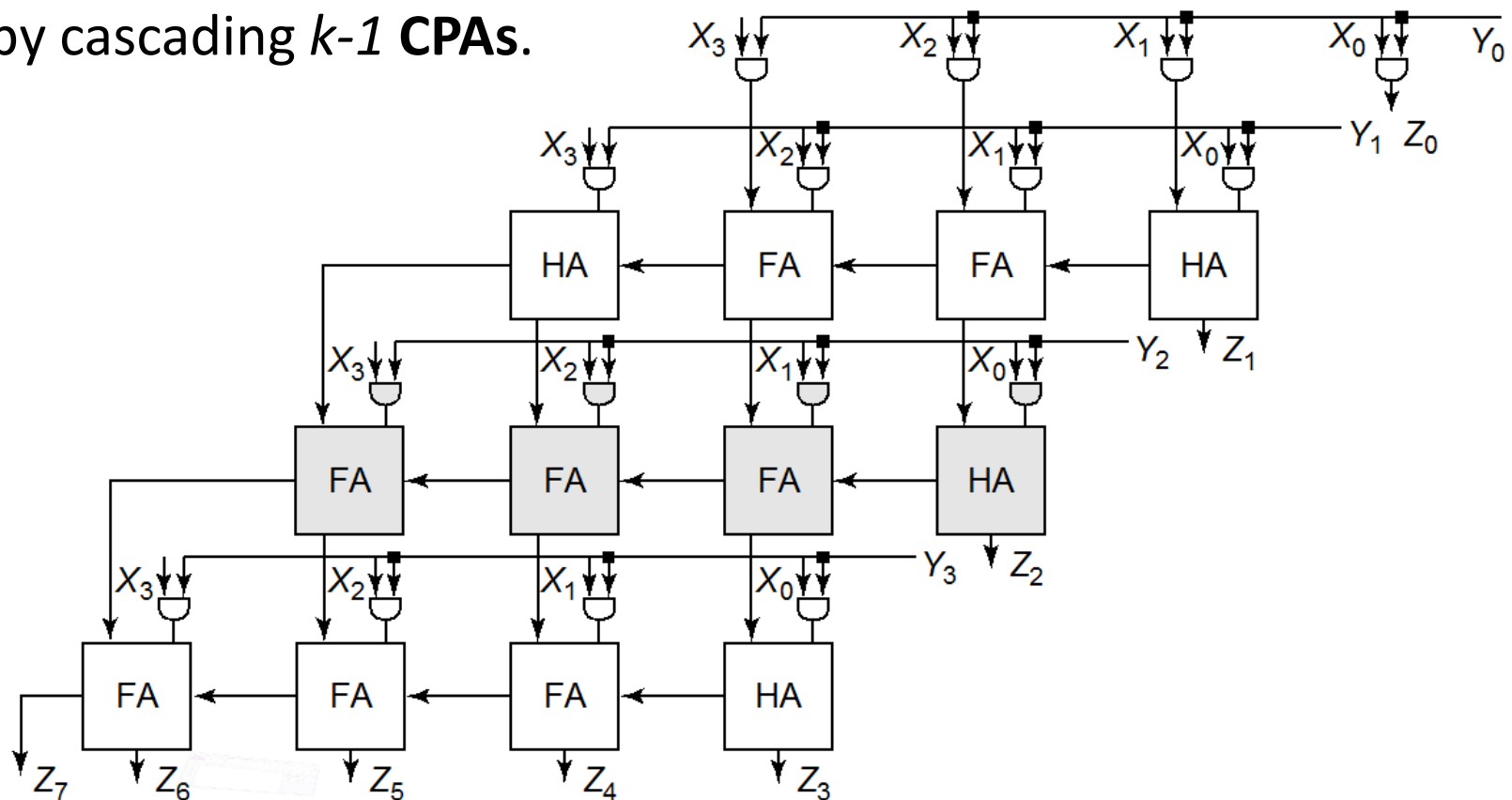The most obvious of adding k N -bit numbers is by cascading $k-1$ **CPAs**.





The most obvious of adding k N -bit numbers is by cascading $k-1$ **CPAs**.


This is slow and area consuming, taking $O(kN)$ time and area (not really).

Observation:

A Full-adder has three inputs x , y and z .

It is producing an output s of weight 1 and an output c of weight 2.


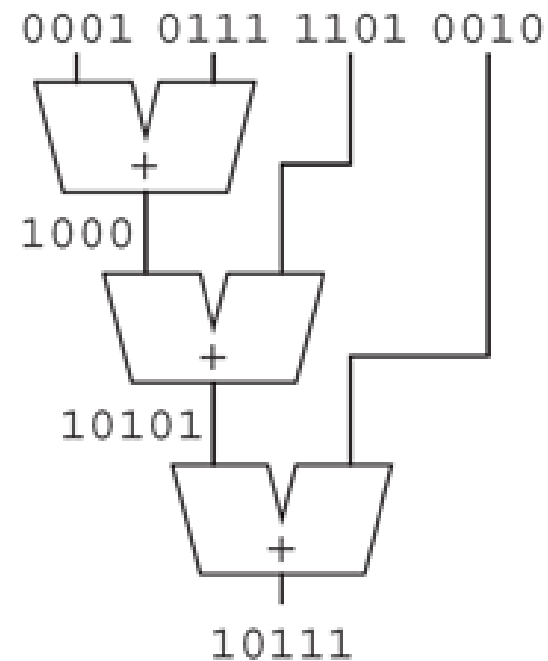
The inputs are symmetric with respect to s and c .






Carry-Save Adder

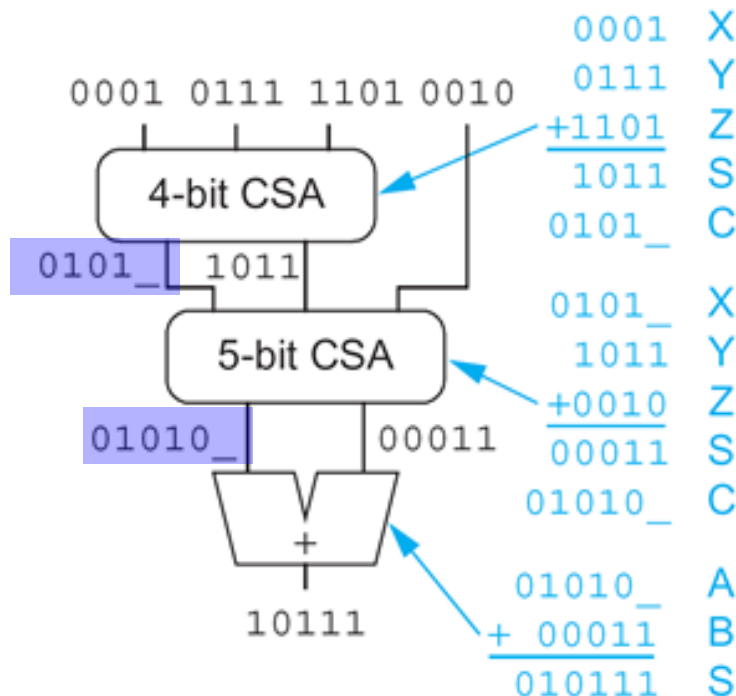 The sum $X+Y+Z$ can therefore be obtained by first summing $x_i+y_i+z_i$ in parallel, producing **C** and **S**.



 Then summing **S** and left shifted **C** by CPA. This is called **Carry-Save Adder** (CSA).




Summation of k numbers requires stacking $k-2$ **CSAs** and a single **CPA**.

The resulting delay is $O(k+n)$ rather than $O(kn)$ if **CPAs** were used (not exactly...).

CSA was invented by von Neumann early digital computer (1946).



Unsigned Array Multiplication

 

Critical path has N CASs and M -bit CPAs, yielding $O(N+M)$ delay.
The N LSBs are obtained directly from the sum outputs of CSAs.
The M MSBs are obtained by CPA.
It can be squashed in layout to occupy a rectangle.



2's Complement Array Multiplication

Same CSA array multiplication can be used.

$$\begin{aligned} P = yx &= \left(-y_{M-1} 2^{M-1} + \sum_{j=0}^{M-2} y_j 2^j \right) \left(-x_{N-1} 2^{N-1} + \sum_{i=0}^{N-2} x_i 2^i \right) \begin{array}{l} \text{2's} \\ \text{complement} \end{array} \\ &= \sum_{i=0}^{N-2} \sum_{j=0}^{M-2} x_i y_j 2^{i+j} + x_{N-1} y_{M-1} 2^{M+N-2} \quad \text{positive} \\ &\quad - \left(\sum_{i=0}^{N-2} x_i y_{M-1} 2^{i+M-1} + \sum_{j=0}^{M-2} x_{N-1} y_j 2^{j+N-1} \right) \text{negative} \end{aligned}$$

To handle the negative part, 2's complement will be used.

Recall that 2's complement equals 1's complement plus 1.

1's complement is obtained by bit complement.




$$\begin{aligned} & x_{N-1}y_{M-1}2^{M+N-2} \\ & - \sum_{i=0}^{N-2} x_i y_{M-1} 2^{i+M-1} \\ & - \sum_{j=0}^{M-2} x_{N-1} y_j 2^{j+N-1} \end{aligned}$$

23



Physical layout

 Notice how all 1s were summed and propagated leftward.



	y_5	y_4	y_3	y_2	y_1	y_0
	x_5	x_4	x_3	x_2	x_1	x_0
<u>1</u>	<u>x_5y_0</u>	x_0y_4	x_0y_3	x_0y_2	x_0y_1	x_0y_0
x_5y_1	x_1y_4	x_1y_3	x_1y_2	x_1y_1	x_1y_0	
<u>x_5y_2</u>	x_2y_4	x_2y_3	x_2y_2	x_2y_1	x_2y_0	
<u>x_5y_3</u>	x_3y_4	x_3y_3	x_3y_2	x_3y_1	x_3y_0	
<u>x_5y_4</u>	x_4y_4	x_4y_3	x_4y_2	x_4y_1	x_4y_0	
<u>1</u>	x_5y_5	<u>x_4y_5</u>	<u>x_3y_5</u>	<u>x_2y_5</u>	<u>x_1y_5</u>	<u>x_0y_5</u>
P_{11}	P_{10}	P_9	P_8	P_7	P_6	P_5
P_4	P_3	P_2	P_1	P_0		



Acceleration of Serial Multiplication

$$\text{Observation: } 2^j + 2^{j-1} + \dots + 2^{i+1} + 2^i = 2^{j+1} - 2^i$$

Consequently, additions occurring by a string of 1s in the multiplier can be replaced by an addition and a subtraction.

Bits x_{i-1} and x_i of the multiplier are encoded in y_i as follows:

$(x_i, x_{i-1}) = (00) \Rightarrow y_i = 0$; No string of 1s in sight

$(x_i, x_{i-1}) = (01) \Rightarrow y_i = 1$; End of string of 1s

$(x_i, x_{i-1}) = (10) \Rightarrow y_i = -1$; Beginning of string of 1s

$(x_i, x_{i-1}) = (11) \Rightarrow y_i = 0$; Continuation of string of 1s

Example: radix-2 encoding of a 16-bit word artifact

1	0	0	1	1	1	0	1	1	0	1	0	1	0	1	1	0	0	x
-1	0	1	0	0	-1	1	0	-1	1	-1	1	0	0	-1	0			y



$$\begin{array}{cccccccccccccccccc} & 1 & 0 & 0 & 1 & 1 & 1 & 0 & 1 & 1 & 0 & 1 & 0 & 1 & 1 & 1 & 0 & 0 & x \\ (1) & -1 & 0 & 1 & 0 & 0 & -1 & 1 & 0 & -1 & 1 & -1 & 1 & 0 & 0 & -1 & 0 & y \end{array}$$

Above is a proper interpretation for signed multiplication. A MSB string 111...111 of 1s will be encoded into a string of 000...00-1, resulting in appropriate subtraction.

Problem: Assume that the unsigned value of X is intended.

Booth encoding results in -2^{15} rather than $+2^{15}$.

Solution: Add 2^{16} by extending y with 1 MSB.



=====											
a	1	0	1	1	0						
x	1	0	1	0	1	Multiplier					
y	-1	1	-1	1	-1	Booth-recoded					
=====											
$p^{(0)}$	0	0	0	0	0						
$+y_0a$	0	1	0	1	0						
=====											
$2p^{(1)}$	0	0	1	0	1	0					
$p^{(1)}$	0	0	1	0	1	0					
$+y_1a$	1	0	1	1	0						
=====											
$2p^{(2)}$	1	1	1	0	1	1	0				
$p^{(2)}$	1	1	1	0	1	1	0				
$+y_2a$	0	1	0	1	0						
=====											
$2p^{(3)}$	0	0	0	1	1	1	1	0			
$p^{(3)}$	0	0	0	1	1	1	1	0			
$+y_3a$	1	0	1	1	0						
=====											
$2p^{(4)}$	1	1	1	0	0	1	1	1	0		
$p^{(4)}$	1	1	1	0	0	1	1	1	0		
$+y_4a$	0	1	0	1	0						
=====											
$2p^{(5)}$	0	0	0	1	1	0	1	1	1	0	
$p^{(5)}$	0	0	0	1	1	0	1	1	1	0	
=====											

2's Comp. addition (negative)

2's Comp. addition (positive)



Booth Encoding

Proposed by Booth in 1951 to accelerate serial multiplication (series of shift and add).

$P = Y \times X = Y \times 00111110$ requires 5 shifts and additions.

$$\begin{aligned} Y \times 00111110 &= Y \times (2^5 + 2^4 + 2^3 + 2^2 + 2^1) \\ &= Y \times (2^6 - 2^1) = Y \times (01000000 - 00000010) \end{aligned}$$

requires 1 add, 1 subtract (add 2's complement) and 2 shifts.

$$\begin{aligned} Y \times 00111010 &= Y \times (2^5 + 2^4 + 2^3 + 2^1) = Y \times [(2^6 - 2^3) + 2^1] \\ &= Y \times (01000000 - 00001000 + 00000010) \end{aligned}$$

Multiplication can be considerably accelerated by turning sequences of 1s into leading and trailing 1s.



$$P = \overbrace{011001}^Y \times \overbrace{100111}^X = \overbrace{011001}^Y \times \underbrace{\underbrace{10}_2 \underbrace{01}_1 \underbrace{11}_3}_X$$

Instead of multiplying Y and adding bit-by-bit of X we look at groups of 2 bits, hence working in **radix-4**.

In radix-4 each partial product has 4 times the weight of its predecessor one.

Radix-4 multiplication will **reduce to half** the number of partial products, with 2-bit left shift at each one. The partial products are $\{0, Y, 2Y, 3Y\}$.

$3Y$ is a problem since it cannot be obtained by a shift but rather requires addition $3Y = 2Y + Y$.

Radix-4 algorithm implements $3Y = 4Y - Y$ and $2Y = 4Y - 2Y$.



Weight of LSB in current pair is twice the MSB in previous.

Weight of MSB in current pair is 4 times the MSB in previous.


$$P = \overbrace{011001}^Y \times \underbrace{100111}_X$$

$X=3$. $PP=-Y$. $4Y$ will be discovered in next step.

$X=1$. $PP=2Y$. $4Y$ is carried from previous, which is 1 in current.

$X=2$. $PP=-2Y$. $4Y$ will be discovered in next step.

 $X=0$. $PP=Y$. No need for sign. Always Y or 0.





PP table defines the appropriate encoding of multiplicand: 0, Y , $-Y$, $2Y$ or $-2Y$.

Partial Product (PP) Selection Table

Multiplier	Selection	Explanations
------------	-----------	--------------




Radix-4 modified Booth encoding values

Inputs			Partial Products	Booth Selects		
X_{2i+1}	X_{2i}	X_{2i-1}	$PP\ i$	SINGLE i	DOUBLE i	NEG i
0	0	0	0	0	0	0
0	0	1	Y	1	0	0
0	1	0	Y	1	0	0
0	1	1	$2Y$	0	1	0
1	0	0	$-2Y$	0	1	1
1	0	1	$-Y$	1	0	1
1	1	0	$-Y$	1	0	1
1	1	1	$-0(=0)$	0	0	1



Radix-4 Booth encoder and selector

 


Encodes 0, Y , or $2Y$ according to 3 successive bits of multiplier.

Multiplicand Y is 0-extended to $M+1$ bits. If the NEG is asserted Y is negated and extra 1 is added in the next row.



 Radix-4 Booth-encoded partial products with sign extension for unsigned multiplication




Though unsigned, Booth Alg. generates negative PPs.

Negative PPs are handled in 2's complement by sign extension and addition of the sign bit.

To squash into rectangular floor plan the sign bit triangle should better be out.




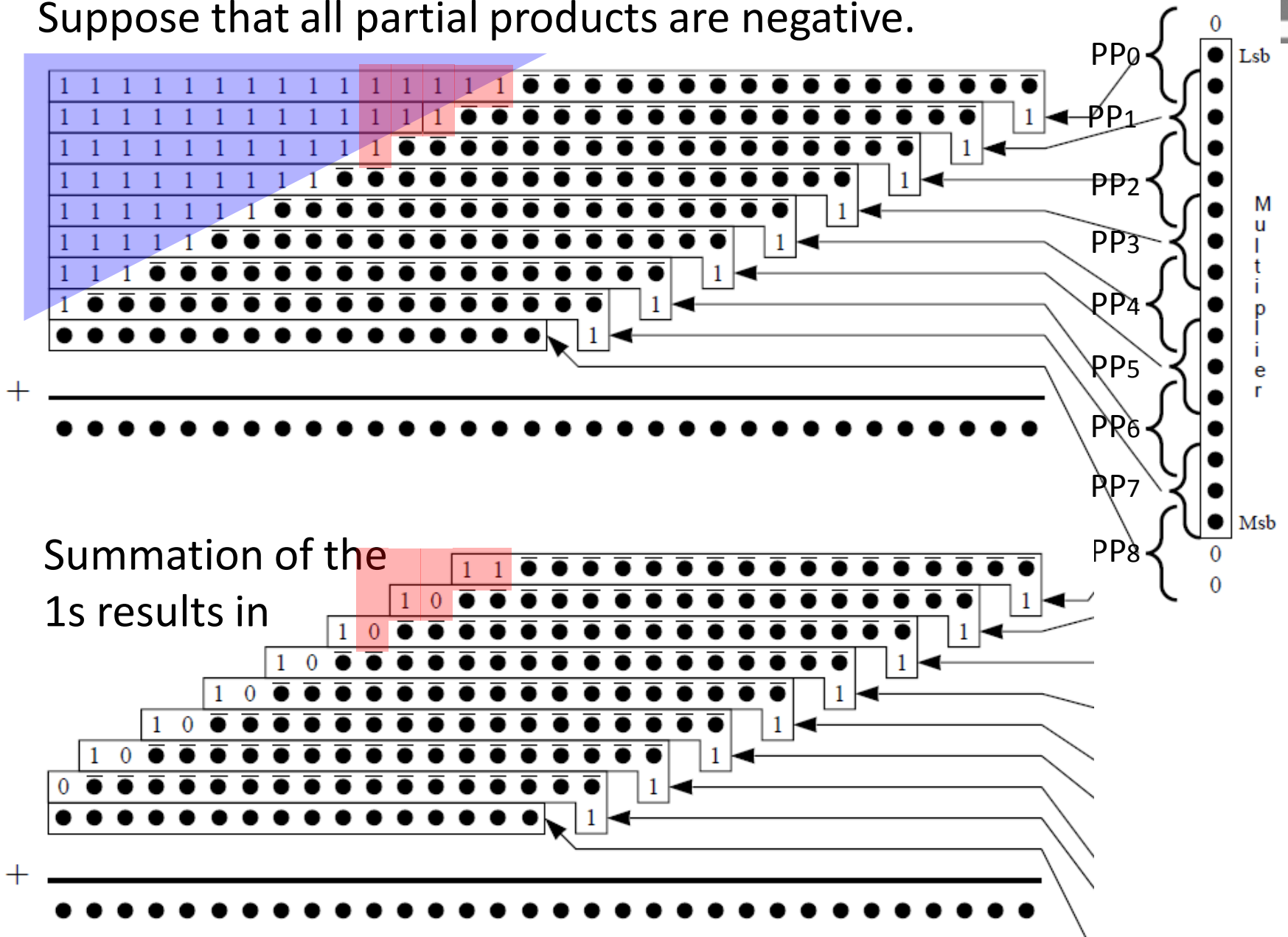Suppose that all partial products are negative.







 If a particular PP is positive, the negation can be reverted by adding 1 to the LSB of the original 1s string.



resulting in this configuration

 

 


Critical path involves: Booth encoder, select line driver, Booth selector, $N/2$ CSAs and final CPA.

Selector resides in every bit of the array, consuming significant area. Good area/power/performance tradeoff is to downsize it as much as possible. (why?)



Booth Encoding Signed Multiplier

 

Multiplier needs not 2-bit extension (x_{16}, x_{17}) since it is already sign extended (x_{15}). Then $x_{15}=x_{16}=x_{17}$ and encoding is 0.

PP₈ is therefore not required.




Wallace Tree Multiplication

Consider the following 9-bit unsigned multiplication

Every dot of the array represents a partial product.

 Partial products are vertically summed by half and full adders (CSA).



Multiplication time complexity is $O(n)$, There are $n-2$ sequential CSAs additions.

Wallace tree accelerates CSAs time complexity to $O(\log n)$ by different organization of CSAs sums.




In each column of partial products, every three adjacent rows construct a group.

Reduction in each group is done by one of the following cases:

Applying a full adder (CSA) to the 3-bit groups

Applying a half adder to the 2-bit groups

 Passing any 1-bit group to the next stage without change







Passing any 1-bit group to the next stage without change

Sum of half adder stays in column, carry sent to next column.

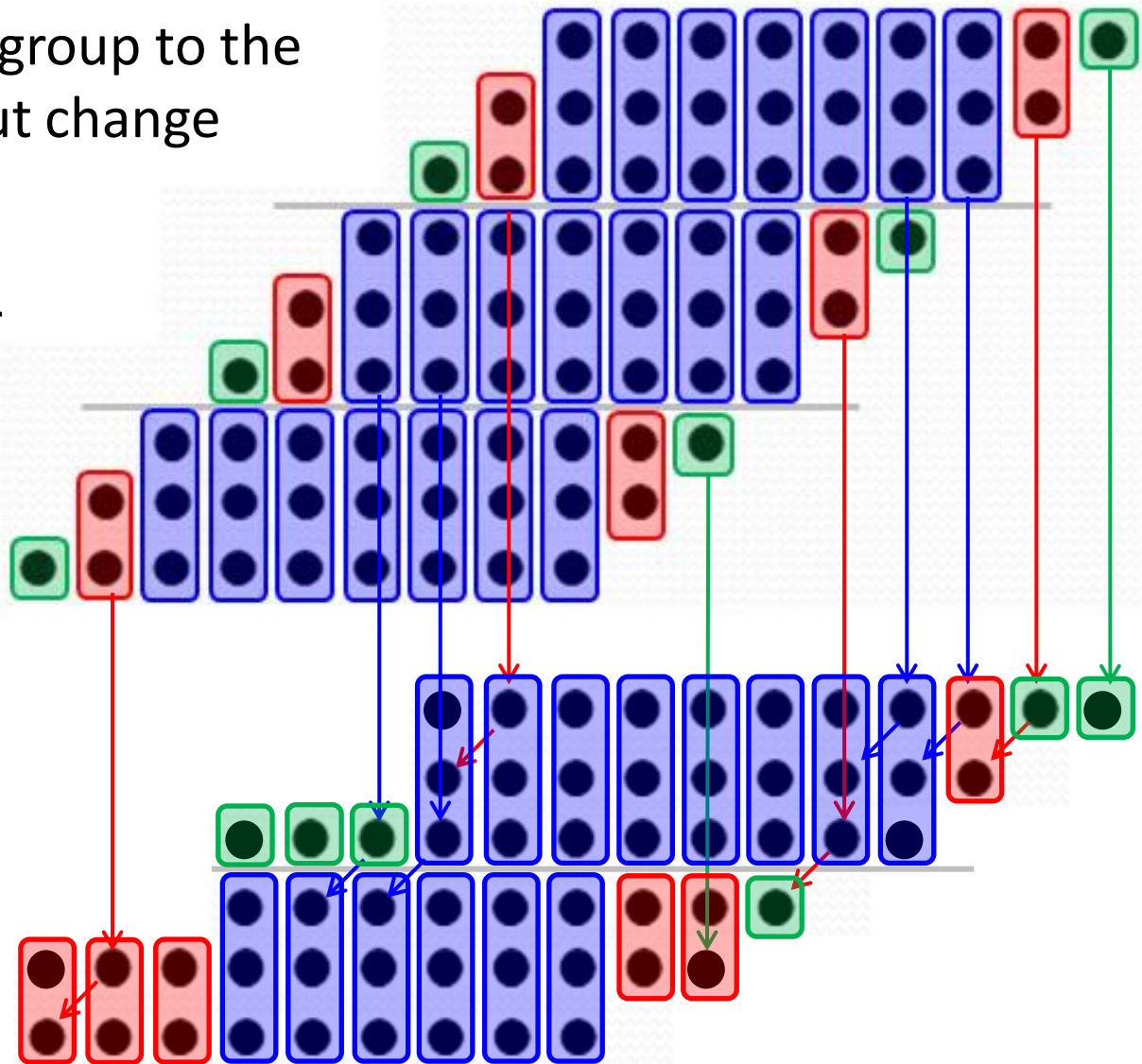Sum of full adder stays in column, carry sent to next column.



 



All the full-adder (CSA) and half-adder additions in a stage are performed simultaneously.

Every stage has its own adders.

Data is progressing through $O(\log_{3/2} n)$ stages (proven below).

The final two rows are summed by CPA.

Other groups organizations called ***Modified Wallace*** and ***Dadda*** reductions, yielding slight area improvement (number of circuits), are possible. Asymptotically all are similar.



Time and Area Complexity

At each stage of the computation each group of 3 bits is reduced to 2 bits, with at most 2 bits left over.

The depth of Wallace tree $D(n)$ satisfies

$$D(n) = \begin{cases} 0 & \text{if } n \leq 2 \\ 1 & \text{if } n = 3 \\ 1 + D(\lceil 2n/3 \rceil) & \text{if } n \geq 4 \end{cases}$$

This is a recursive equation solved to $D(n) = \Theta(\log n)$.

The final addition is implemented by CPA.

Carry-lookahead adder takes $\Theta(\log n)$, so using CLA for final addition yields $\Theta(\log n)$ overall time complexity.



The number of adders $C(n)$ is $\Theta(n^2)$.

The number of bits in a row is between n and $2n$. There are n rows so $2/3n^2$ full and half adders are required in the first stage.

The number of rows is reducing by factor $2/3$ from stage to stage, hence the total sums to $\Theta(n^2)$ as well.



Shifters

Logical shifter: Shifts the number to left or right and fills the empty spots with 0s. Specified by << or >> in Verilog.

1011 LSR 1 = 0101; 1011 LSL 1 = 0110

Arithmetic shifter: Similar to logical, but on right shift fills empty spots with sign bit. Specified by <<< or >>> in Verilog.

1011 ASR 1 = 1101; 1011 ASL 1 = 0110

Barrel shifter (rotator): Rotates numbers cyclically.

1011 ROR 1 = 1101; 1011 ROL 1 = 0111



Conceptually, rotation of N -bit word involves array of N N -input MUXes to select each of the outputs from each of the possible input positions. This is called ***array shifter***.

Array shifter requires a decoder to produce 1-of- N shift.

MUXes of more than 8 inputs have excessive parasitic capacitance, so it is faster to construct shifters from $\log_v N$ v -input MUXes. This is called ***logarithmic shifter***.

Left rotate by k bits is equivalent to right rotate by $N-k$ bits.

Computing $N-k$ requires subtracter in the critical path.



We take advantage of 2's complement and the fact that rotation is cyclic modulo N $N - k = N + \bar{k} + 1 = \bar{k} + 1$.


Left shift can therefore be done by first pre shifting right by 1 and then right shifting by the complement.

Logical and arithmetic shifts are similar to rotate except that the bits at one end or the other are replaced by 0 or sign bit.



Funnel Shifter

 Creates a $2N-1$ bit input word Z from A and kill variables. It then selects N -bit field from Z according to shift amount.



Shift Style	$Z_{2N-2:N}$	Z_{N-1}	$Z_{N-2:0}$	Offset
Logical Right	0	A_{N-1}	$A_{N-2:0}$	k
Logical Left	$A_{N-1:1}$	A_0	0	$\bar{k}$
Arithmetic Right	A_{N-1}	A_{N-1}	$A_{N-2:0}$	k
Arithmetic Left	$A_{N-1:1}$	A_0	0	$\bar{k}$
Rotate Right	$A_{N-2:0}$	A_{N-1}	$A_{N-2:0}$	k
Rotate Left	$A_{N-1:1}$	A_0	$A_{N-1:1}$	$\bar{k}$

