

第11回の内容

- ・ 三相交流発電機の基本式
- ・ 無負荷三相交流発電機の故障計算

キーワード: 一線地絡故障

中性点接地インピーダンス, 健全相電圧


対称成分

$$\dot{E}_0 = \frac{1}{3}(\dot{E}_a + \dot{E}_b + \dot{E}_c)$$

$$\dot{E}_1 = \frac{1}{3}(\dot{E}_a + \alpha\dot{E}_b + \alpha^2\dot{E}_c)$$

$$\dot{E}_2 = \frac{1}{3}(\dot{E}_a + \alpha^2\dot{E}_b + \alpha\dot{E}_c)$$
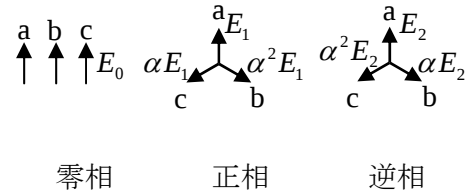
$$\alpha = e^{j\frac{2}{3}\pi} = e^{j\frac{4}{3}\pi} = -\frac{1}{2} + j\frac{\sqrt{3}}{2}, \quad \alpha^2 = e^{j\frac{4}{3}\pi} = e^{j\frac{2}{3}\pi} = -\frac{1}{2} - j\frac{\sqrt{3}}{2}, \quad 1 + \alpha + \alpha^2 = 0, \quad \alpha^3 = 1$$



4.2.1 対称分インピーダンス

(a) 同期機

$$\dot{Z}_2 < \dot{Z}_1, \quad \dot{Z}_0 \text{ は } \dot{Z}_1 \text{ の } 10\% \text{ 以下}$$

(b) 変圧器

$$\dot{Z}_2 = \dot{Z}_1, \quad \dot{Z}_0 = \dot{Z}_1 \text{ 又は接地方法でかわる}$$

(c) 送電線

$$\dot{Z}_2 = \dot{Z}_1, \quad \dot{Z}_0 \text{ は対地容量, インダクタンス}$$

(d) 三相对称負荷

$$\text{三相对称構造の静止機器は } \dot{Z}_2 = \dot{Z}_1$$

$$\dot{Z}_0 = \dot{Z}_1 \text{ 又は接地方法でかわる}$$

4.2.2 三相交流発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0$$


$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1 \dot{I}_1$$

$$\dot{V}_2 = -\dot{Z}_2 \dot{I}_2$$

導出:

発電機の端子電圧

$$\dot{V}_a = \dot{E}_a - \dot{v}_a, \quad \dot{V}_b = \dot{E}_b - \dot{v}_b, \quad \dot{V}_c = \dot{E}_c - \dot{v}_c$$

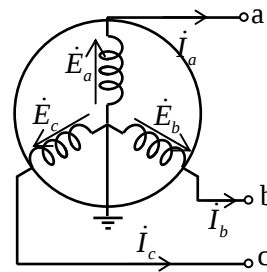ここで, $\dot{V}_a, \dot{V}_b, \dot{V}_c$: 端子電圧, $\dot{E}_a, \dot{E}_b, \dot{E}_c$: 起電力, $\dot{v}_a, \dot{v}_b, \dot{v}_c$: 発電機内部での電圧降下また, $\dot{E}_a = \dot{E}_a, \quad \dot{E}_b = \alpha^2 \dot{E}_a, \quad \dot{E}_c = \alpha \dot{E}_a$ 

端子電圧の対称分

$$\dot{V}_0 = \frac{1}{3} \{ (\dot{E}_a - \dot{v}_a) + (\dot{E}_b - \dot{v}_b) + (\dot{E}_c - \dot{v}_c) \}$$

$$\dot{V}_1 = \frac{1}{3} \{ (\dot{E}_a - \dot{v}_a) + \alpha (\dot{E}_b - \dot{v}_b) + \alpha^2 (\dot{E}_c - \dot{v}_c) \}$$

$$\dot{V}_2 = \frac{1}{3} \{ (\dot{E}_a - \dot{v}_a) + \alpha^2 (\dot{E}_b - \dot{v}_b) + \alpha (\dot{E}_c - \dot{v}_c) \}$$

より

$$\dot{V}_0 = \frac{1}{3} \{ (\dot{E}_a + \dot{E}_b + \dot{E}_c) - (\dot{v}_a + \dot{v}_b + \dot{v}_c) \}$$

$$\dot{V}_1 = \frac{1}{3} \{ (\dot{E}_a + \alpha \dot{E}_b + \alpha^2 \dot{E}_c) - (\dot{v}_a + \alpha \dot{v}_b + \alpha^2 \dot{v}_c) \}$$

$$\dot{V}_2 = \frac{1}{3} \{ (\dot{E}_a + \alpha^2 \dot{E}_b + \alpha \dot{E}_c) - (\dot{v}_a + \alpha^2 \dot{v}_b + \alpha \dot{v}_c) \}$$

ここで, $\dot{E}_a = \dot{E}_a, \quad \dot{E}_b = \alpha^2 \dot{E}_a, \quad \dot{E}_c = \alpha \dot{E}_a$ だから

$$\begin{aligned}\dot{V}_0 &= \frac{1}{3} \{ (\dot{E}_a + \alpha^2 \dot{E}_a + \alpha \dot{E}_a) - (\dot{V}_a + \dot{V}_b + \dot{V}_c) \} \\ &= -\frac{1}{3} (\dot{V}_a + \dot{V}_b + \dot{V}_c)\end{aligned}$$

$$\begin{aligned}\dot{V}_1 &= \frac{1}{3} \{ (\dot{E}_a + \alpha \alpha^2 \dot{E}_a + \alpha^2 \alpha \dot{E}_a) - (\dot{V}_a + \alpha \dot{V}_b + \alpha^2 \dot{V}_c) \} \\ &= \dot{E}_a - \frac{1}{3} (\dot{V}_a + \alpha \dot{V}_b + \alpha^2 \dot{V}_c)\end{aligned}$$

$$\begin{aligned}\dot{V}_2 &= \frac{1}{3} \{ (\dot{E}_a + \alpha^2 \alpha^2 \dot{E}_a + \alpha \alpha \dot{E}_a) - (\dot{V}_a + \alpha^2 \dot{V}_b + \alpha \dot{V}_c) \} \\ &= -\frac{1}{3} (\dot{V}_a + \alpha^2 \dot{V}_b + \alpha \dot{V}_c)\end{aligned}$$

発電機1相あたりの零相, 正相, 逆相インピーダンスを $\dot{Z}_0, \dot{Z}_1, \dot{Z}_2$ とし, $\dot{I}_0, \dot{I}_1, \dot{I}_2$ を零相, 正相, 逆相電流とすると, 発電機各相電圧降下は

$$\dot{V}_a = \dot{Z}_0 \dot{I}_0 + \dot{Z}_1 \dot{I}_1 + \dot{Z}_2 \dot{I}_2$$

$$\dot{V}_b = \dot{Z}_0 \dot{I}_0 + \alpha^2 \dot{Z}_1 \dot{I}_1 + \alpha \dot{Z}_2 \dot{I}_2$$

$$\dot{V}_c = \dot{Z}_0 \dot{I}_0 + \alpha \dot{Z}_1 \dot{I}_1 + \alpha^2 \dot{Z}_2 \dot{I}_2$$

よつて,

$$\dot{V}_0 = -\frac{1}{3} (\dot{V}_a + \dot{V}_b + \dot{V}_c) = -\frac{1}{3} 3 \dot{Z}_0 \dot{I}_0 = -\dot{Z}_0 \dot{I}_0$$

$$\begin{aligned}\dot{V}_1 &= \dot{E}_a - \frac{1}{3} (\dot{V}_a + \alpha \dot{V}_b + \alpha^2 \dot{V}_c) \\ &= \dot{E}_a - \frac{1}{3} 3 \dot{Z}_1 \dot{I}_1\end{aligned}$$

$$\begin{aligned}\dot{V}_2 &= -\frac{1}{3} (\dot{V}_a + \alpha^2 \dot{V}_b + \alpha \dot{V}_c) \\ &= -\frac{1}{3} 3 \dot{Z}_2 \dot{I}_2\end{aligned}$$

以上から, 三相交流発電機の基本式は

$$\dot{V}_0 = \dot{E}_0 - \dot{Z}_0 \dot{I}_0 = -\dot{Z}_0 \dot{I}_0$$

$$\dot{V}_1 = \dot{E}_1 - \dot{Z}_1 \dot{I}_1 = \dot{E}_a - \dot{Z}_1 \dot{I}_1$$

$$\dot{V}_2 = \dot{E}_2 - \dot{Z}_2 \dot{I}_2 = -\dot{Z}_2 \dot{I}_2$$

ここで, $\dot{E}_0, \dot{E}_1, \dot{E}_2$ は $\dot{E}_a, \dot{E}_b, \dot{E}_c$ の対称分

4.2.4 無負荷三相交流発電機の故障計算

[1] 一線地絡故障

a 端子で地絡故障発生。端子条件は

$$(i) \quad \dot{I}_b = \dot{I}_c = 0$$

$$(ii) \quad \dot{V}_a = 0$$

$$\dot{I}_0 = \frac{1}{3} (\dot{I}_a + \dot{I}_b + \dot{I}_c) = \frac{1}{3} \dot{I}_a$$

$$\dot{I}_1 = \frac{1}{3} (\dot{I}_a + \alpha \dot{I}_b + \alpha^2 \dot{I}_c) = \frac{1}{3} \dot{I}_a \quad ,$$

$$\dot{I}_2 = \frac{1}{3} (\dot{I}_a + \alpha^2 \dot{I}_b + \alpha \dot{I}_c) = \frac{1}{3} \dot{I}_a$$

$$\dot{I}_0 = \dot{I}_1 = \dot{I}_2 \quad (iii)$$

(ii) 式に, 発電機の基本式を代入

$$\begin{aligned}\dot{V}_a &= \dot{V}_0 + \dot{V}_1 + \dot{V}_2 = -\dot{Z}_0 \dot{I}_0 + \dot{E}_a - \dot{Z}_1 \dot{I}_1 - \dot{Z}_2 \dot{I}_2 \\ &= \dot{E}_a - (\dot{Z}_0 \dot{I}_0 + \dot{Z}_1 \dot{I}_1 + \dot{Z}_2 \dot{I}_2) = 0\end{aligned}$$

(iii) 式を代入

$$\dot{I}_0 = \dot{I}_1 = \dot{I}_2 = \frac{\dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} = \frac{1}{3} \dot{I}_a \quad \text{だから}$$

$$\dot{I}_a = \frac{3 \dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2}$$

a 端子からみた発電機の内部インピーダンスは

$$\frac{\dot{E}_a}{\dot{I}_a} = \frac{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2}{3}$$

健全相 b,c の端子電圧は, $\dot{V}_0, \dot{V}_1, \dot{V}_2$ から求める

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0 = -\frac{\dot{Z}_0 \dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2}$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1 \dot{I}_1 = \dot{E}_a - \frac{\dot{Z}_1 \dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} = \frac{(\dot{Z}_0 + \dot{Z}_2) \dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2}$$

$$\dot{V}_2 = -\dot{Z}_2 \dot{I}_2 = -\frac{\dot{Z}_2 \dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2}$$

端子電圧は

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 = 0$$

$$\dot{V}_b = \dot{V}_0 + \alpha^2 \dot{V}_1 + \alpha \dot{V}_2 = \frac{(\alpha^2 - 1) \dot{Z}_0 + (\alpha^2 - \alpha) \dot{Z}_2}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a$$

$$\dot{V}_c = \dot{V}_0 + \alpha \dot{V}_1 + \alpha^2 \dot{V}_2 = \frac{(\alpha - 1) \dot{Z}_0 + (\alpha - \alpha^2) \dot{Z}_2}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a$$

[2] 二線地絡故障

a 端子で地絡故障発生。端子条件は

(i) $\dot{V}_b = \dot{V}_c = 0$

(ii) $\dot{I}_a = 0$

(i) と $\begin{aligned} \dot{V}_b &= \dot{V}_0 + \alpha^2 \dot{V}_1 + \alpha \dot{V}_2 = 0 \\ \dot{V}_c &= \dot{V}_0 + \alpha \dot{V}_1 + \alpha^2 \dot{V}_2 = 0 \end{aligned}$

より $\dot{V}_0 = \dot{V}_1 = \dot{V}_2$

3 相交流発電機の基本式より

$$\dot{E}_a - \dot{Z}_1 \dot{I}_1 = -\dot{Z}_0 \dot{I}_0 = -\dot{Z}_2 \dot{I}_2 \text{ だから}$$

$$\dot{I}_0 = -\frac{\dot{E}_a - \dot{Z}_1 \dot{I}_1}{\dot{Z}_0}, \quad \dot{I}_2 = -\frac{\dot{E}_a - \dot{Z}_1 \dot{I}_1}{\dot{Z}_2}$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 0 \text{ だから,}$$

$$\dot{I}_0 = \frac{-\dot{Z}_2}{\dot{Z}_0 \dot{Z}_1 + \dot{Z}_0 \dot{Z}_2 + \dot{Z}_1 \dot{Z}_2} \dot{E}_a$$

$$\dot{I}_1 = \frac{\dot{Z}_0 + \dot{Z}_2}{\dot{Z}_0 \dot{Z}_1 + \dot{Z}_0 \dot{Z}_2 + \dot{Z}_1 \dot{Z}_2} \dot{E}_a$$

$$\dot{I}_2 = \frac{-\dot{Z}_0}{\dot{Z}_0 \dot{Z}_1 + \dot{Z}_0 \dot{Z}_2 + \dot{Z}_1 \dot{Z}_2} \dot{E}_a$$

基本式より

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0 = \frac{\dot{Z}_0 \dot{Z}_2}{\dot{Z}_0 \dot{Z}_1 + \dot{Z}_0 \dot{Z}_2 + \dot{Z}_1 \dot{Z}_2} \dot{E}_a = \dot{V}_1 = \dot{V}_2$$

端子電圧は

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 = \frac{3\dot{Z}_0 \dot{Z}_2}{\dot{Z}_0 \dot{Z}_1 + \dot{Z}_0 \dot{Z}_2 + \dot{Z}_1 \dot{Z}_2} \dot{E}_a$$

故障電流は

$$\dot{I}_b = \dot{I}_0 + \alpha^2 \dot{I}_1 + \alpha \dot{I}_2 = \frac{(\alpha^2 - \alpha)\dot{Z}_0 + (\alpha^2 - 1)\dot{Z}_2}{\dot{Z}_0 \dot{Z}_1 + \dot{Z}_0 \dot{Z}_2 + \dot{Z}_1 \dot{Z}_2} \dot{E}_a$$

$$\dot{I}_c = \dot{V}_0 + \alpha \dot{I}_1 + \alpha^2 \dot{I}_2 = \frac{(\alpha - \alpha^2)\dot{Z}_0 + (\alpha - 1)\dot{Z}_2}{\dot{Z}_0 \dot{Z}_1 + \dot{Z}_0 \dot{Z}_2 + \dot{Z}_1 \dot{Z}_2} \dot{E}_a$$

[3] 二線短絡故障

bc 端子で短絡故障発生。端子条件は

(i) $\dot{V}_b = \dot{V}_c$

(ii) $\dot{I}_a = 0$

(ii) $\dot{I}_b = -\dot{I}_c$

$$\dot{I}_1 = \frac{\dot{E}_a}{\dot{Z}_1 + \dot{Z}_2}, \quad \dot{V}_1 = \frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a$$

$$\dot{I}_b = \frac{-j\sqrt{3}\dot{E}_a}{\dot{Z}_1 + \dot{Z}_2}, \quad \dot{V}_a = \frac{2\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a$$

[4] 三線短絡故障

(i) $\dot{I}_a + \dot{I}_b + \dot{I}_c = 0$

(ii) $\dot{V}_a = \dot{V}_b = \dot{V}_c$

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0 = 0$$

$$\dot{V}_1 = 0$$

$$\dot{V}_2 = 0$$

$$\dot{I}_a = \frac{\dot{E}_a}{\dot{Z}_1}$$