

RF Devices and RF Circuit Design for Digital Communication

Agenda

- Fundamentals of RF Circuits
- Transmission Line
- Reflection Coefficient & Smith Chart
- Impedance Matching
- S-matrix Representation
- Amplifiers & Unilateral Gain
- RF Devices
- Digital RF

2010/07/02

Wireless Communication Engineering I

- Fundamentals of RF Circuits
 - **Lumped-element** circuits: $\lambda \gg L$, L is a typical length of device.
e.g. $\lambda = 30$ cm for $f = 1$ GHz
 - **Distributed-element** circuits: $\lambda \sim L$
Lead Line becomes a coil and/or capacitance.

Historically **Rayleigh** analyzed an undersea cable based on distributed circuit concept.

→ **Image Impedance and Propagation Constant**

2010/07/02

Wireless Communication Engineering I

– Basic distributed element: **Transmission Line**

F-matrix of Transmission Line

$$F = \begin{bmatrix} \cos \theta & jZ_0 \sin \theta \\ j \sin \theta / Z_0 & \cos \theta \end{bmatrix}$$

Z_0 : Characteristic impedance of Transmission Line

θ : Phase delay $(= \beta \ell = \omega \sqrt{\epsilon \mu} \ell = \omega \ell / v)$

ℓ : length

v : velocity

2010/07/02

Wireless Communication Engineering I


Transmission Line



Inductance, Capacitance,
Filter, Impedance Transformer

2010/07/02

Wireless Communication Engineering I

 


Short-end

Open-end

2010/07/02

Wireless Communication Engineering I

 
Impedance Inverter : $Z_L \Rightarrow Z_{in}$



2010/07/02

Wireless Communication Engineering I

Shunt to Series Connection

 

2010/07/02

Wireless Communication Engineering I

Impedance Matrix of Transmission Line


$$Z = \frac{Z_o}{j \sin \theta} \begin{bmatrix} \cos \theta & 1 \\ 1 & \cos \theta \end{bmatrix}$$

$$= \frac{Z_o}{j} \left\{ \frac{1}{\theta} \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} + \sum_{n=1}^{\infty} \frac{2\theta}{\theta^2 - (n\pi)^2} \begin{bmatrix} 1 & (-1)^n \\ (-1)^n & 1 \end{bmatrix} \right\}$$

2010/07/02

Wireless Communication Engineering I

 Equivalent Circuit of Transmission Line by Foster Expansion



A Series Connection of Parallel Resonance Circuits

2010/07/02

Wireless Communication Engineering I

- Short (Open) - circuited load: → **Reactance element**
 $X_{in} = Z_o \tan \theta$: short-circuited load

$0 < \theta < \pi/2$: Inductance


$\theta \approx \pi/2$: Parallel resonance circuit

$\pi/2 < \theta < \pi$: Capacitance

- Stub
- Quarter-wavelength Transformer
- **Matching coating lense**

2010/07/02

Wireless Communication Engineering I

 

Short-terminated Line

Wireless Communication Engineering I

2010/07/02

- Reflection coefficient (Γ) and Load Impedance (Z_L)

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} : \text{Bilinear mapping}$$


Z_0 : reference characteristic impedance

Circle to Circle Mapping
(Moebius Transform)

2010/07/02

Wireless Communication Engineering 1

Smith Chart

 

2010/07/02

Wireless Communication Engineering 1

$$\text{Re}(Z_L) > 0 : |\Gamma| < 1 \text{ (Passive)}$$

$$\text{Re}(Z_L) = 0 : |\Gamma| = 1 \text{ (Lossless)}$$

Reflection type phase modulator

$$\text{Re}(Z_L) < 0 : |\Gamma| > 1 \text{ (Active)}$$

Reflection type amplifier

2010/07/02

Wireless Communication Engineering 1

- Voltage Standing Wave Ratio (VSWR) ≥ 1

$$\text{VSWR} = \frac{V_{\max}}{V_{\min}} = \frac{V_i + V_r}{V_i - V_r}$$

$$|\Gamma| = \frac{V_r}{V_i} = \frac{\text{VSWR} - 1}{\text{VSWR} + 1}$$

V_i : incident wave

V_r : reflected wave

- Special Terminations / Circuits

– Matched load: ($Z_L = Z_0$) $\rightarrow \Gamma = 0$, No reflection

2010/07/02

Wireless Communication Engineering 1

– Smith-chart and its usage

- Smith-chart (Bell Lab. 1950's)

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \theta}{Z_0 + jZ_L \tan \theta}$$


$$Z_L \rightarrow \tilde{Z}_L = \frac{Z_L}{Z_0} \rightarrow \Gamma_L = \frac{\tilde{Z}_L - 1}{\tilde{Z}_L + 1} \rightarrow$$

$$\Gamma_{in} = \Gamma_L \exp^{-j2\theta} \rightarrow \tilde{Z}_{in} = \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \rightarrow Z_{in}$$

2010/07/02


Wireless Communication Engineering I

Impedance Transforming

 

2010/07/02

Wireless Communication Engineering I


 


Smith Chart

2010/07/02

Wireless Communication Engineering I

  - How to use Smith-chart
- Matching Circuit Design



Single-stub Matching

2010/07/02


Wireless Communication Engineering I

– Microstrip Line

- Effective permittivity and guided wavelength
- Characteristic Impedance
- Several notes : Finite conductor thickness

2010/07/02

Wireless Communication Engineering I

 


Microstrip Line (Effective Permittivity)

2010/07/02

Wireless Communication Engineering I

Coaxial Line
 
$$Z_0 = \frac{138}{\sqrt{\epsilon_r}} \log \frac{b}{a}$$




2010/07/02

Wireless Communication Engineering I


Pair-cable Line
 
$$Z_0 = 120 \cosh^{-1} \left(\frac{b}{a} \right)$$




2010/07/02

Wireless Communication Engineering I

 

2010/07/02

Wireless Communication Engineering I

 

2010/07/02

Wireless Communication Engineering I


Meta Material

- Right-Hand Transmission Line
- Left-Hand Transmission Line
- Composite RH/LH Transmission Line
- Compact Directional Coupler
- Super-Lense


2010/07/02

Wireless Communication Engineering I

RHTL




 




LHTL

 

2010/07/02

Wireless Communication Engineering I

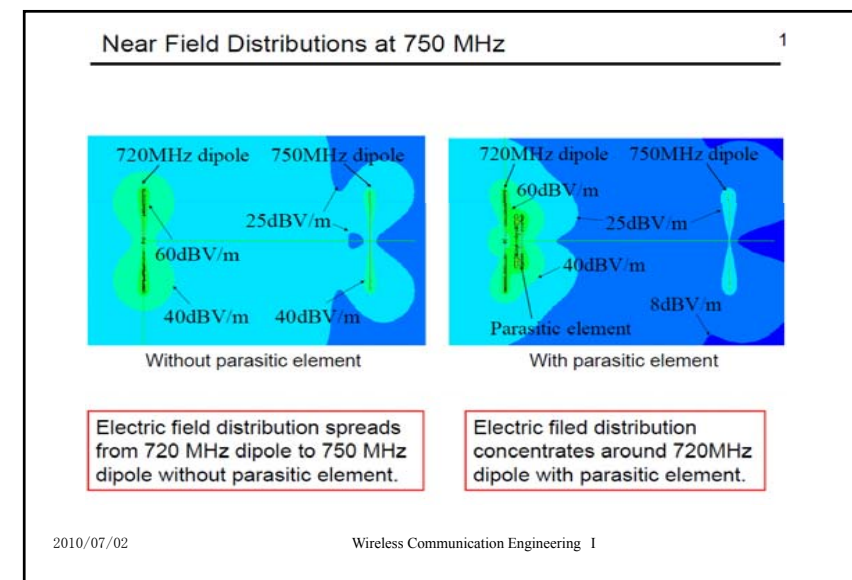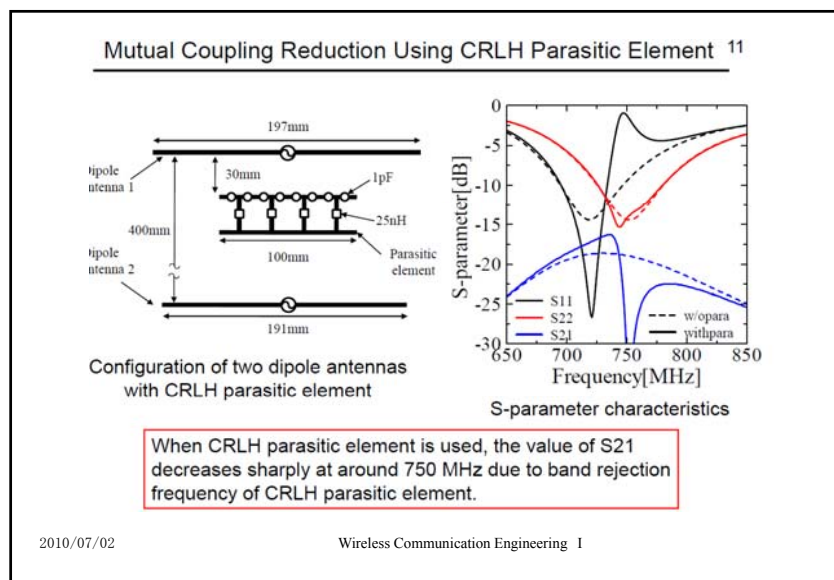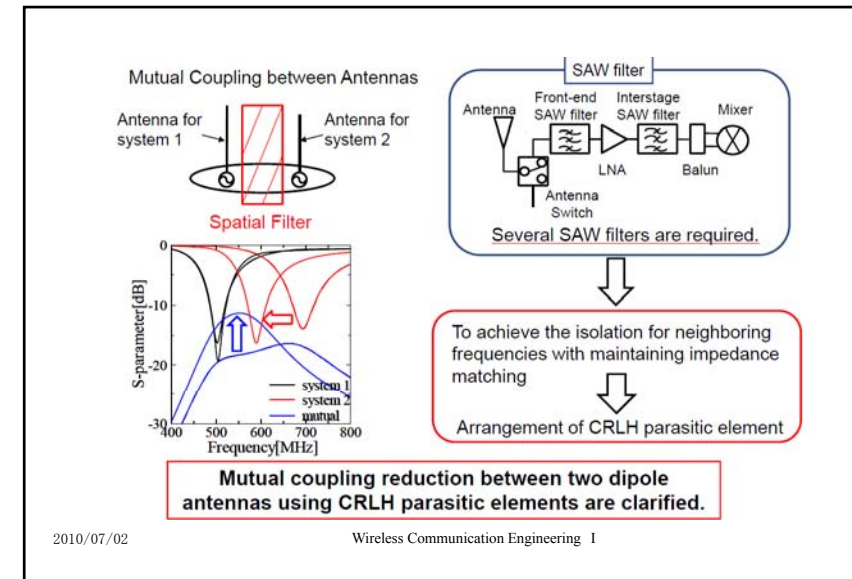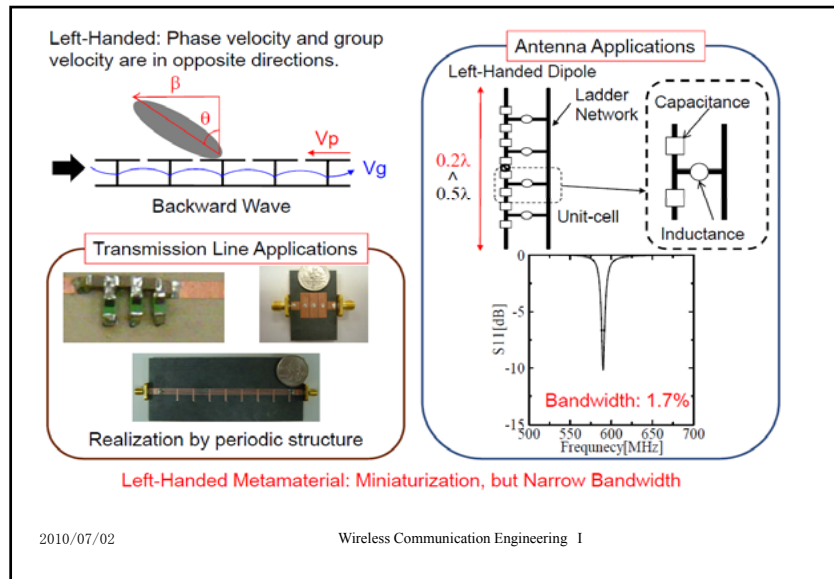

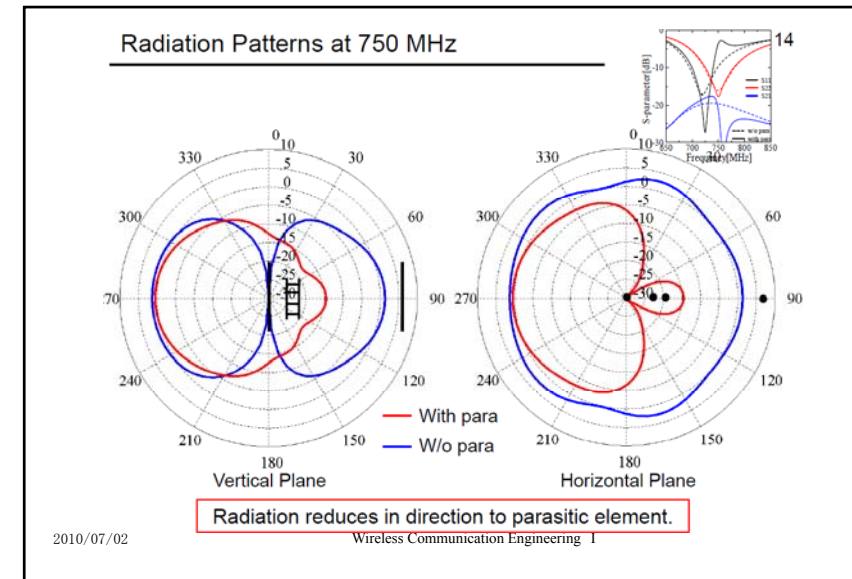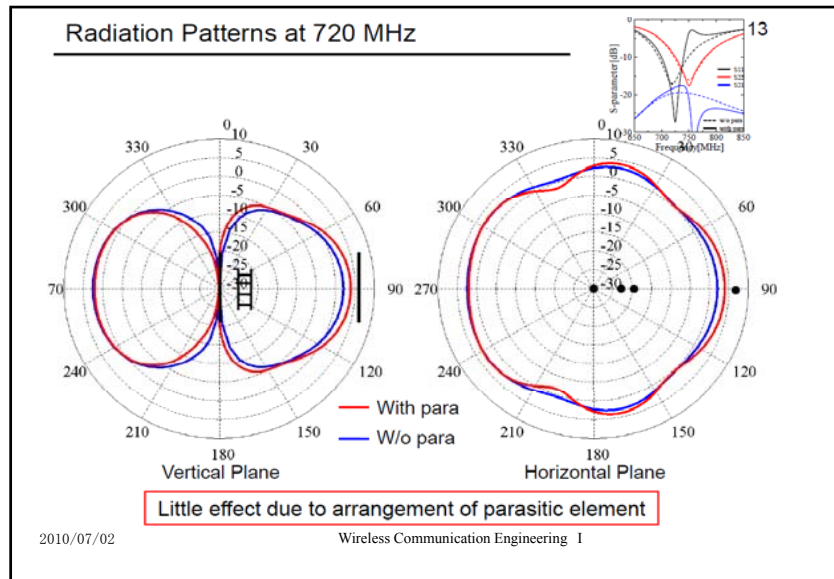

• S-parameter and RF Circuit Design

– S-parameter (1950's ← Nuclear Physics)

voltage, current → incident wave, reflected wave

impedance → reflection coefficient

impedance matrix → scattering matrix, $[S]$

2010/07/02

Wireless Communication Engineering I

For **lossless** circuit, **S-matrix** = **Unitary Matrix**

For **lossy** circuit, $S^\dagger S \leq I$ **Para-unitary**

For **Reciprocal** circuit, S-matrix = **Symmetric matrix**

2010/07/02

Wireless Communication Engineering I

SVD (Singular Value Decomposition)

$$S = U^\dagger D V \quad (\text{Youla})$$

U, V : Unitary matrix (Lossless Circuit)

D : Diagonal Matrix (\rightarrow Isolated n -port circuit)

$$D = \text{Diag}[\lambda_1, \dots, \lambda_n]$$


$\lambda_i < 1 \quad \rightarrow$ resistance

$\lambda_i > 1 \quad \rightarrow$ negative resistance

2010/07/02

Wireless Communication Engineering I

Generalization of Darlington realization

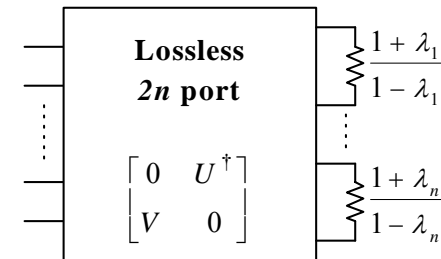

2010/07/02

Wireless Communication Engineering I

– Basics of RF Circuit Design

- Impedance Matching Circuits

$$Z_g = Z_L^*$$


Z_g : Generator Impedance

Z_L : Load Impedance

2010/07/02

Wireless Communication Engineering I

Conjugate Matching

 

2010/07/02

Wireless Communication Engineering I

Unilateral Transducer Gain G_{TU}

(For the case, $S_{12} = 0$ Reverse transfer coefficient from output to input)

$$\text{FET } S\text{-parameter} \begin{vmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{vmatrix}$$

$$G_{TU} = \frac{(1 - |\Gamma_s|^2)}{|1 - S_{11}\Gamma_s|^2} \cdot |S_{21}|^2 \cdot \frac{(1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2}$$


$$= G_s \cdot G_0 \cdot G_L$$

$$G_{TU, \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2}$$

2010/07/02

Wireless Communication Engineering I


Input and Output Matching Circuit

 

2010/07/02

Wireless Communication Engineering I

Unilateral Gain U : Mason's Invariant

 

Unilateralization of a two-port network

2010/07/02

Wireless Communication Engineering I


Circuit Invariant

- Unilateral Gain (U)
- Maximum Available Gain (MAG)
- Noise Measure (M)
- 2-state diode (m, Q)
- Circulator Invariant (α)
- Directional Coupler Invariant (K)

2010/07/02

Wireless Communication Engineering I

Available Power

 

2-state device

- On-state impedance Z_1 , Off-state impedance Z_2
- $M = |Z_1 - Z_2| / |Z_1 + Z_2^*| \Rightarrow$ Invariant w.r.t. Lossless 2port connection
- $M = |\Gamma_1 - \Gamma_2| / |1 - \Gamma_1 \Gamma_2^*| \Rightarrow$ Optimum BPSK Direct Modulation Design

2010/07/02

Wireless Communication Engineering I

• RF Devices

– Passive Components / Circuits

• Reactance Elements

– Distributed-element:

Open-stub, Short-stub, Line Gap

Wide Line, Narrow Line

– Lumped-element:

Spiral Inductor, Gap Capacitor, Thin Film Capacitor

2010/07/02

Wireless Communication Engineering I

Attenuators:

Thin Film Resistor

• Impedance Transformers:

Quarter-wavelength Impedance Transformer

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

2010/07/02

Wireless Communication Engineering I

- **Resonator:**

- Lumped Element Type
- Microstrip Line Type
- Dielectric Resonator Type (Good Ceramic)

2010/07/02


Wireless Communication Engineering I

- **Distributing Components / Circuits**

- Directional Coupler:
 - Power Monitor, Balanced Type Modulator / Amplifier / Mixer
 - Lossless reciprocal matched two-fold symmetry 4-port**
 - **Perfect Directional Coupler with 90deg. Phase Difference**
 - Coupled Line Type
 - Inter-digital Type
 - Branch Line Type
 - Rat-race Type

2010/07/02

Wireless Communication Engineering I

 

Branch-line Coupler

2010/07/02

Wireless Communication Engineering I

- **Power Divider / Combiner:**

Perfect Matching + Perfect Isolation → Absorbing Resistance

- **Filter**

- Low Pass Filter (LPF):
 - L, C Ladder Filter
- Band Pass Filter (BPF):
 - Half-wavelength transmission line resonator
- Band Stop Filter (BSF):

2010/07/02

Wireless Communication Engineering I


• Transmission Scheme and RF Circuits

Objectives: Low Power Consumption,
Higher Frequency, Small Size,
Low Weight

2010/07/02

Wireless Communication Engineering I

Block diagram of Transceiver

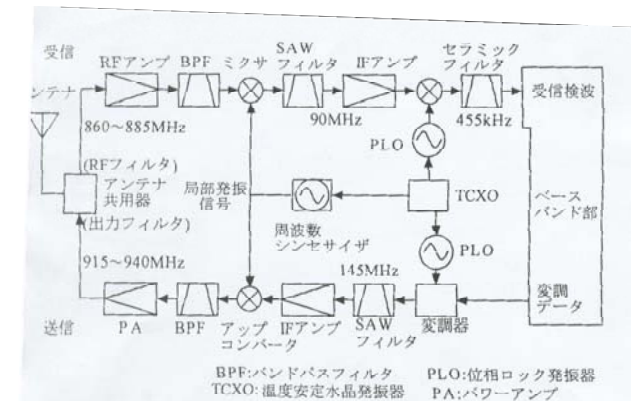

2010/07/02

Wireless Communication Engineering I


– Basic configuration of RF Circuits: Super-Heterodyne

Mixer: Up-conversion Down-conversion
Amplifier: Power Amp. (TX) Low Noise Amp. (RX)
Oscillator: Local Oscillator
Filter: LPF, BPF

2010/07/02

Wireless Communication Engineering I


TX Level Diagram

 

2010/07/02

Wireless Communication Engineering I

RX Level Diagram

 

2010/07/02

Wireless Communication Engineering I


Digital RF Circuits

- RF-CMOS Technology
- Analog Signal Processing & Digital Signal Processing
- Continuous Time & Discrete Time
- Direct Conversion & Sampling
- Built-in RF Self Test & Calibration

2010/07/02

Wireless Communication Engineering I


Typical Cell-Phone Block Diagram

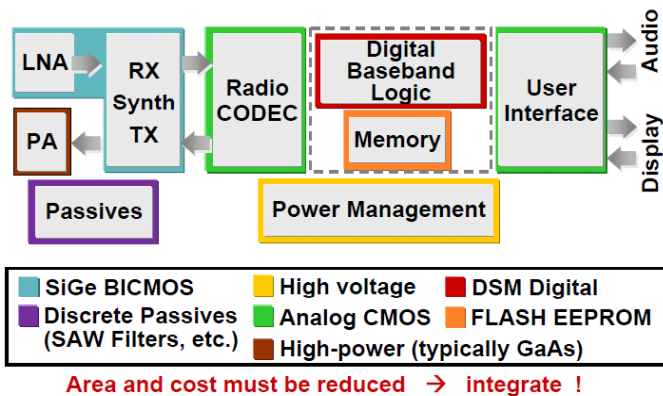

2010/07/02

Wireless Communication Engineering I

SoC Drives Cost Reduction

 

◆ SoC Integration Includes:

- ◆ Digital baseband
- ◆ SRAM
- ◆ Power management
- ◆ Analog
- ◆ RF
- ◆ Processors & Software


◆ The DRP technology enables digital implementation of traditional analog RF functions in standard CMOS

- ◆ Most advanced process technology used to maximize integration while minimizing cost
 - ◆ 90nm (shipping)
 - ◆ 65nm (mature design)
 - ◆ 45nm and beyond (preliminary)

2010/07/02

Wireless Communication Engineering I


DRP/SoC Proven Across Many Products

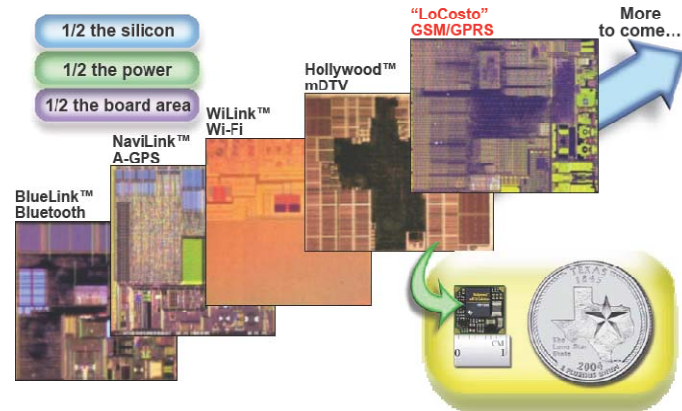

2010/07/02

Wireless Communication Engineering I

Analog RF Challenges in DSM CMOS

 


- Power supply voltage overhead – must scale to ~1Volt
- Passives – need high quality inductors, caps, etc.
- Noise/clock coupling – time-align to avoid interference
- Development time – should not delay node migration of digital baseband processor portion.
- Cost – need to minimize multiple pass testing and yield loss

2010/07/02

Wireless Communication Engineering I

Digital Transceiver Architecture

 


Conventional Direct Conversion is a Great Technology
... but not well suited for CMOS integration
... and digital techniques improve perf/power
... and digital provides a path to SDR!!

2010/07/02

Wireless Communication Engineering I

The DRP Approach for Transceivers

 


- Minimize analog and RF circuitry**
 - Self-calibrate remaining analog (with dedicated processor)
 - Relax passive requirements as much as possible
- Digital approach speeds debug and development**
- Self-test and calibration made possible**
- Production yield dominated by silicon defect density**

2010/07/02

Wireless Communication Engineering I

The DRP Approach (continued)

 


- Move functions to domains of CMOS-process strengths
 - Operate in fine time resolution, avoid fine voltage resolution
 - Inductor area could be equal to ~100K gates (use digital!)
 - Use switched cap techniques – excellent matching in DSM CMOS (not sensitive to process variations)
 - Logic and switched cap circuits can work well at low voltage

2010/07/02

Wireless Communication Engineering I


DRP RF Architecture

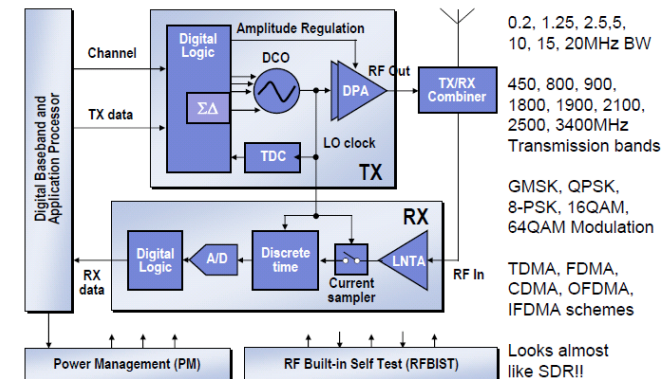

2010/07/02

Wireless Communication Engineering I

All-Digital PLL Vs. Conventional PLL

 


- The ADPLL is "Analog" only in FF, TDC and DCO
- Varactors operate in low sensitivity states ("on" or "off")
- Self-calibration is easy -- DCO gain can be assessed numerically
- Can lock very fast, dynamically change loop bandwidth (<10μsec), and collect register settings for "instant restart" on frequency.

2010/07/02

Wireless Communication Engineering I

Drawbacks of Conventional Analog PLL

 


- Many analog functions = multiple noise sources
- Varactors in VCO are sensitive (high tuning factor, i.e. KVCO)
- Loop filter may be large, leaky capacitors (for open loop "freeze"), variances in passives...
- Hard to calibrate
- Lock times can be long (>100μsec)

2010/07/02

Wireless Communication Engineering I


All-Digital PLL (ADPLL)

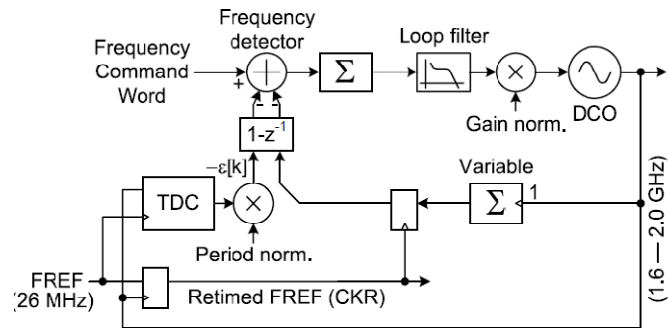

2010/07/02

Wireless Communication Engineering I


Digitally-Controlled Oscillator Core

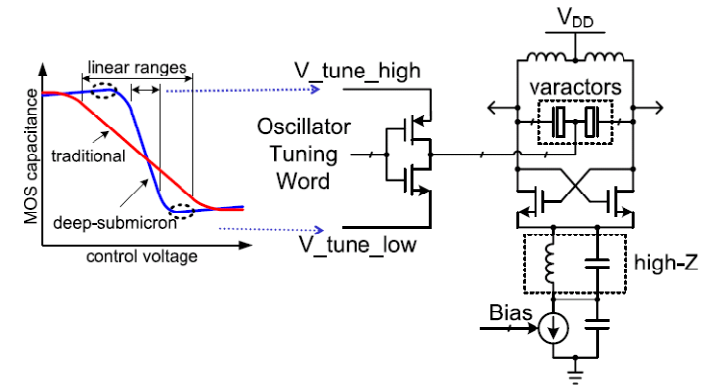

2010/07/02

Wireless Communication Engineering I

DCO Varactor Banks

 


High-speed dithering and dynamic element matching are used to achieve high resolution (LSB = ~1.5Hz).

2010/07/02

Wireless Communication Engineering I

Time-to-digital Converter (TDC)

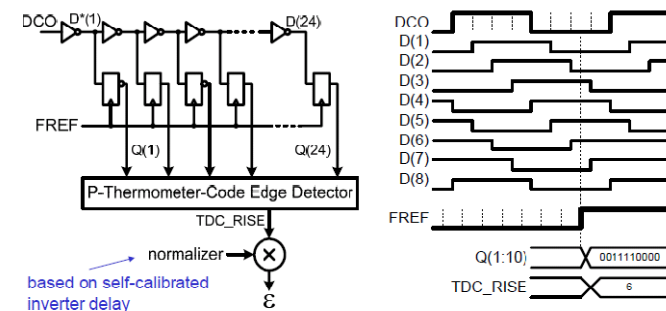- ◆ Quantized phase detector with resolution of about 20 ps
- ◆ DCO clock passes through the inverter chain
- ◆ Delayed outputs are sampled by FREF




2010/07/02

Wireless Communication Engineering I

Production Testing Simplification

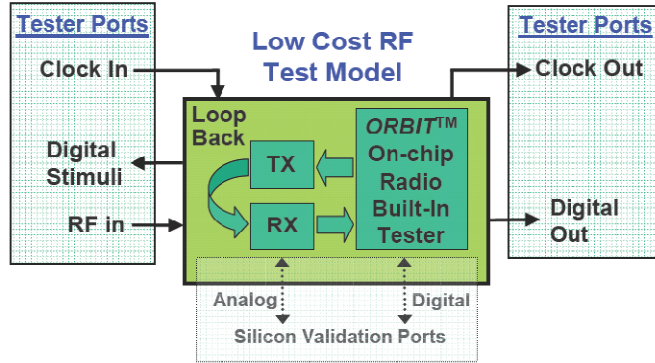
- Extensive use of built-in-testing capabilities to reduce test costs.
- Tester is simple (low cost) and test time is minimal.



2010/07/02

Wireless Communication Engineering I

The DRP Technology - Summary

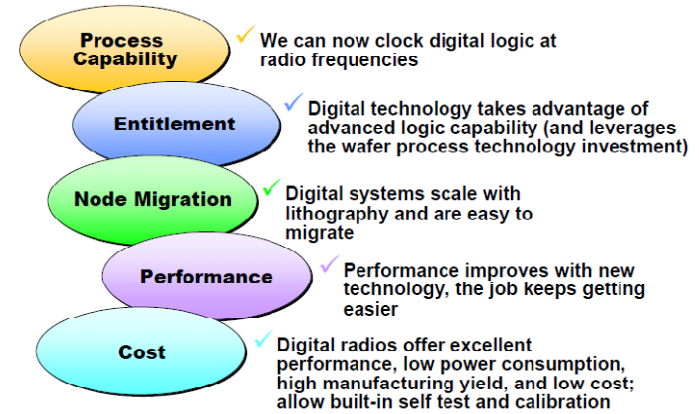

2010/07/02

Wireless Communication Engineering I