

Mechanical-to-Electrical Energy Conversion

12. Variable Speed Operation of Induction Generators

Hideaki Fujita

fujita@ee.e.titech.ac.jp




Contents of Today

1. System Configurations
2. Fundamental principles
3. Fundamental characteristics.




Self Excitation Induction Generator

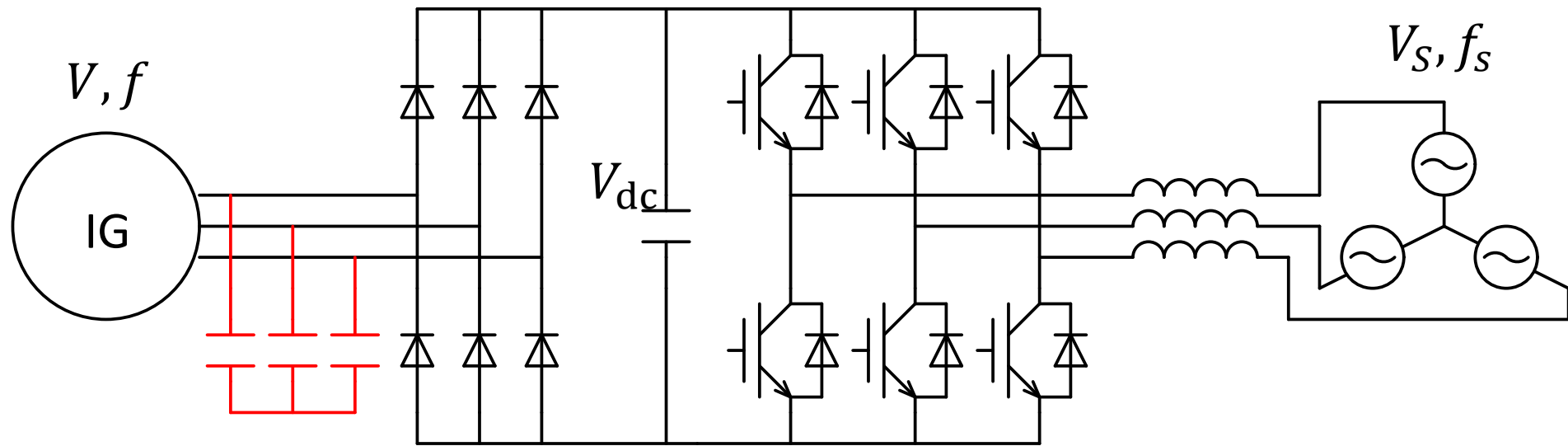

- Additional Capacitors are required to supply the excitation current to the generator.


Application of a PWM Rectifier

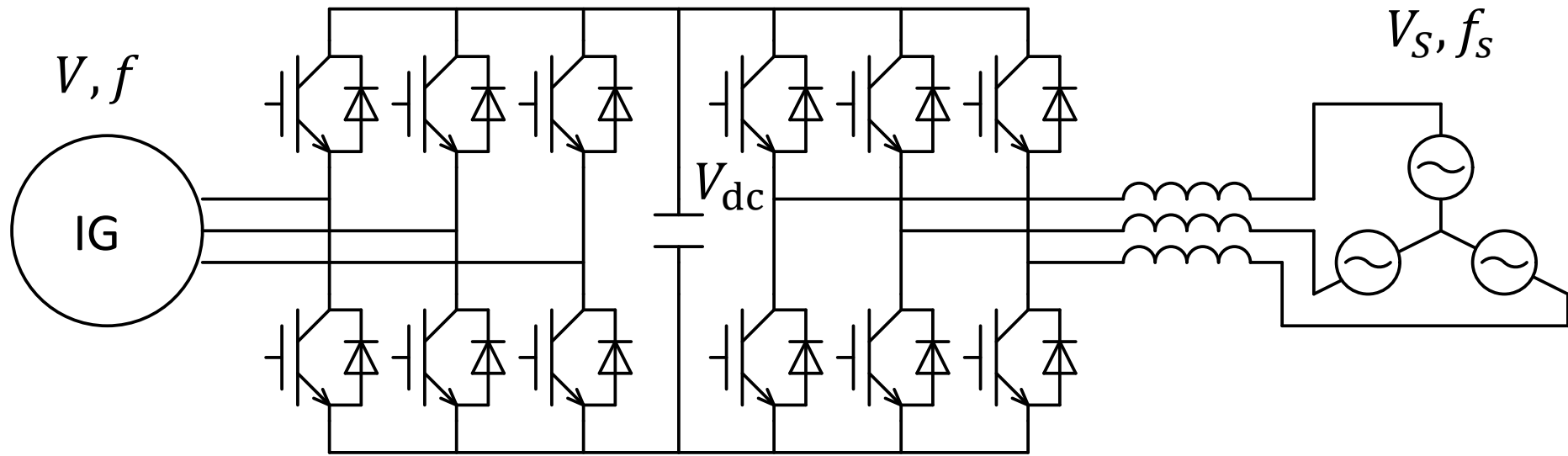

PWM Rectifier:

- Supply the excitation current.
- Boost-up Capability
- Adjustment of Voltage and Frequency

ω_s vs T at a constant E_1/ω

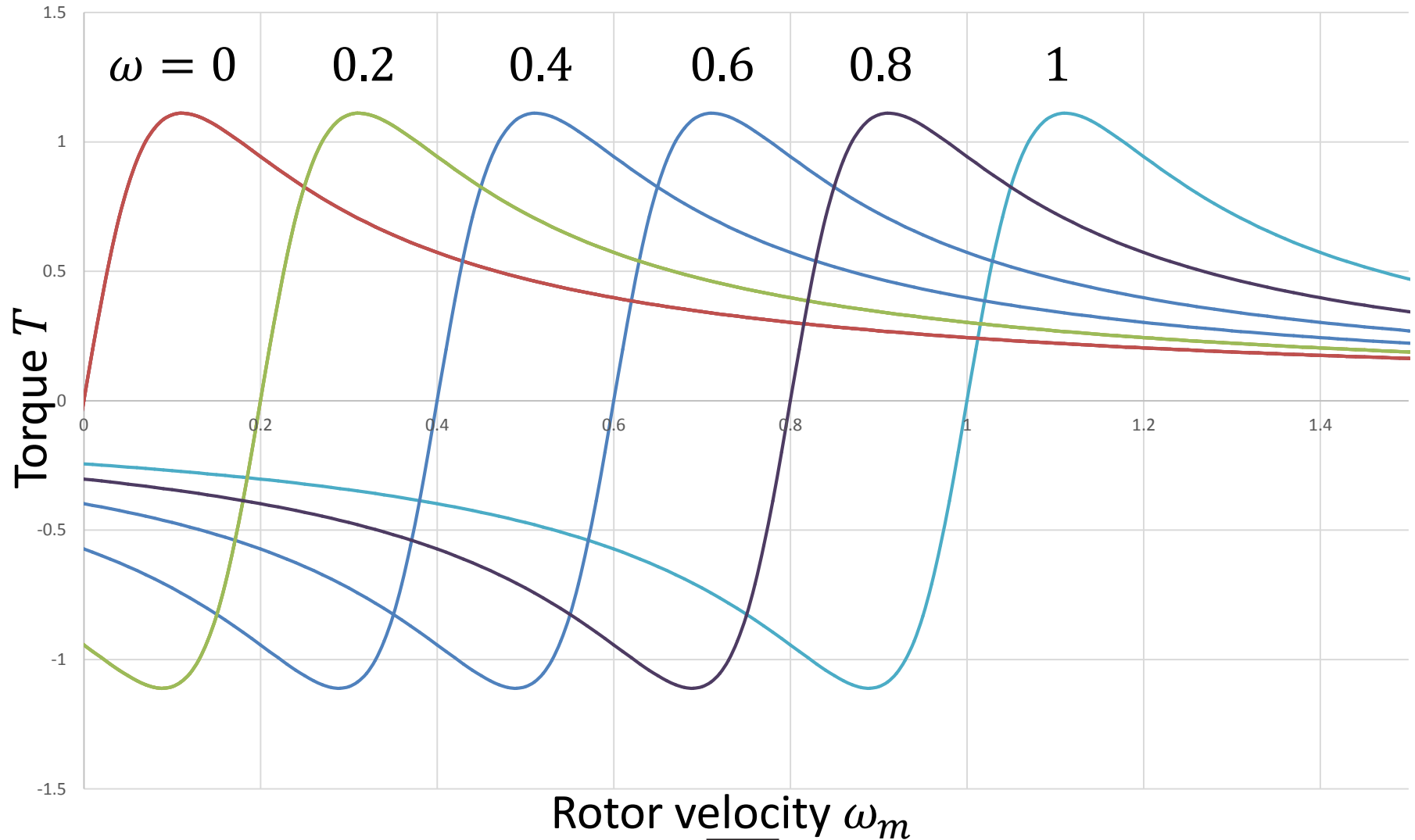

To be Continued in the Lecture.....