

Digital Integrated Circuits 1: Fundamentals

Atsushi Takahashi


Department of Information and Communications Engineering

School of Engineering

Tokyo Institute of Technology

VLSI and Computer System

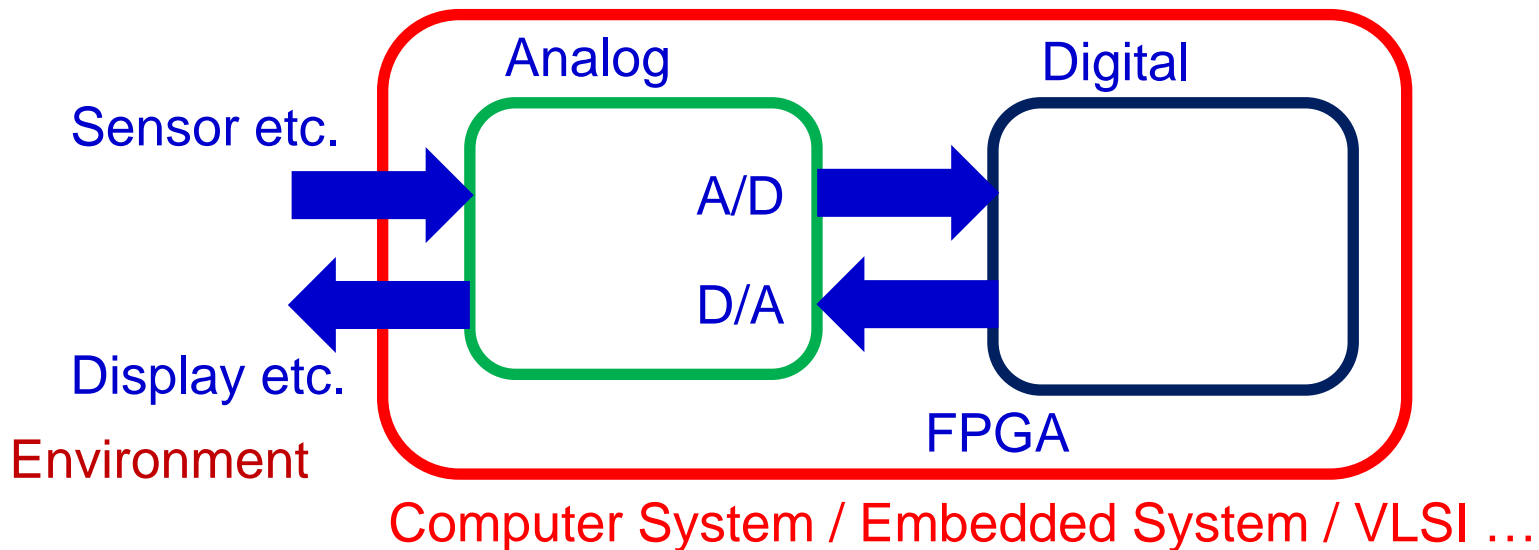
- VLSI (Very Large Scale Integrated Circuits)
- Computer System



Architecture : Microprocessor / Deep Neural Network ...
Hardware : Logic Functions, Hardware Description Language ...
Software : Algorithm, Real Time Operating System ...
Design : Synthesis, Compiler, Physical Design ...

VLSI

 - Very Large Scale Integrated Circuits
- Contained in a variety of products
 - Computer
 - CPU, Network
 - Consumer electronics
 - Digital TV, DVD, Mobile phone, iPad, ...
 - Automotive
 - Navigation, Engine Control, ...
 - Autonomous Driving
 - Others




History of VLSI

■ 1959

- Transistors, diffusive resistances, wires are fabricated on a silicon substrate by using lithography and etching technology
- Few elements are in one chip
- **Robert Noyce** (A founder of Intel)
- **Jack Kilby** (Nobel Prize in Physics, 2000)

■ Moore's Law: #elements in one chip

 - Twice in 1.5 year (+58% per year)
- Now : More than 1G elements in one chip




■ Makimoto's Wave


- Alternate standardization and customization in 10 year cycles

Transistor Switch

 - Basic Item to control the voltage of a node
- nMOS (npn type) Transistor




3D Image

 

Top view Image

MOSFET: MOS field-effect transistor

 Metal: Poly-silicon
Oxide: SiO₂: Insulator
Semiconductor: Silicon



Symbol

Historical Computers in Japan

- Relay Computer, Fujitsu
 - Relay-elements from telephone exchange equipment
 - Toshio Ikeda
 - FACOM100, 1954
 - FACOM128A, 1956
 - FACOM128B, 1958
 - Commercial computer
 - Still working model was manufactured in 1959
 - IPSJ Information Processing Technology Heritage

Historical Computers in Japan

- Parametron Computer, NEC
 - SENAC-1(NEAC1102), 1958
 - First commercial computer by NEC
 - Hitoshi Watanabe
 - IEEE Kirchhoff Award 2010
 - » Filter design theory and computer-aided circuit design
 - IPSJ Information Processing Technology Heritage


Historical Computers in Japan

- Electronic Calculators, Sharp
 - CS-10A, 1964
 - Germanium-Transistor
 - First all-transistor diode electronic desktop calculator in the world
 - 25 kg
 - 535,000 Yen (= 1,500 US\$)
 - Initial monthly salary of graduate = 21,526 Yen
 - Toyota Corolla 1100cc = 432,000 Yen (1966)
 - 50th Anniversary G“50 Limited” = 2,400,000 Yen (2016)
 - IEEE milestone 1964-1973
 - IPSJ Information Processing Technology Heritage

VLSI Design / Manufacturing



Integration of Various Technologies

 - Device Manufacture
 - Make transistors small
 - Mask Design, Exposure, Polishing, Dicing
- Circuit Design, Layout Design
 - High Speed, Low Power, Reliability
- Packaging, Printed Circuit Board
 - Wire Bonding
- System Design
- Software Design
- Marketing



Moore's law (1965)

  - Gordon E. Moore (A founder of Intel)
 - #Tr/Chip doubling every 18 months (or two years)



Inevitable Paradigm Shifts

- The number of transistors in one chip becomes 100 times in every 10 years
- The smaller the feature size of VLSI chip is
 - the higher the performance of VLSI is
 - the larger the difficulty in VLSI design is
- Time-to-market constraint
- Performance (area, speed, power...) constraint


Change of Names

- IC: Integrated Circuit (1960-)
- LSI: Large Scale IC (1970-)
- VLSI: Very Large Scale IC (1980-)
- ULSI: Ultra Large Scale IC (1990-)

- System LSI
- SoC (System on Chip)
- SiP (System in Package),...


VLSI Manufacture vs. Design

 - #transistor in VLSI chip +58%/year
- VLSI design productivity +21%/year



Makimoto's Wave (1987)

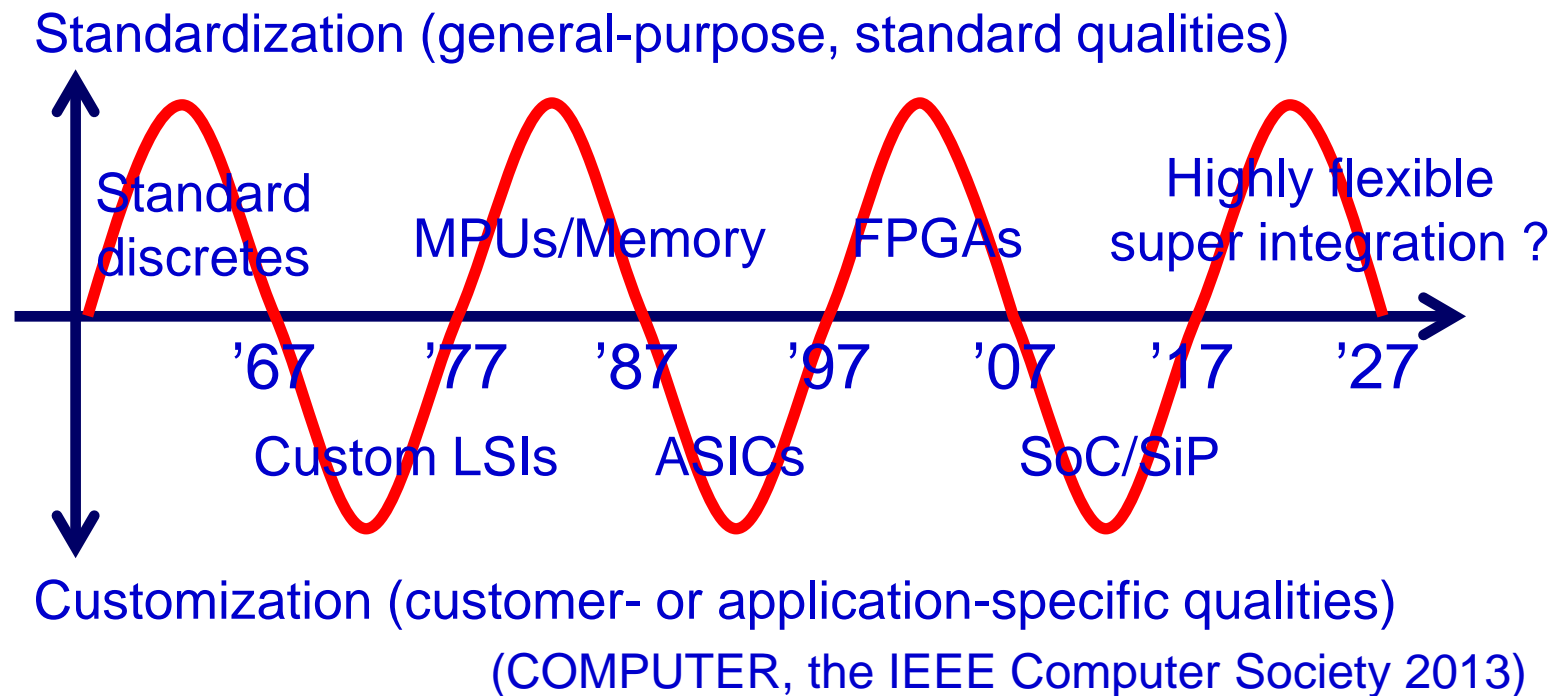- Tsugio Makimoto (former Sony CTO etc.)
 - Semiconductor industry's cyclical alternation between standardization and customization



Digital Integrated Circuits

■ What is Digital?

- Digital vs. Analog
 - Discrete vs. Continuous
 - Integer or Boolean (0,1) vs. Real
 - Countable vs. Uncountable

■ What is Digital Integrated Circuits?

- Realize Boolean Function: $\{0,1\}^n \rightarrow \{0,1\}^m$
- Objective
 - Cost : Size, Speed, Power, etc.

Why Digital Integrated Circuits

■ Why Digital?

- Digital Applications
 - Digital Signal Processing
 - Video Processing,...
- Robustness for Instability and Uncertainty
- High Performance and Low Cost
- VLSI (Very Large Scale Integrated Circuit)

Digital System Implementation

■ Combinatorial Circuits



- Outputs are determined by Inputs
- Every Boolean Function is realized
- Often impractical due to size and speed

■ Sequential Circuits

- State Machine
- Outputs are not determined only by current inputs
- Outputs depend on input sequence as well
- Most Digital System Implementation


Combinatorial Circuits

 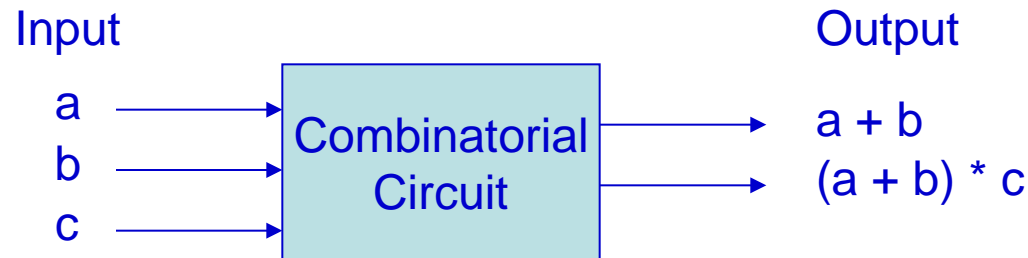- Inputs are given at a time
- Outputs are generated at a time




Sequential Circuits

 - Inputs are given sequentially
- Input history is stored in circuit
- Outputs are generated sequentially by using inputs and stored data (history, state)



Sequential Circuit Implementation

 - Performance depends on
 - State-machine itself
 - Time to transit from one state to another
 - Correct output must be recognized
 - Correct state must be stored




Synchronous Circuits

- Progresses in Design Automation, but still require human intelligence due to huge design space
- **Synchronous** Circuit Implementation
 - Synchronization by Global Clock
 - Physical Solution
- **Asynchronous** Circuit Implementation
 - Synchronization without Global Clock
 - **Self-Synchronous**
 - Logical Solution


Typical Synchronous Circuits

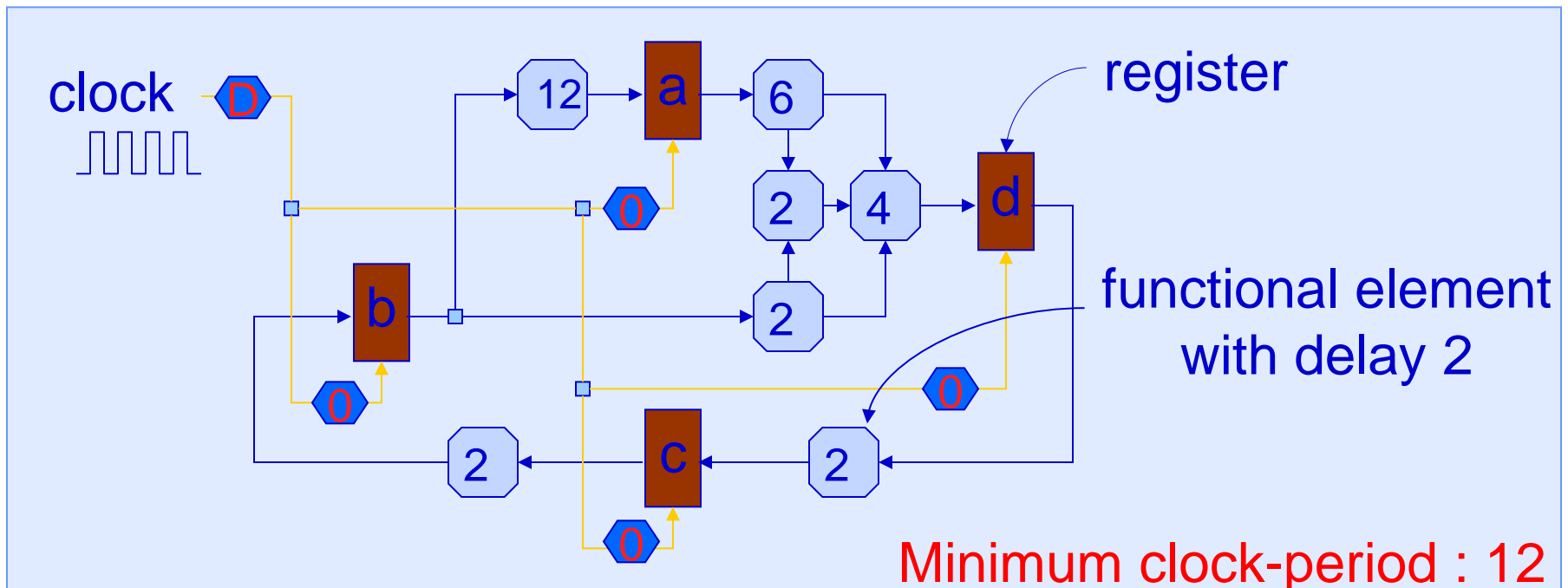- Every register (memory) is ticked by clock
 - Periodically (same period)
 - Simultaneously (same timing)
- Complete-synchronous circuit



Typical Asynchronous Circuits

 - Synchronization by Handshake Protocol
 - Request and acknowledge
 - 2-wire 2-phase implementation



Wire value	Status
00	Not ready
01	0
10	1
11	Not valid

2-wires for 1-signal

Synchronous vs. Asynchronous

■ Synchronous Circuit

- overhead of clock circuitry
- simultaneous clock distribution becomes harder
- needs innovation on clock distribution

■ Asynchronous Circuit

- overhead of circuitry that guarantees stability
- relatively slow to maintain delay insensitivity
- needs practical delay assumption


■ Mixture of Synchronous and Asynchronous Technique

Digital Integrated Circuit Synthesis

- How to generate a Synchronous Circuit?
 - Combinatorial circuit
 - Sequential circuitthat realizes a given Boolean Function
- Optimization Targets
 - Circuit Size
 - Speed
 - Power
 - etc.

Typical VLSI Design Flow

 
Behavioral specification (C, VHDL, data flow graph, etc.)



high-level synthesis

RTL description


(registers, modules, MUX, etc.)

 

logic synthesis

Gate level circuit

(NAND, NOR, etc.)

 

physical (layout) synthesis

Layout


Change of Design Method

■ Design Method

- Manual Design
 - Circuit Diagram, Mask
- Computer Aided Design
 - Boring simple tasks
- Design Automation
 - Inferior quality but used since a circuit is too big to design manually

■ Design Objectives

 
- Area (Request from manufacturing, Yield, Cost)
- Speed (Request from market, Emergence of PC)
- Power (Emergence of Mobile products)
- Noise (Influence to TV, Medical products)



Change of Design Style

History of Standardization and Abstraction

 
- ✓ Overcome performance degradation by scale profit
- Full Custom Design
- Semi Custom Design
- Standard Cell
 - Same cell height
- Gate Array
 - Same transistor layout
- FPGA (Field Programmable Gate Array)
 - Same logic elements
- Reconfigurable
- IP base



Design Objective : Chip Area Reduction

More chips and more earnings

Chip Area: Large

 

16


6

chip

#chip

#actual chip

Small

 


25

14


dust

Packing Problem

 - Not so difficult if the number of modules is small
- An optimal solution can not be found in practical time in general if the number of modules is large
- In VLSI design, routing should be taken into account





bad

 

good


Design Objective : Delay Minimization

  - Delay characteristics changes
 - Feature size becomes small, then
 - transistor switching speed increases
 - wire resistance increases



Delay Model Evolution

 
- Previous: routing delay = length
- Current: routing delay = length + distance
- Future: more accurate model is necessary



Growth of Layout Importance

■ Signal Delay Estimation


 
- Previous: gate level consideration is enough
 - signal delay is proportional to #gate
routing hardly affect signal delay
- Future: layout consideration is essential
 - signal delay depends on its path
existence of gate hardly affect signal delay



same delay?



Increase in Delay Uncertainty

  - Delay variation increases
 - System should work correctly under the predefined range of conditions
 - Robustness against delay uncertainty becomes important



Routing

  
- Connect pins under the design rule
 - Many nets (many connection requests)
 - 100% completion ratio
 - 100% without manual correction
 - Near 100% + manual correction
 - Various design rules
 - # of layers
 - Obstacles
 - Various properties of instances
 - Pin distribution
 - Various objectives
 - Total length, delay, power, shape



Hierarchical Design

- Global routing



 
- Design rule insensitive
- Routing area is divided into subareas
- Balance the congestion of subareas
 - Greedy approach
 - Shortest Path (Two terminal)
 - Steiner Tree (Three or more terminal)
 - Rip-up and Reroute



Hierarchical Design



■ Detailed routing

   - Design rule sensitive
- Multiple Nets
 - Channel routing (Two or Three layer)
 - Switch box routing (Two or Three layer)
 - Area routing (Three or more layer)
- Single Nets
 - Wire sizing
 - Buffer Insertion
 - Signal integrity
 - Via planning
 - Clock routing



Objectives

  
- Objectives are changing depending on technological environments
 - 100% routing
 - Area (total length) minimization
 - Delay minimization
 - Skew minimization
 - Power minimization
 - Noise minimization
 - Delay control




Design Objectives in Channel Routing

■ 2-Layer Channel Routing

 - Connect pins on the boundary of routing area using 2-layer
- Minimize the number of tracks (height, width) of channel



HV rule

 


Via Problem

■ Via Minimization


- Minimize #via by assigning wires into proper layer

#via = 10

 

HV rule

#via = 1

 


arbitrary rule

Via Problem (2)


■ Double Via Insertion

- Minimize #single-via to improve the reliability

#single-via = 10

 

#single-via = 2

 

Boolean Function

- Boolean Function $f : B^n \rightarrow B^m$
 - Input variables : x_1, x_2, \dots, x_n (in B)
 - Output variables : f_1, f_2, \dots, f_m (in B)

- Boolean Set B
 - $\{ 0, 1 \}$
 - $\{ \text{False}, \text{True} \}$
 - $\{ \text{GND}, \text{VDD} \}$
 - is represented by the voltage of a node in a circuit
 - 1 : high voltage (say 5[v])
 - 0 : low voltage (say 0[v])

- Boolean variable : takes values in B

Example: Summation

■ Number Notation

– Integer (Unsigned)

dec.	binary	hex	dec.	bin.	Hex
0	0	0	9	1001	9
1	1	1	10	1010	A
2	10	2	11	1011	B
3	11	3	12	1100	C
4	100	4	13	1101	D
5	101	5	14	1110	E
6	110	6	15	1111	F
7	111	7	16	10000	10
8	1000	8	17	10001	11

– Signed Integer

■ 2's-complement

dec.	binary	dec.	binary
0	0000	-8	1000
1	0001	-7	1001
2	0010	-6	1010
3	0011	-5	1011
4	0100	-4	1100
5	0101	-3	1101
6	0110	-2	1110
7	0111	-1	1111

Enable efficient circuit synthesis

Example: Summation

■ $X+Y$

$+$: $B^2 \times B^2 \rightarrow B^3$

$+$: $B^4 \rightarrow B^3$

■ Input

– two 2-bit binaries

■ $X: (x_1, x_0)$

■ $Y: (y_1, y_0)$

■ Output

– one 3-bit binary


■ $X+Y : (f_2, f_1, f_0)$

X	Y	X+Y	X	Y	X+Y
0	0	0	10	0	10
0	1	1	10	1	11
0	10	10	10	10	100
0	11	11	10	11	101
1	0	1	11	0	11
1	1	10	11	1	100
1	10	11	11	10	101
1	11	100	11	11	110

Basic Logic Gates


■ NOT gate (Inverter)

- Output = \neg Input

 


■ AND gate

 - Output = $\text{Input1} \wedge \text{Input2}$
- Looks like production (times)
 - often write as $Y=AB$



■ OR gate

 - Output = $\text{Input1} \vee \text{Input2}$
- Looks like summation (plus)
 - often write as $Y=A+B$




Logic Synthesis

- Get a small logic circuit that realizes a given Boolean function
 - NP-hard problem
 - Exact methods
 - Exponential time algorithm
 - Heuristics
 - Good quality
- Smallest logic circuit is not necessarily optimum
 - Objectives are Size, Delay, Power and etc.

CMOS Implementation

 - Complementary Metal-Oxide-Silicon
- Pull-up and pull-down transistor networks
 - Larger area
 - Low power




- Single-stage CMOS
 - Complex function can be realized
 - May cause area and/or speed overhead
 - AND / OR functions can not be realized

CMOS Property (1)


- When all inputs are 0
 - Pull-up is ON
 - Pull-down is OFF
 - Output is 1
- When all inputs are 1
 - Pull-up is OFF
 - Pull-down is ON
 - Output is 0

Cannot realize AND, OR functions

 

CMOS Property (2)

 - Pull-up and pull-down transistor networks operate complementary
 - When Pull-up is ON, Pull-down is OFF
 - When Pull-up is OFF, Pull-down is ON




Low Power since no direct current from VDD to VSS

nMOS and pMOS Transistors



■ nMOS (npn)

 - ON when gate is high
- OFF when gate is low





■ pMOS (pnp)

  - ON when gate is low
- OFF when gate is high




CMOS NOT Gate Behavior

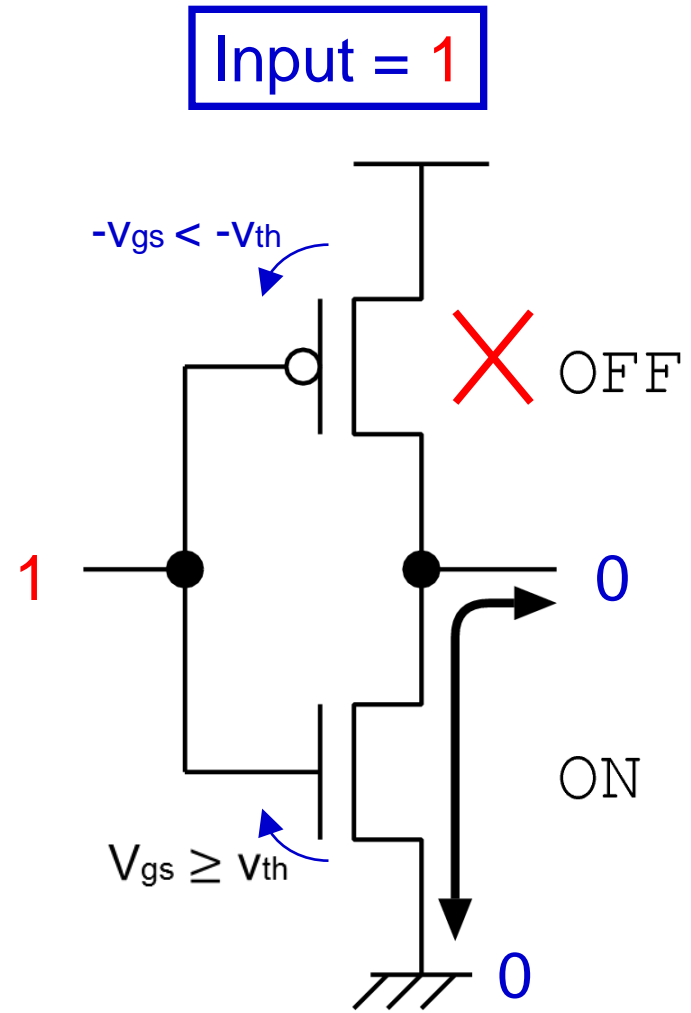 


CMOS NOT Gate Layout

Circuit Diagram

 


Layout Image (top view)

 


CMOS AND Gate ($Y=X_1 \wedge X_2$)

Circuit Diagram

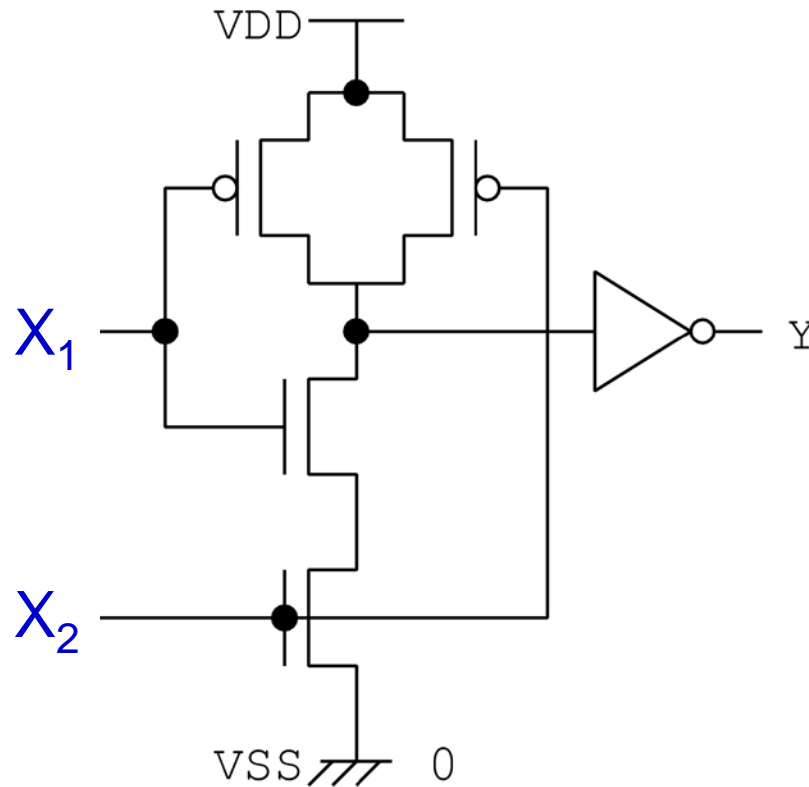

Symbol

 


Truth Table


X_1	X_2	Y
0	0	0
0	1	0
1	0	0
1	1	1

AND Gate Behavior

$$X_1 = X_2 = 0$$


 


$$X_1 = 1, X_2 = 0$$

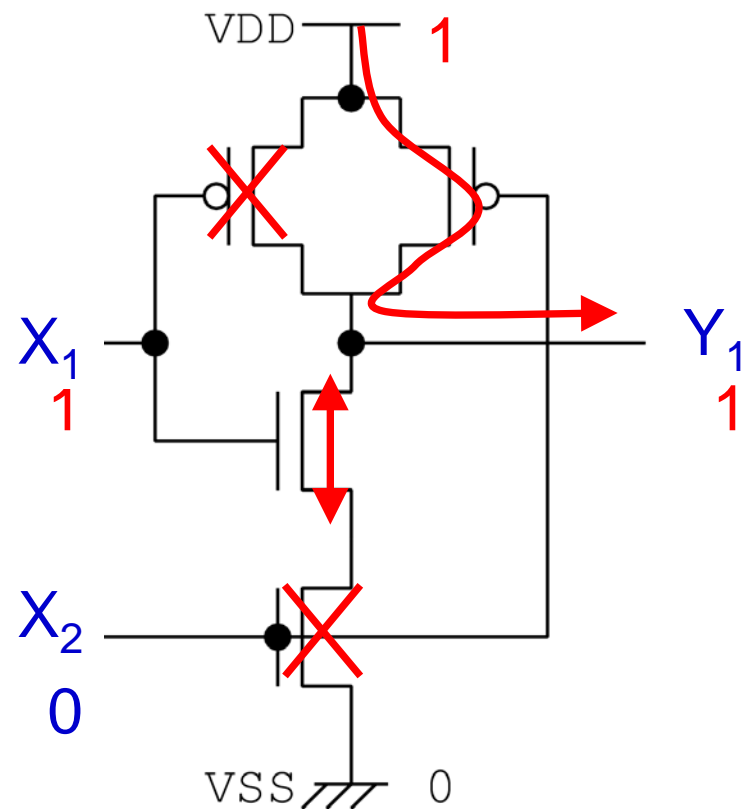

AND Gate Behavior (2)

$$X_1 = X_2 = 1$$

 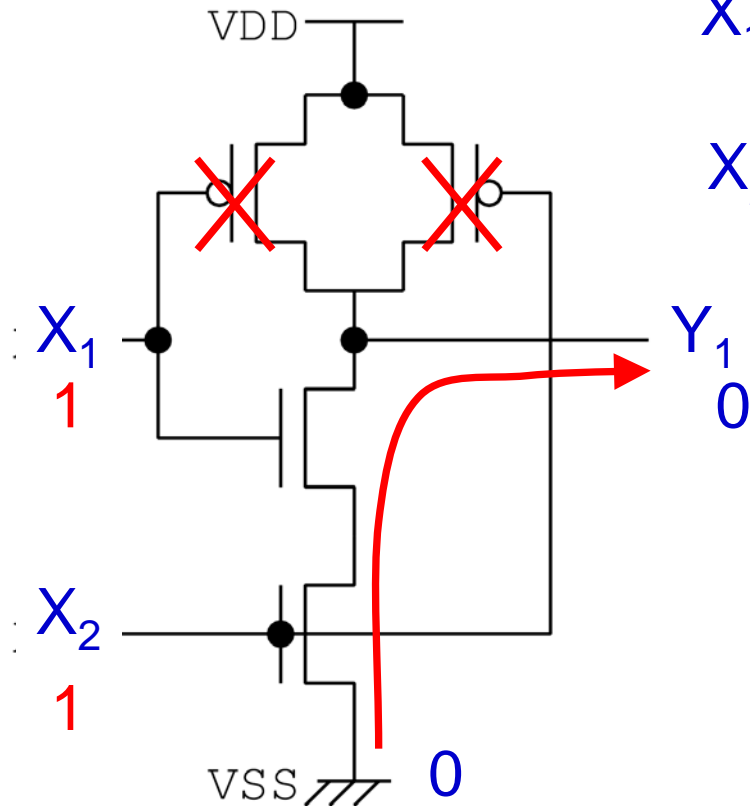


$$Y = \overline{Y_1}$$

Truth Table


X_1	X_2	Y_1	Y
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

CMOS OR Gate ($Y=X_1 \vee X_2$)

Circuit Diagram

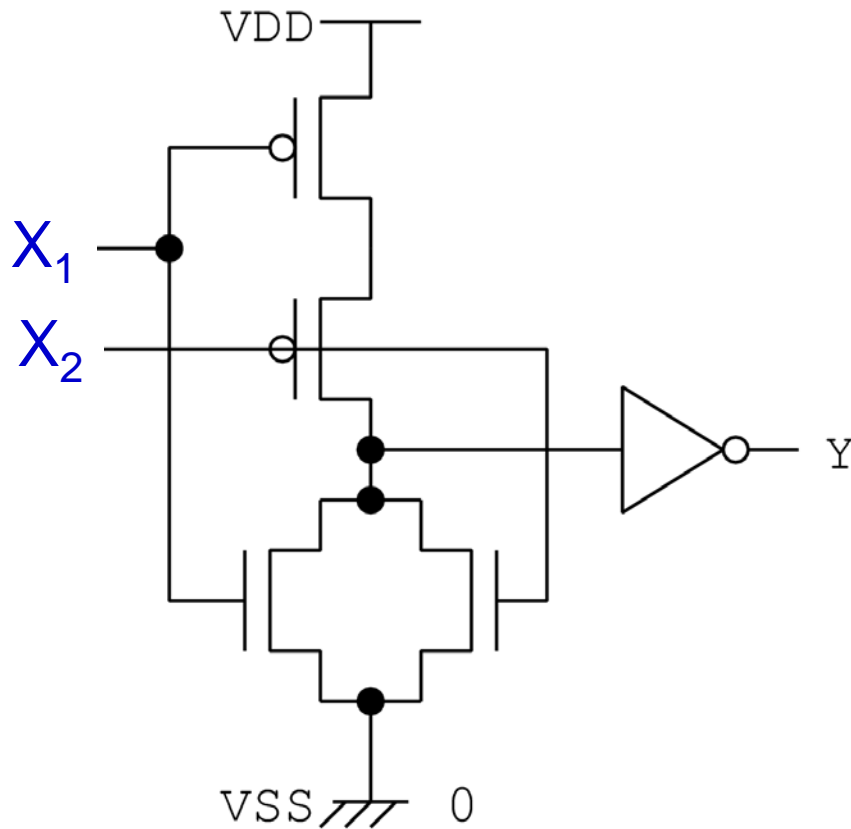

Symbol

 


Truth Table


X_1	X_2	Y
0	0	0
0	1	1
1	0	1
1	1	1

OR Gate Behavior

$$X_1 = X_2 = 0$$

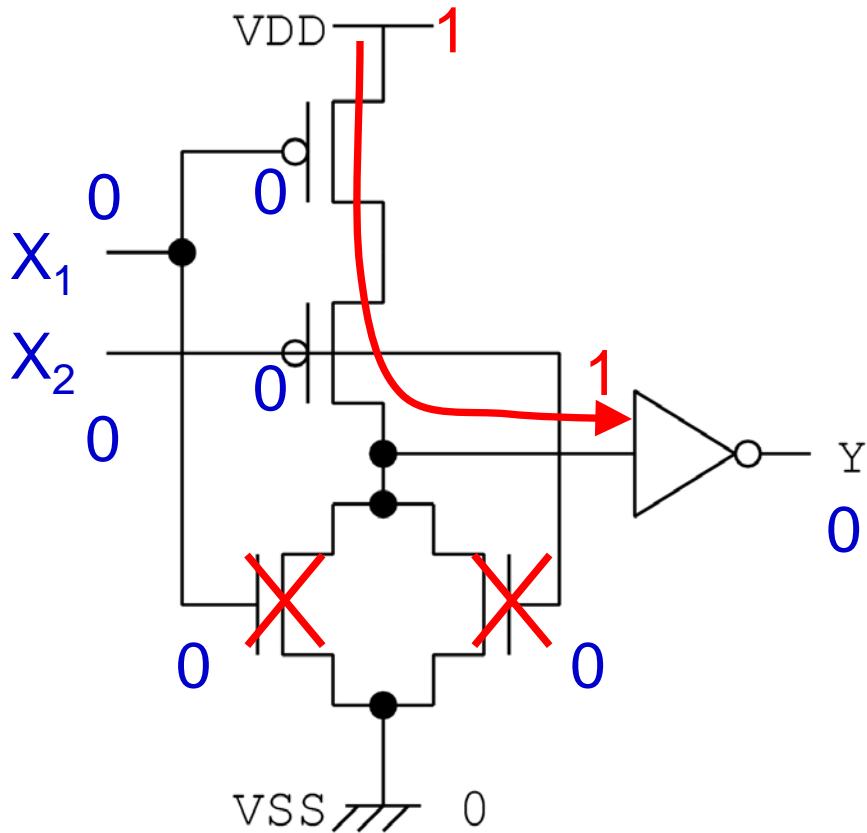


$$X_1 = 0, X_2 = 1$$

 

OR Gate Behavior (2)

$$X_1 = X_2 = 1$$

 



Truth Table

X_1	X_2	Y_1	Y
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

$$Y = \overline{Y_1}$$

CMOS Challenges

  - Lower supply voltage
 - Increase of leak current
 - Dynamic power vs. Static power
- New Devices
 - FinFET
 - gate wraps around the channel or “fin”
 - 3D Integration
 - ✓ Different properties



VLSI and Computer System

- Integration of Various Technologies
- Roadmap
 - Need technologies on an appropriate timing
 - One missing technology ruins whole
 - Technology too early to use might be wasteful

