

# 10. Eigen Vector (Eigen Excitation) and Eigen Value

## 10.1 Eigen vector

The input impedance measured at every port , eg., becomes identical in eigen excitation. This impedance is an eigen value of the impedance matrix of the circuit.

## 10.2 Eigen values and eigen vectors in circuit matrices

When eigen values are obtained for one of circuit matrices, those of remaining matrices are determined. Also, **eigen vectors are identical for all matrices in a given circuit.**

## 10.3 Method for determination of eigen values and eigen vectors

The eigen values and eigen vectors of rotationally symmetric circuit is calculated as an example.

# Eigen vector and eigen value : Definition


Consider the case that the following relation holds. That is, the input impedance measured at every port is identical.


$$\frac{V_1^i}{I_1^i} = \frac{V_2^i}{I_2^i} = \dots = \frac{V_n^i}{I_n^i} = z_i$$

$$[V^i] = z_i [I^i] = [Z][I^i]$$

$$([Z] - z_i [1])[I] = 0$$

$$\det([Z] - z_i [1]) = 0$$

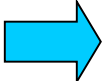n solutions for  $z_i$ .  eigen values

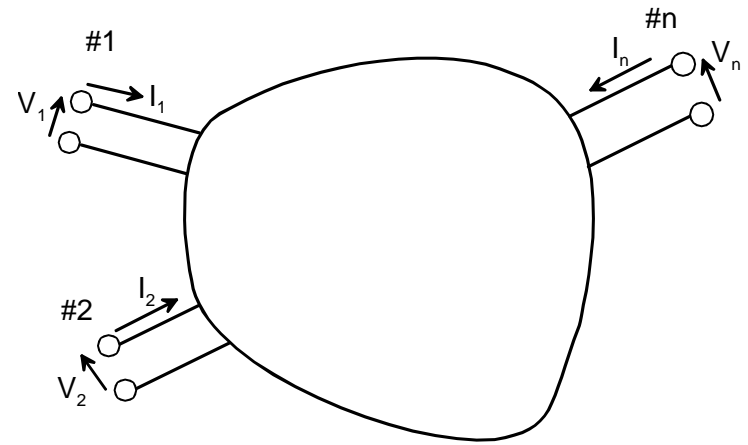

# Eigen vector and eigen value : Example

Symmetric 2 port circuit

$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{12} & Z_{11} \end{bmatrix}$$

$$\det([Z] - z[1]) = 0$$

$$\therefore z_i = Z_{11} \pm Z_{12}$$

$$(a) \quad z_1 = Z_{11} + Z_{12}$$

$$\begin{bmatrix} & \\ & \end{bmatrix} \begin{bmatrix} I_1^1 \\ I_2^1 \end{bmatrix} = 0$$

$$\therefore I_1^1 = I_2^1 \quad (\text{even excitation})$$

$$(b) \quad z_2 = Z_{11} - Z_{12}$$

$$\begin{bmatrix} & \\ & \end{bmatrix} \begin{bmatrix} I_1^2 \\ I_2^2 \end{bmatrix} = 0$$

$$\therefore I_1^2 = -I_2^2 \quad (\text{odd excitation})$$

# Relation between circuit matrices

Rational function of a square matrix  $[M]$

$$f([M]) = c_0([M] - c_1[1])([M] - c_2[1]) \cdots ([M] - c_{-1}[1])^{-1}([M] - c_{-2}[1])^{-1} \cdots$$

$$[M]\mathbf{E}^i = \lambda_i \mathbf{E}^i$$

$\mathbf{E}^i$  : the eigen vector of  $[M]$ .

$$c_k[1]\mathbf{E}^i = c_k \mathbf{E}^i$$

$$([M] - c_k[1])\mathbf{E}^i = (\lambda_i - c_k)\mathbf{E}^i$$

$$\mathbf{E}^i = (\lambda_i - c_k)([M] - c_k[1])^{-1}\mathbf{E}^i \Rightarrow ([M] - c_k[1])^{-1}\mathbf{E}^i = (\lambda_i - c_k)^{-1}\mathbf{E}^i$$

$$\begin{aligned} f([M])\mathbf{E}^i &= c_0([M] - c_1[1])([M] - c_2[1]) \cdots ([M] - c_{-1}[1])^{-1}([M] - c_{-2}[1])^{-1} \cdots \mathbf{E}^i \\ &= c_0([M] - c_1[1])([M] - c_2[1]) \cdots ([M] - c_{-1}[1])^{-1}(\lambda_i - c_{-2})^{-1} \cdots \mathbf{E}^i \\ &= c_0(\lambda_i - c_1)(\lambda_i - c_2) \cdots (\lambda_i - c_{-1})^{-1}(\lambda_i - c_{-2})^{-1} \cdots \mathbf{E}^i \end{aligned}$$

the eigen vector of rational matrix function  $f([M])$  = the eigen vector of matrix  $[M]$ .

the eigen value of rational matrix function  $f([M])$

$$c_0(\lambda_i - c_1)(\lambda_i - c_2) \cdots (\lambda_i - c_{-1})^{-1}(\lambda_i - c_{-2})^{-1} \cdots$$

# Relation between circuit matrices

$$[Z][I^i] = z_i[I^i]$$

$$[Y][V^i] = y_i[V^i]$$

Here, the following relation holds.

$$[Y] = f([Z]) = ([Z] - c_{-1}[1])^{-1} \quad c_{-1} = 0$$

eigen vectors of impedance matrix = eigen vectors of admittance matrix  
eigen values of admittance matrix is given by the following simple eq. :

$$y_i = (z_i - c_{-1})^{-1} = z_i^{-1}$$

Scattering matrix and impedance matrix

$$[S] = \left(\frac{1}{R_0}[Z] + 1\right)^{-1} \left(\frac{1}{R_0}[Z] - 1\right) = ([Z] + R_0)^{-1}([Z] - R_0)$$

$$S_i = (z_i + R_0)^{-1}(z_i - R_0) = \frac{z_i - R_0}{z_i + R_0}$$

# How to find eigen vectors and eigen values ?

$$[P]\mathbf{u}^i = p_i\mathbf{u}^i$$

$$[Q][P]\mathbf{u}^i = p_i[Q]\mathbf{u}^i$$

Commutative matrices  $[P]$  and  $[Q]$ :  $[P][Q] = [Q][P]$

$$[Q][P]\mathbf{u}^i = [P][Q]\mathbf{u}^i = [P]([Q]\mathbf{u}^i) = p_i([Q]\mathbf{u}^i)$$

$[Q]\mathbf{u}^i$  is the eigen vector of  $[P]$ , and has the eigen value  $p_i$ .  
Therefore,  $[Q]\mathbf{u}^i$  is to be proportional to  $\mathbf{u}^i$ .

$$\therefore [Q]\mathbf{u}^i = q_i\mathbf{u}^i$$

$\mathbf{u}^i$  is also the eigen vector of matrix  $[Q]$ .

Eigen vectors  $\mathbf{u}^i$  are obtainable from either  $[P]$  or  $[Q]$ ,  
if  $[P]$  and  $[Q]$  are commutative.

# How to find eigen vectors and eigen values ?

rotationally symmetric 3 port circuit

$$[R] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

$$[R][Z]\mathbf{i} = [R]\mathbf{v} = \mathbf{v}' = [Z]\mathbf{i}' = [Z][R]\mathbf{i}$$

$$\therefore [R][Z] = [Z][R]$$


$[R]$  and  $[Z]$  are commutative.

The eigen vectors of  $[Z]$  become identical to that of  $[R]$ .

$$[R]\mathbf{u}^i = r^i \mathbf{u}^i$$

$$\det([R] - r[1]) = 0$$
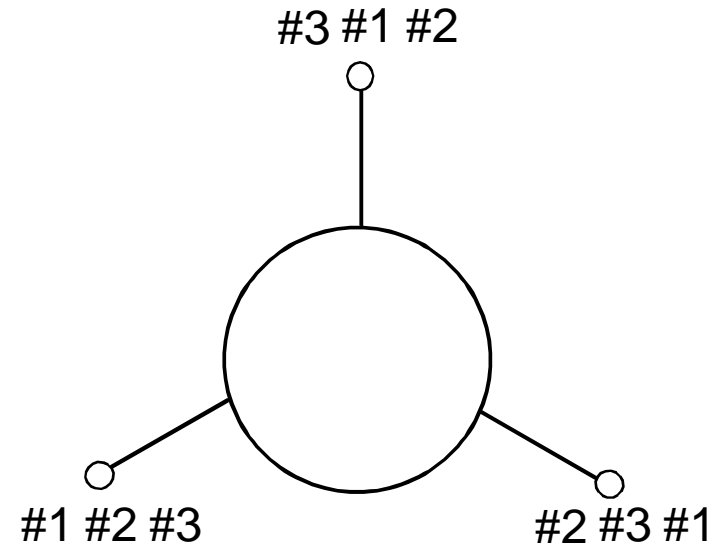
$$\det \begin{pmatrix} -r & 0 & 1 \\ 1 & -r & 0 \\ 0 & 1 & -r \end{pmatrix} = 0, \quad r^3 - 1 = 0 \quad \therefore r = 1, e^{j\frac{2\pi}{3}}, e^{-j\frac{2\pi}{3}}$$



# How to find eigen vectors and eigen values ?

(i)  $r = 1$

$$\begin{pmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix} \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} = \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} \quad \Rightarrow \quad \mathbf{u}^1 = \begin{pmatrix} \phantom{0} \\ \phantom{0} \\ \phantom{0} \end{pmatrix}$$

(ii)  $r = e^{j\frac{2\pi}{3}}$

$$\begin{pmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix} \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} = \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} \quad \Rightarrow \quad \mathbf{u}^2 = \begin{pmatrix} \phantom{0} \\ \phantom{0} \\ \phantom{0} \end{pmatrix}$$

(iii)  $r = e^{-j\frac{2\pi}{3}}$

$$\begin{pmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix} \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} = \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} \quad \Rightarrow \quad \mathbf{u}^3 = \begin{pmatrix} \phantom{0} \\ \phantom{0} \\ \phantom{0} \end{pmatrix}$$