

VLSI System Design

Part III : Technology Mapping (1)


Lecturer : Tsuyoshi Isshiki

Dept. Communications and Computer Engineering,

Tokyo Institute of Technology

issiki@vlsi.ce.titech.ac.jp


Logic Synthesis Flow

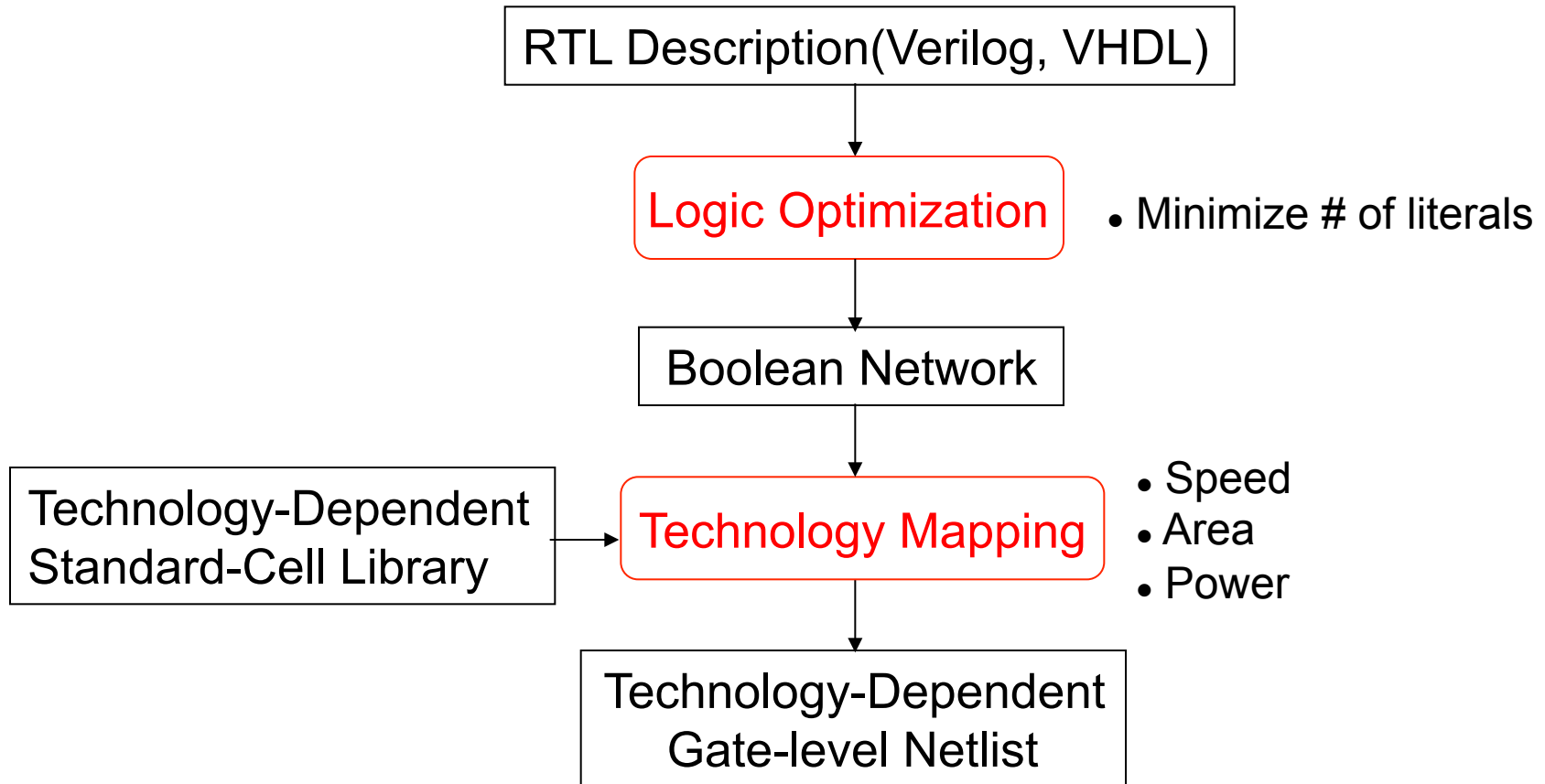



Technology Mapping and Circuit Cell Library

1. *Technology Mapping* transforms the Boolean Network into netlist composed of predefined circuit cells (mask layout for the cells provided).
2. Circuit cell types
 - a. Functionality
 - Primitive cells : INV, AND, OR, NAND, NOR
 - Compound cells : XOR, AND-OR, MUX, TBUF
 - Storage cells : LATCH, FF
 - Options : Positive/negative clock, asynchronous/synchronous set & reset, clock enable
 - b. Drive Power



INV Cell (Schematic / Layout)

 


Power :x1

  


Power :x2

  


Power :x4

 


INV Cell (Schematic / Layout)

 

Power :x1

 

Power :x2

 

Power :x4

Size : 3.0 x 16.5 μm

Load :

A : 0.025pF

Internal delay :

A=>Y(rise) : 0.042 ns

A=>Y(fall) : 0.039 ns

Output transition delay :

Y(rise) : 1.534 ns/pF

Y(fall) : 0.715 ns/pF

Size : 7.5 x 16.5 μm

Load :

A : 0.050pF

Internal delay :

A=>Y(rise) : 0.035 ns

A=>Y(fall) : 0.033 ns

Output transition delay :

Y(rise) : 0.754 ns/pF

Y(fall) : 0.355 ns/pF

Size : 13.5 x 16.5 μm

Load :

A : 0.100pF

Internal delay :

A=>Y(rise) : 0.035 ns


A=>Y(fall) : 0.034 ns

Output transition delay :



Y(rise) : 0.374 ns/pF

Y(fall) : 0.176 ns/pF



NAND2 Cell (Schematic / Layout)

 


Power :x1

  


Power :x2

  


Power :x4

 


NAND2 Cell (Schematic / Layout)

 

Power :×1

 

Power :×2

 

Power :×4

Size : 4.5 x 16.5 um

Load :

A : 0.025pF

B : 0.024pF

Internal delay :

A=>Y(rise) : 0.055 ns

A=>Y(fall) : 0.051 ns

B=>Y(rise) : 0.073 ns

B=>Y(fall) : 0.060 ns

Output transition delay :

Y(rise) : 1.532 ns/pF

Y(fall) : 1.153 ns/pF

Size : 7.5 x 16.5 um

Load :

A : 0.050pF

B : 0.050pF

Internal delay :

A=>Y(rise) : 0.048 ns

A=>Y(fall) : 0.050 ns

B=>Y(rise) : 0.068 ns

B=>Y(fall) : 0.058 ns

Output transition delay :

Y(rise) : 0.755 ns/pF

Y(fall) : 0.577 ns/pF

Size : 13.5 x 16.5 um

Load :

A : 0.017pF

B : 0.017pF

Internal delay :

A=>Y(rise) : 0.299 ns

A=>Y(fall) : 0.325 ns

B=>Y(rise) : 0.327 ns

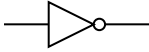
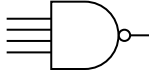
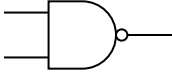

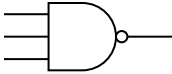
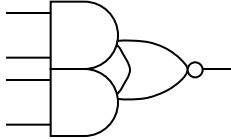
B=>Y(fall) : 0.340 ns

Output transition delay :

Y(rise) : 0.373 ns/pF

Y(fall) : 0.205 ns/pF

Cell Library Example

Cell name	cost	symbol	Cell name	cost	symbol
INV	2		NAND4	5	
NAND2	3		AOI21	4	
NAND3	4		AOI22	5	


Area Optimal Technology Mapping Flow

1. Transform the optimized Boolean Network into NAND network
2. Decompose NAND network into trees
 - Fan-out : # of destination pins for output pin of a node
 - Tree : DAG (directed acyclic graph) where all nodes have a fan-out of 1
 - Fast algorithms exist for solving the Optimal Tree Covering Problem
3. Transform each NAND-tree into NAND2-tree
 - Balanced NAND2 decomposition
4. For each NAND2-tree, obtain the optimal tree covering in terms of circuit area by *dynamic programming*

Transformation of Boolean Network to NAND Network


- At each node of Boolean Network, convert the sum-of-product form into NAND-NAND form
 
$$\begin{aligned} F &= abc + de + fg \\ &= \overline{\overline{abc}} + \overline{\overline{de}} + \overline{\overline{fg}} \\ &= \overline{(\overline{abc})(\overline{de})(\overline{fg})} \end{aligned}$$




DAG-to-Tree Decomposition

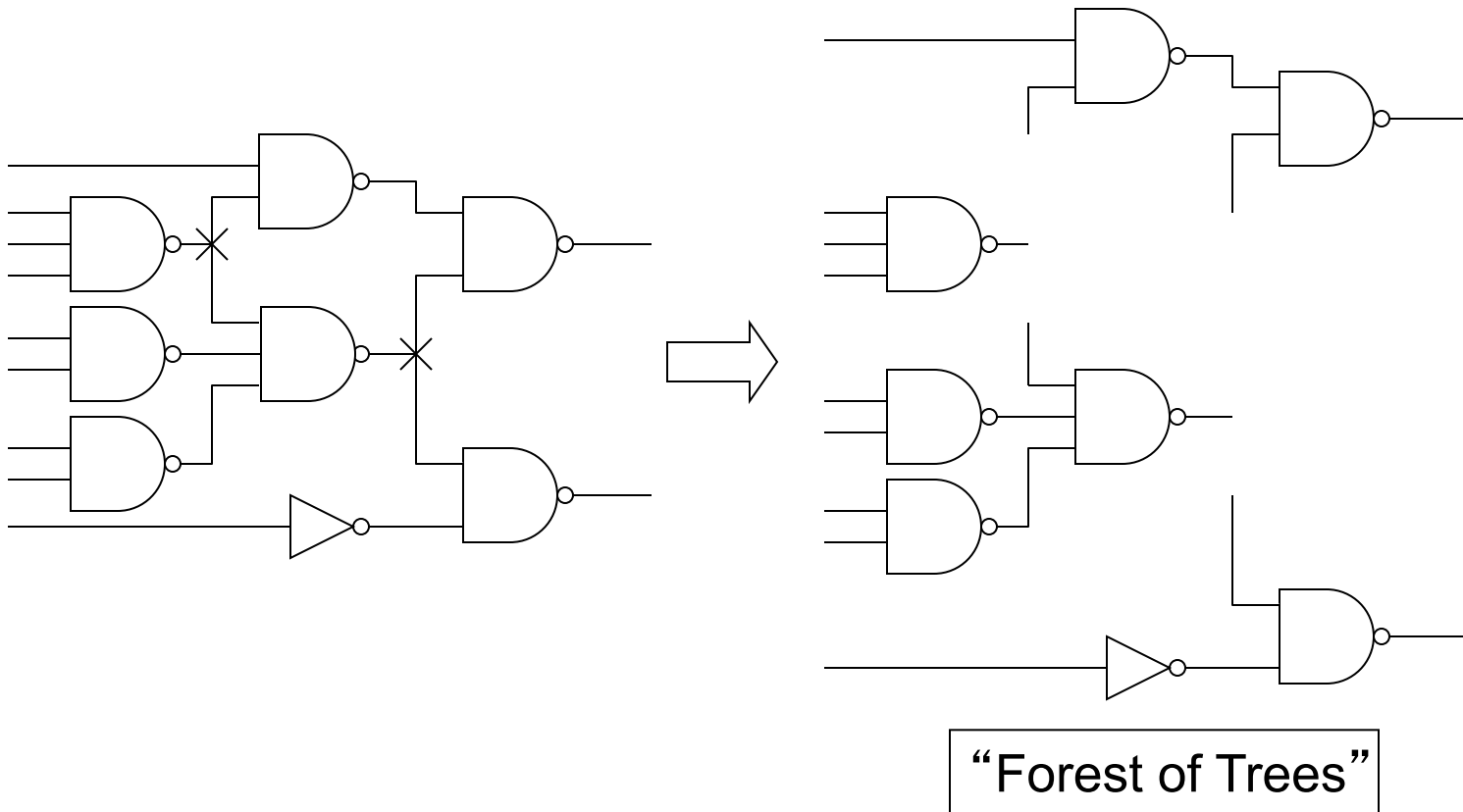- If the gate output has a fan-out of more than 1, disconnect all pins from the arc (net).




NAND2 Decomposition (NAND2-Tree)

 - For each NAND gate on the NAND-tree, decompose into NAND2 gates
- If there are multiple decomposition solutions, choose the tree with the smallest height (balanced tree decomposition)
















Cell Patterns

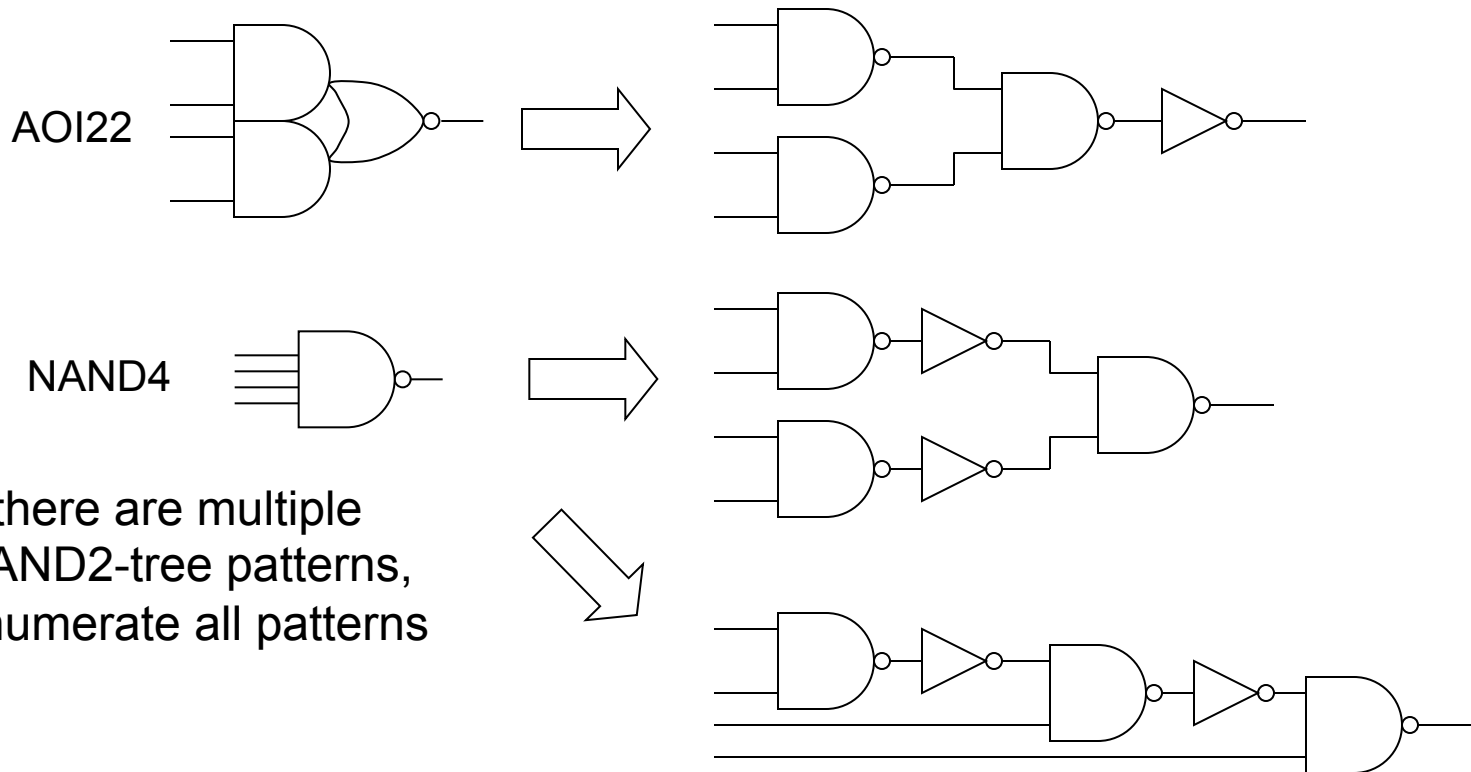- For each cell in the library, enumerate all functionally equivalent NAND2-trees and register them as *cell patterns*.




Cell Library Example

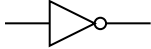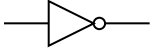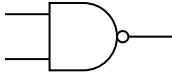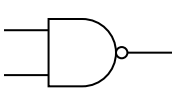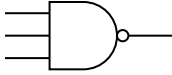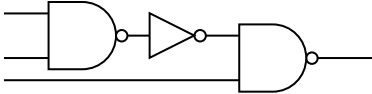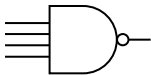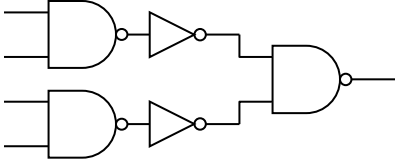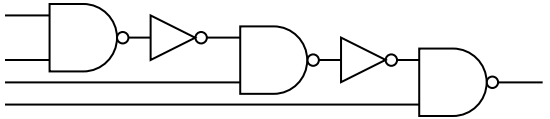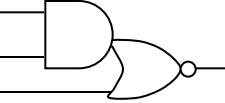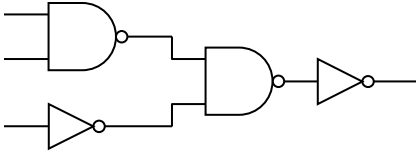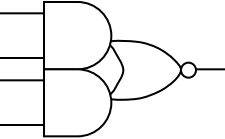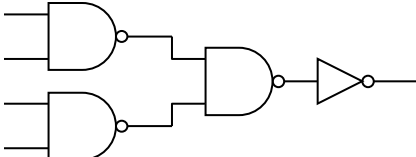Cell name	cost	symbol	Primitive DAG (NAND2+INV representation)	
INV	2			
NAND2	3			
NAND3	4			
NAND4	5			
AOI21	4			
AOI22	5			



Technology Mapping as Tree Covering Problem (1)

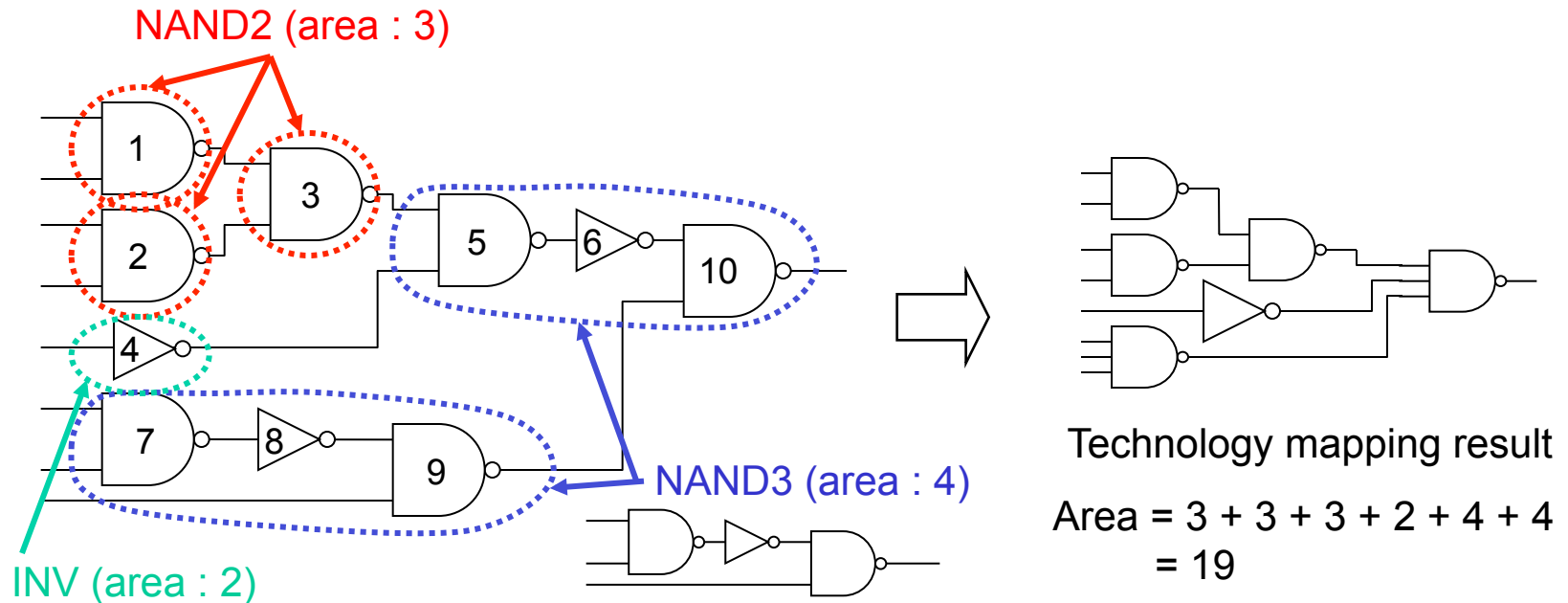- Cover the NAND2-tree with registered cell patterns with the minimum cost (circuit area, speed, etc.)
- Each node must be covered by exactly one pattern



Technology Mapping as Tree Covering Problem (2)

 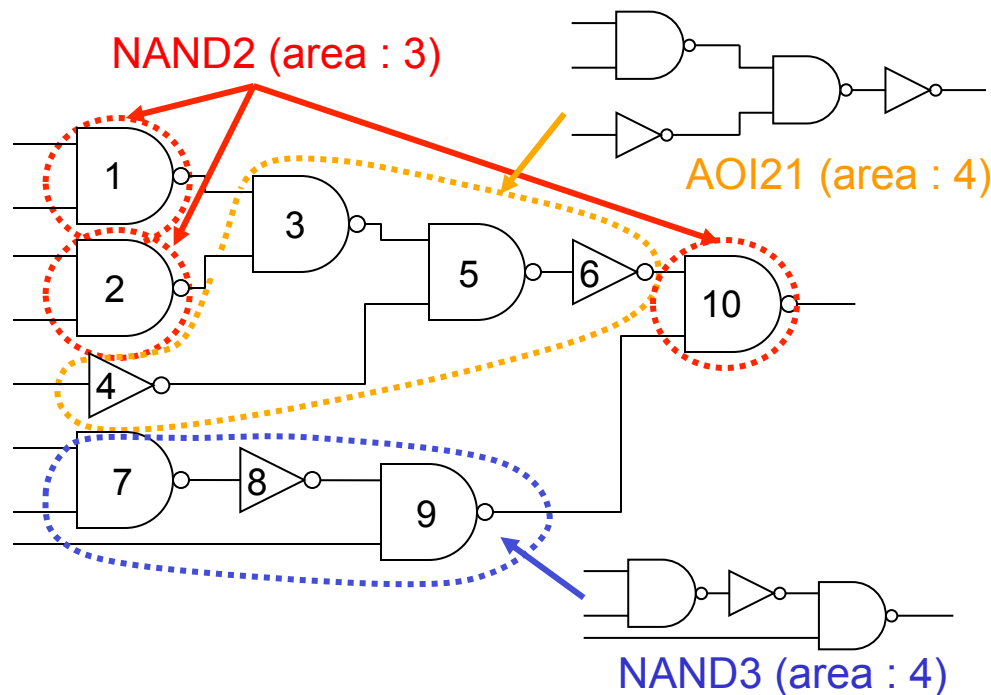- Cover the NAND2-tree with registered cell patterns with the minimum cost (circuit area, speed, etc.)
- Each node must be covered by exactly one pattern




Technology mapping result

$$\begin{aligned} \text{Area} &= 3 + 3 + 4 + 4 + 3 \\ &= 17 \end{aligned}$$

Tree Covering Approach (1)

- Definition of *tree* graph :
 - Each node consist of several *child* nodes and a *parent* node.
 - A *root* is a node with no parent node. (only one root in a tree)
 - A *leaf* is a node with no child nodes.
- Divide the covering problem on tree T into smaller covering problems on the *subtrees* of T .
 - Recursively solve the covering problem on the subtrees rooted at each node of T and store the optimal covering cost at each node.
 - Start from the leaf nodes and continue towards the root
 - *Here, assume that the covering cost is circuit area*

 


Target NAND2-tree

Tree Covering Example (1)

- $C(p_j)$: cost of cell pattern p_j
 - $C_{opt}(i)$: optimal covering cost of the subtree rooted at node i
 - $C_{map}(i, p_j)$: optimal covering cost of the subtree rooted at node i when p_j is used to cover i
- $C_{opt}(i) = \text{MIN}\{C_{map}(i, p_j)\}$


$C(\text{NAND2}) = 3$

 

$$C_{map}(1, \text{NAND2}) = C(\text{NAND2}) = 3$$

$$C_{opt}(1) = C_{map}(1, \text{NAND2}) = 3$$


$C(\text{NAND2}) = 3$

 

$$C_{map}(2, \text{NAND2}) = C(\text{NAND2}) = 3$$

$$C_{opt}(2) = C_{map}(2, \text{NAND2}) = 3$$

$C_{opt}(1) = 3$

 


$C(\text{NAND2}) = 3$

$$C_{map}(3, \text{NAND2}) = C_{opt}(1) + C_{opt}(2) + C(\text{NAND2}) = 9$$


$$C_{opt}(3) = C_{map}(3, \text{NAND2}) = 9$$

$C_{opt}(2) = 3$

 


Tree Covering Example (2)

$$C(\text{INV}) = 2$$

 




$$C_{\text{map}}(4, \text{INV}) = C(\text{INV}) = 2$$
 
$$C_{\text{opt}}(4) = C_{\text{map}}(4, \text{INV}) = 2$$



$$C_{\text{map}}(5, \text{NAND2}) = C_{\text{opt}}(3) + C_{\text{opt}}(4) + C(\text{NAND2}) = 14$$
   
$$C_{\text{opt}}(5) = C_{\text{map}}(5, \text{NAND2}) = 14$$




$$C_{\text{map}}(6, \text{INV}) = C_{\text{opt}}(5) + C(\text{INV}) = 16$$

$$C_{\text{map}}(6, \text{AOI21}) = C_{\text{opt}}(1) + C_{\text{opt}}(2) + C(\text{AOI21}) = 10$$

$$C_{\text{opt}}(6) = C_{\text{map}}(6, \text{AOI21}) = 10$$


Tree Covering Example (3)

$C(\text{NAND2}) = 3$

 


$$C_{\text{map}}(7, \text{NAND2}) = C(\text{NAND2}) = 3$$
 
$$C_{\text{opt}}(7) = C_{\text{map}}(7, \text{NAND2}) = 3$$



$C(\text{INV}) = 2$

 


$C_{\text{opt}}(7) = 3$

$$C_{\text{map}}(7, \text{INV}) = C_{\text{opt}}(7) + C(\text{INV}) = 5$$


$$C_{\text{opt}}(8) = C_{\text{map}}(8, \text{INV}) = 5$$

$C_{\text{opt}}(8) = 5$

 

$C(\text{NAND2}) = 3$

$C(\text{NAND3}) = 4$


 


$$C_{\text{map}}(9, \text{NAND2}) = C_{\text{opt}}(8) + C(\text{NAND2}) = 8$$

$$C_{\text{map}}(9, \text{NAND3}) = C(\text{NAND3}) = 4$$

$$C_{\text{opt}}(9) = C_{\text{map}}(9, \text{NAND3}) = 4$$

Tree Covering Example (4)

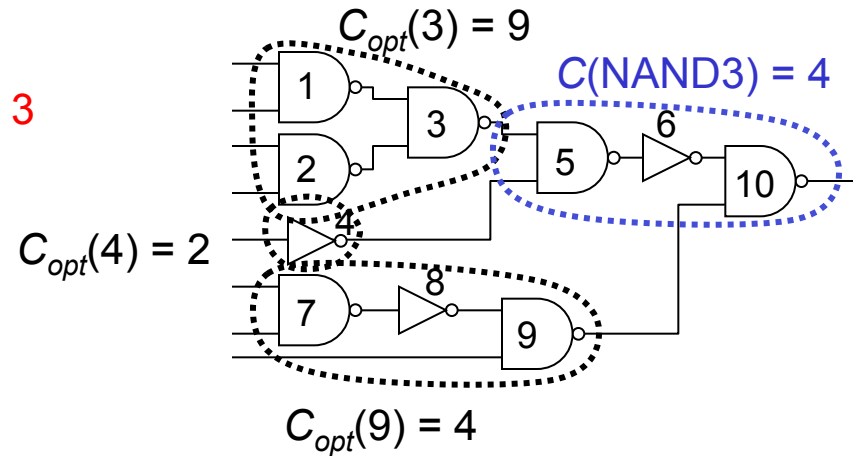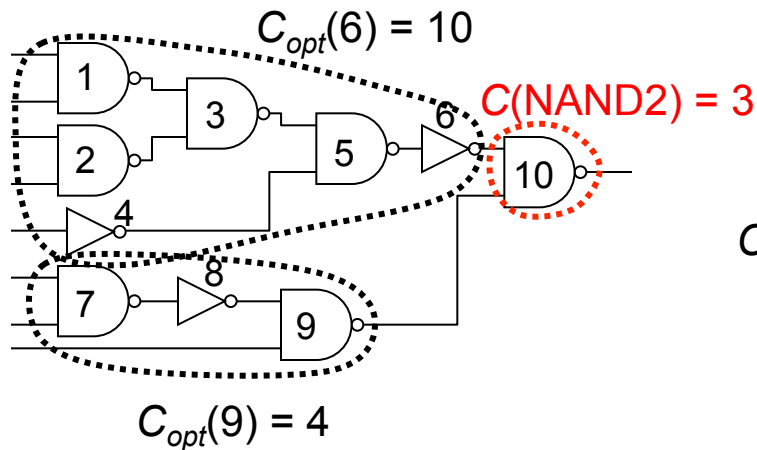


$$C_{map}(10, NAND2) = C_{opt}(6) + C_{opt}(9) + C(NAND2) = 17$$

$$C_{map}(10, NAND3) = C_{opt}(3) + C_{opt}(4) + C_{opt}(9) + C(NAND3) = 19$$



$$C_{opt}(10) = C_{map}(10, NAND2) = 17$$

Optimal tree cover \rightarrow

 

Principle of Optimality for Area-Optimal Tree Covering

  - Area-optimal covering cost using pattern p_i can be derived from the optimal covering costs of the subtrees whose roots are connected to the leaves of p_i .
- Area-optimal covering on the subtrees rooted at each node needs to be calculated only once and stored.
 → *Dynamic Programming* : Deriving the solution to a problem from a set of solutions on its subproblems.




$$C_{map}(R, p_1) = C_{opt}(A) + C_{opt}(B) + C(p_1) \quad C_{map}(R, p_2) = C_{opt}(A) + C_{opt}(G) + C_{opt}(H) + C(p_2)$$


$$C_{opt}(R) = MIN\{C_{map}(R, p_1) + C_{map}(R, p_2)\}$$


Problems Arising in DAG Decomposition (1)

 1. Gates such as multiplexer and EXOR cannot be expressed in NAND2-trees
 - Instead of decomposing the network into trees, decompose into *Leaf-DAG*
 - Leaf-DAG: primary inputs are allowed to have multiple fan-outs.
 - Tree-covering algorithm can still be applied to Leaf-DAG




Leaf-DAG Decomposition

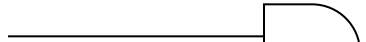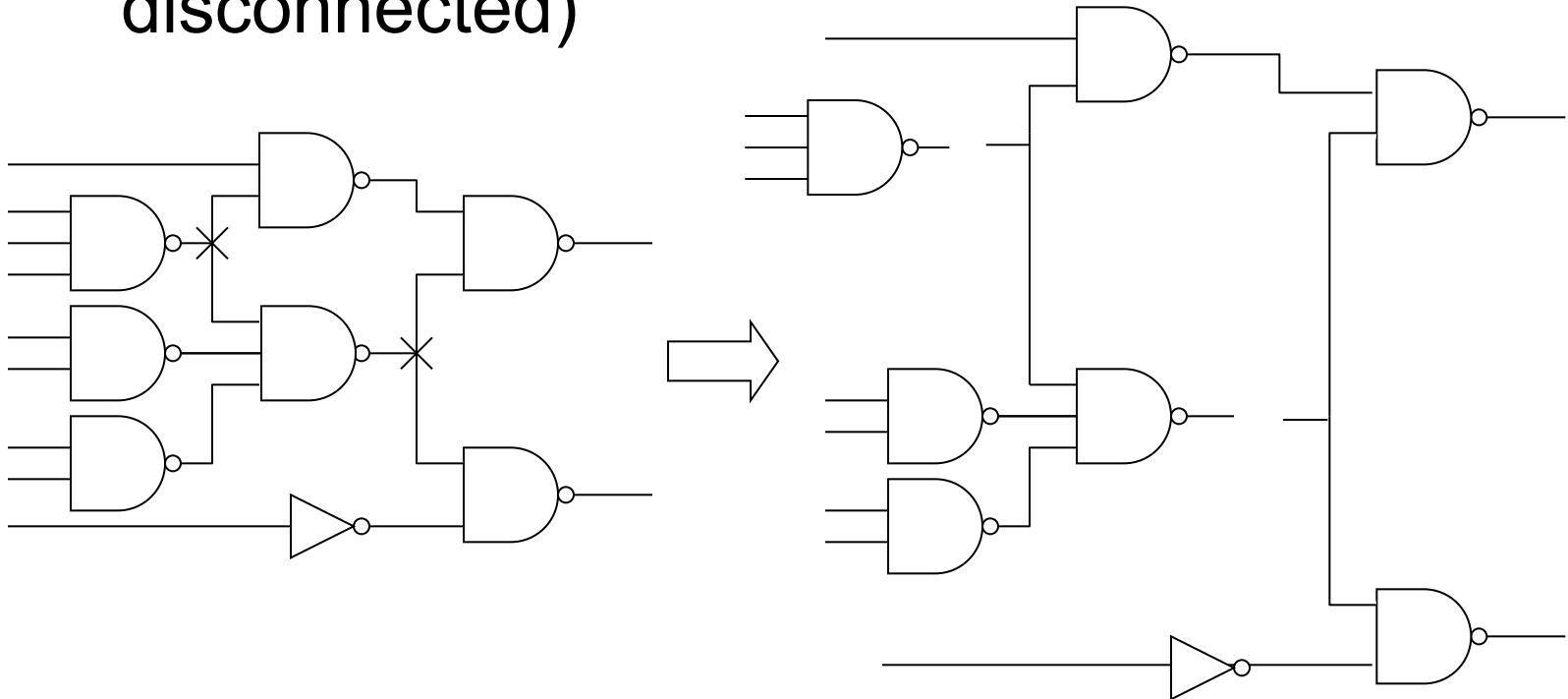- If the gate output has a fan-out of more than 1, disconnect only the output pin from the net. (in tree decomposition, all pins were disconnected)
- 
- The diagram shows a logic gate symbol with a single input line on the left and two output lines on the right. The output lines are connected to two separate nodes, represented by small circles, illustrating a fan-out of 2.



Problems Arising in DAG Decomposition (2)

 2. The solution space for the overall objective of “DAG covering” is restricted by decomposing the target DAG into a tree or a leaf-DAG. Therefore opportunity for deriving the optimal DAG covering can be lost with the decomposition.
3. Single-cone decomposition : At each primary output, exact a “cone” which includes all paths to the primary inputs.



Tree decomposition :
Optimal covering cost = 11

Single-cone decomposition :
Optimal covering cost = 8