

VLSI Interconnects

Instructed by Shmuel Wimer
Eng. School, Bar-Ilan University

Credits: David Harris
Harvey Mudd College


(Some material copied/taken/adapted from
Harris' lecture notes)

Outline


- ☐ Introduction
- ☐ Wire Resistance
- ☐ Wire Capacitance
- ☐ Wire RC Delay
- ☐ Crosstalk
- ☐ Wire Engineering
- ☐ Repeaters
- ☐ Scaling

Introduction

 - ❑ Chips are mostly made of wires called *interconnect*
- ❑ Alternating layers run orthogonally




 - ❑ Transistors are little things under the wires
- ❑ Many layers of wires




❑ Wires are as important as transistors

- Speed
- Power
- Noise

 

Wire Geometry

 - ❑ Pitch = $w + s$
- ❑ Aspect ratio: $AR = t/w$
 - Old processes had $AR \ll 1$
 - Modern processes have $AR \approx 2$
 - Pack in many skinny wires



Layer Stack

❑ Modern processes use 6-10+ metal layers

❑ Example: Intel 180 nm process

❑ M1: thin, narrow ($< 3\lambda$)

– High density cells

❑ M2-M4: thicker

– For longer wires

❑ M5-M6: thickest

– For V_{DD} , GND, clk



Wire Resistance

□ $\rho = \text{resistivity } (\Omega \cdot \text{m})$


$$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$

□ $R_{\square} = \text{sheet resistance } (\Omega/\square)$

– \square is a dimensionless unit(!)

□ Count number of squares

 – $R = R_{\square} * (\# \text{ of squares})$



Choice of Metals

- ❑ Until 180 nm generation, most wires were aluminum
- ❑ Modern processes use copper
 - Cu atoms diffuse into silicon and damage FETs
 - Must be surrounded by a diffusion barrier

| Metal | Bulk resistivity ($\mu\Omega\cdot\text{cm}$) |
|-----------------|--|
| Silver (Ag) | 1.6 |
| Copper (Cu) | 1.7 |
| Gold (Au) | 2.2 |
| Aluminum (Al) | 2.8 |
| Tungsten (W) | 5.3 |
| Molybdenum (Mo) | 5.3 |

Sheet Resistance

- Typical sheet resistances in 180 nm process

| Layer | Sheet Resistance (Ω/\square) |
|---------------------------|---------------------------------------|
| Diffusion (silicided) | 3-10 |
| Diffusion (no silicide) | 50-200 |
| Polysilicon (silicided) | 3-10 |
| Polysilicon (no silicide) | 50-400 |
| Metal1 | 0.08 |
| Metal2 | 0.05 |
| Metal3 | 0.05 |
| Metal4 | 0.03 |
| Metal5 | 0.02 |
| Metal6 | 0.02 |


Contacts Resistance

- ❑ Contacts and vias also have 2-20 Ω
- ❑ Use many contacts for lower R
 - Many small contacts for current crowding around periphery



Wire Capacitance

 - ❑ Wire has capacitance per unit length
 - To neighbors
 - To layers above and below
- ❑ $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$




Capacitance Trends

- ❑ Parallel plate equation: $C = \epsilon A/d$
 - Wires are not parallel plates, but obey trends
 - Increasing area (W , t) increases capacitance
 - Increasing distance (s , h) decreases capacitance
- ❑ Dielectric constant
 - $\epsilon = k\epsilon_0$
- ❑ $\epsilon_0 = 8.85 \times 10^{-14}$ F/cm
- ❑ $k = 3.9$ for SiO_2
- ❑ Processes are starting to use low- k dielectrics
 - $k \approx 3$ (or less) as dielectrics use air pockets

M2 Capacitance Data

- Typical wires have $\sim 0.2 \text{ fF}/\mu\text{m}$
 - Compare to $2 \text{ fF}/\mu\text{m}$ for gate capacitance

 - Capacitance increases with metal planes above and below
- Capacitance decreases with spacing




Diffusion & Polysilicon



- ❑ Diffusion capacitance is very high (about 2 fF/ μm)
 - Comparable to gate capacitance
 - Diffusion also has high resistance
 - Avoid using diffusion (and polysilicon) *runners* for wires!
- ❑ Polysilicon has lower C but high R
 - Use for transistor gates
 - Occasionally for very short wires between gates

Lumped Element Models

 - ❑ Wires are a distributed system
 - Approximate with lumped element models



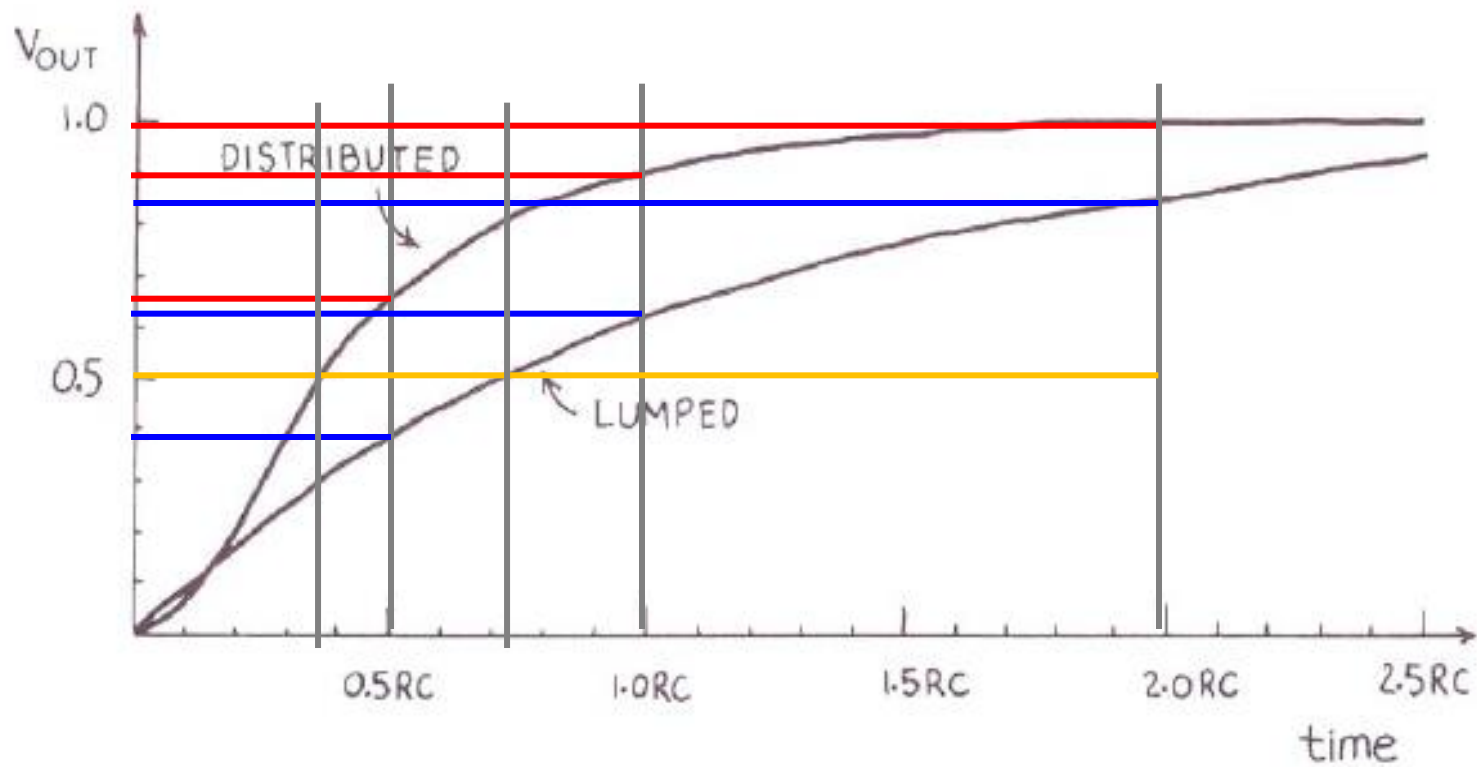 
- ❑ 3-segment π -model is accurate to 3% in simulation




| Output potential range | Time elapsed (Distributed RC Network) | Time elapsed (Lumped RC Network) |
|------------------------|---|--|
| 0 to 90% | 1.0 RC | 2.3 RC |
| 10% to 90% (rise time) | 0.9 RC | 2.2 RC |
| 0 to 63% | 0.5 RC | 1.0 RC |
| 0 to 50% (delay) | 0.4 RC | 0.7 RC |
| 0 to 10% | 0.1 RC | 0.1 RC |

RC Example

 - ❑ Metal2 wire in 180 nm process
 - 5 mm long
 - 0.32 μm wide
- ❑ Construct a 3-segment π -model
 - $R_{\square} = 0.05 \Omega/\square$ $\Rightarrow R = 781 \Omega$
 - $C_{\text{permicron}} = 0.2 \text{ fF}/\mu\text{m}$ $\Rightarrow C = 1 \text{ pF}$



 

$$\begin{array}{c}
 \text{distributed} \qquad \qquad \qquad \text{lumped} \\
 \hline
 T_{90\%} = 1.0R_{int}C_{int} + 2.3(R_{tr}C_{int} + R_{tr}C_L + R_{int}C_L) \\
 \approx (2.3R_{tr} + R_{int})C_{int} \qquad \text{for } C_L \ll C_{int}.
 \end{array}$$

$$\begin{array}{c}
 \text{distributed} \qquad \qquad \qquad \text{lumped} \\
 \hline
 T_{50\%} = 0.4R_{int}C_{int} + 0.7(R_{tr}C_{int} + R_{tr}C_L + R_{int}C_L) \\
 \approx (0.7R_{tr} + 0.4R_{int})C_{int} \qquad \text{for } C_L \ll C_{int}.
 \end{array}$$


Wire RC Delay Example

- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 5mm wire from the previous example

- $R = 2.5 \text{ k}\Omega \cdot \mu\text{m}$ for gates

- Unit inverter: $0.36 \mu\text{m}$ nMOS, $0.72 \mu\text{m}$ pMOS
 
$$10 \times 0.36 \mu\text{m} = 3.6 \mu\text{m}$$




Crosstalk

- ❑ A capacitor does not like to change its voltage instantaneously
- ❑ A wire has high capacitance to its neighbor.
 - When the neighbor switches from $1 \rightarrow 0$ or $0 \rightarrow 1$, the wire tends to switch too.
 - Called capacitive *coupling* or *crosstalk*
- ❑ Crosstalk effects
 - Noise on non switching wires
 - Increased delay on switching wires

Miller Effect

- ❑ Assume layers above and below on average are quiet
 - Second terminal of capacitor can be ignored
 - Model as $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- ❑ Effective C_{adj} depends on behavior of neighbors
 - *Miller effect*


| B | ΔV | $C_{\text{eff(A)}}$ | MCF |
|----------------------|------------------|------------------------------------|-----|
| Constant | V_{DD} | $C_{\text{gnd}} + C_{\text{adj}}$ | 1 |
| Switching with A | 0 | C_{gnd} | 0 |
| Switching opposite A | $2V_{\text{DD}}$ | $C_{\text{gnd}} + 2C_{\text{adj}}$ | 2 |

 

Crosstalk Noise

- ❑ Crosstalk causes noise on non switching wires
- ❑ If victim is floating:
 - model as capacitive voltage divider
 
$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \Delta V_{\text{aggressor}}$$




Driven Victims

- ❑ Usually victim is driven by a gate that fights noise
 - Noise depends on relative resistances
 - Victim driver is in linear region, agg. in saturation
 - If sizes are same, $R_{\text{aggressor}} = 2-4 \times R_{\text{victim}}$


$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \frac{1}{1+k} \Delta V_{\text{aggressor}}$$
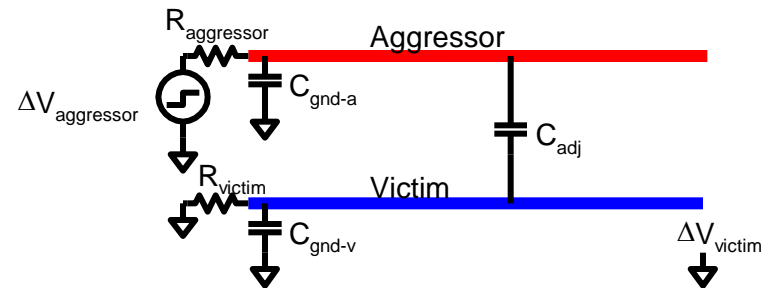
$$k = \frac{\tau_{\text{aggressor}}}{\tau_{\text{victim}}} = \frac{R_{\text{aggressor}} (C_{\text{gnd-a}} + C_{\text{adj}})}{R_{\text{victim}} (C_{\text{gnd-v}} + C_{\text{adj}})}$$



Coupling Waveforms

 - Simulated coupling for $C_{\text{adj}} = C_{\text{victim}}$






Noise Implications


- ❑ *So what if we have noise?*
- ❑ If the noise is less than the noise margin, nothing happens
- ❑ Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes
 - But glitches cause extra delay
 - Also cause extra power from false transitions
- ❑ Dynamic logic never recovers from glitches
- ❑ Memories and other sensitive circuits also can produce the wrong answer

Wire Engineering

WireSpacing
(nm)

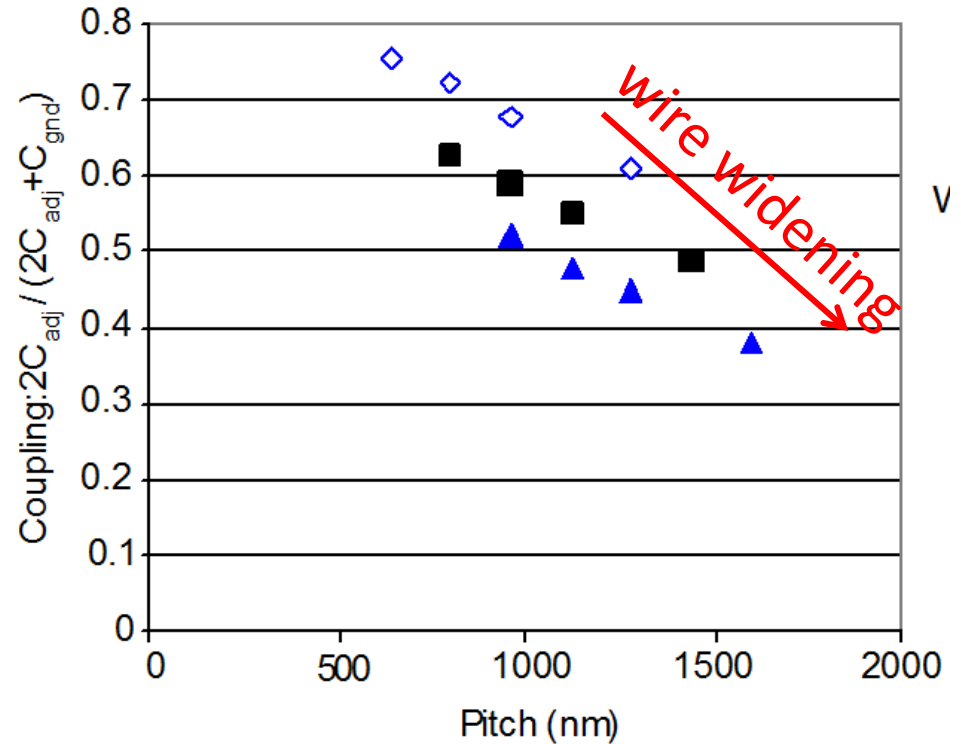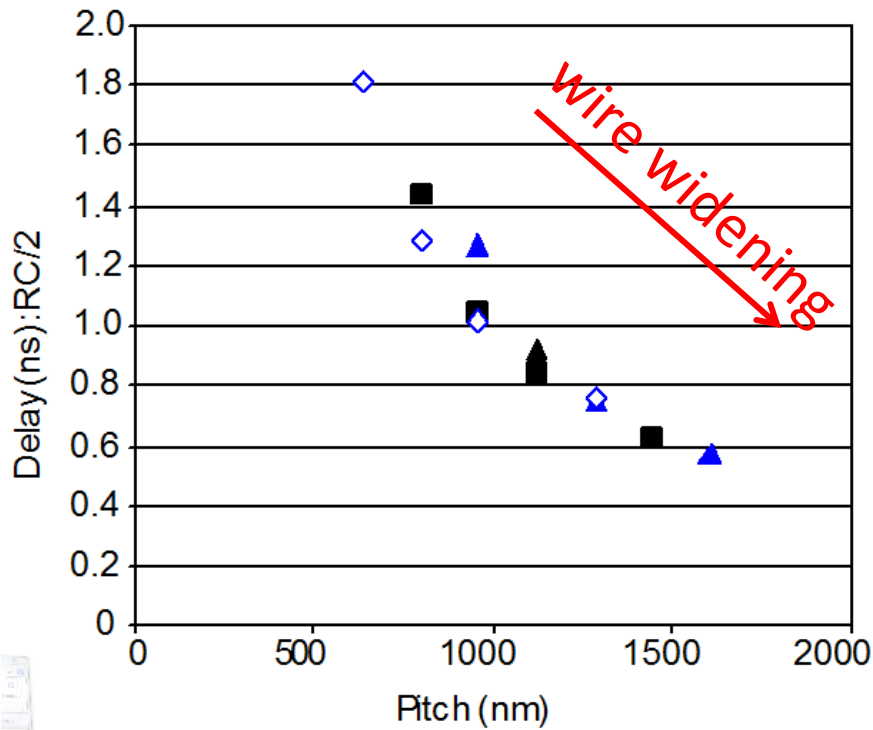 


 - ❑ Goal: achieve delay, area, power with acceptable noise
- ❑ Degrees of freedom:
 - Width
 - Spacing
 - Layer
 - Shielding




Repeaters

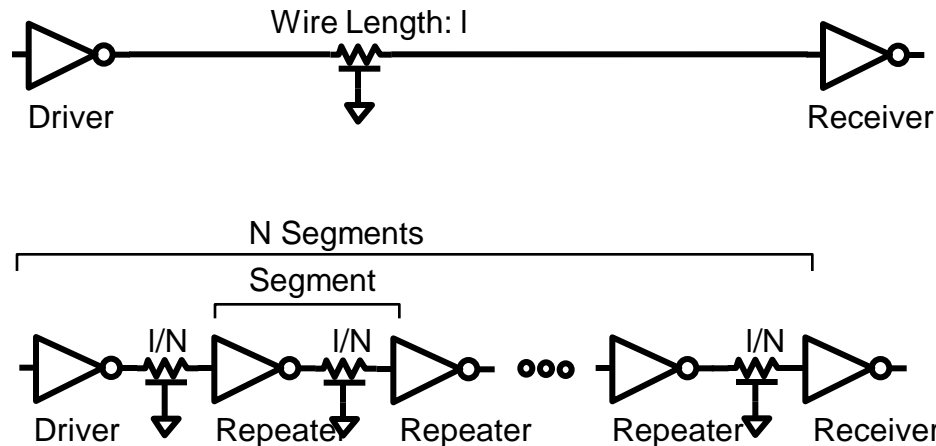- ❑ R and C are proportional to l
- ❑ RC delay is proportional to l^2
 - Unacceptably large for long wires
- ❑ Break long wires into N shorter segments
 - Drive each one with an inverter or buffer




Repeater Design

 - ❑ How many repeaters should we use?
- ❑ How large should each one be?
- ❑ Equivalent Circuit
 - Wire length /
 - Wire Capacitance $C_w * l$, Resistance $R_w * l$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W



(a) minimum-size repeaters,

 

single chain

$$T_{50\%} = k \left[0.7R_o \left(\frac{C_{int}}{k} + C_o \right) + \frac{R_{int}}{k} \left(0.4 \frac{C_{int}}{k} + 0.7C_o \right) \right]$$

$$dT/dk = 0,$$

$$0.4 \frac{R_{int}C_{int}}{k^2} = 0.7R_oC_o,$$


$$k = \sqrt{\frac{0.4R_{int}C_{int}}{0.7R_oC_o}}.$$

$$k = \sqrt{\frac{0.4 R_{int} C_{int}}{0.7 R_o C_o}}$$

Under what condition repeater insertion should take place?

$$\sqrt{\frac{0.4 C_{int} R_{int}}{0.7 C_o R_o}} \geq 2 \quad \frac{C_{int} R_{int}}{C_o R_o} \geq 7$$

(b) optimal repeaters,

 


$$T_{50\%} = k \left[0.7 \frac{R_o}{h} \left(\frac{C_{int}}{k} + hC_o \right) + \frac{R_{int}}{k} \left(0.4 \frac{C_{int}}{k} + 0.7hC_o \right) \right]$$


setting dT/dk and dT/dh to zero,

$$k = \sqrt{\frac{0.4 R_{int} C_{int}}{0.7 R_o C_o}} \quad h = \sqrt{\frac{R_o C_{int}}{R_{int} C_o}}$$

 
$$T_{50\%} = 2.5 \sqrt{R_o C_o R_{int} C_{int}}$$



(c) cascaded drivers,

 

 The method is useful when R_{tr} is dominant and C_{int} is large




$$T_{50\%} = 0.7(n-1)fR_oC_o + \left(\frac{0.7R_o}{f^{n-1}} + 0.4R_{int} \right) C_{int} + \left(\frac{0.7R_o}{f^{n-1}} + 0.7R_{int} \right) C_L$$


setting dT/dn and dT/df to zero,

$$f = e \qquad n = \ln \left(\frac{C_{int} + C_L}{C_o} \right)$$

 (d) optimal repeaters with a cascaded first stage



Optimal Buffer Insertion

 


$d(v, u_i)$: driver to receiver delay.

Root required time: $T = \min_i \{q_i - d(v, u_i)\}$.

Optimal Buffer Insertion

Buffer reduces load delay
but adds internal delay,
power and area.

 

Problem 1:


$$\max_{\text{buffer insertions}} \left\{ \min_i \{q_i - d(v, u_i)\} \right\} \text{ by buffer insertions.}$$

Problem 2:

$$\max_{\text{buffer insertions}} \left\{ \min_i \{q_i - d(v, u_i)\} \right\}, \text{ s.t. power and area constraints.}$$

Delay Model
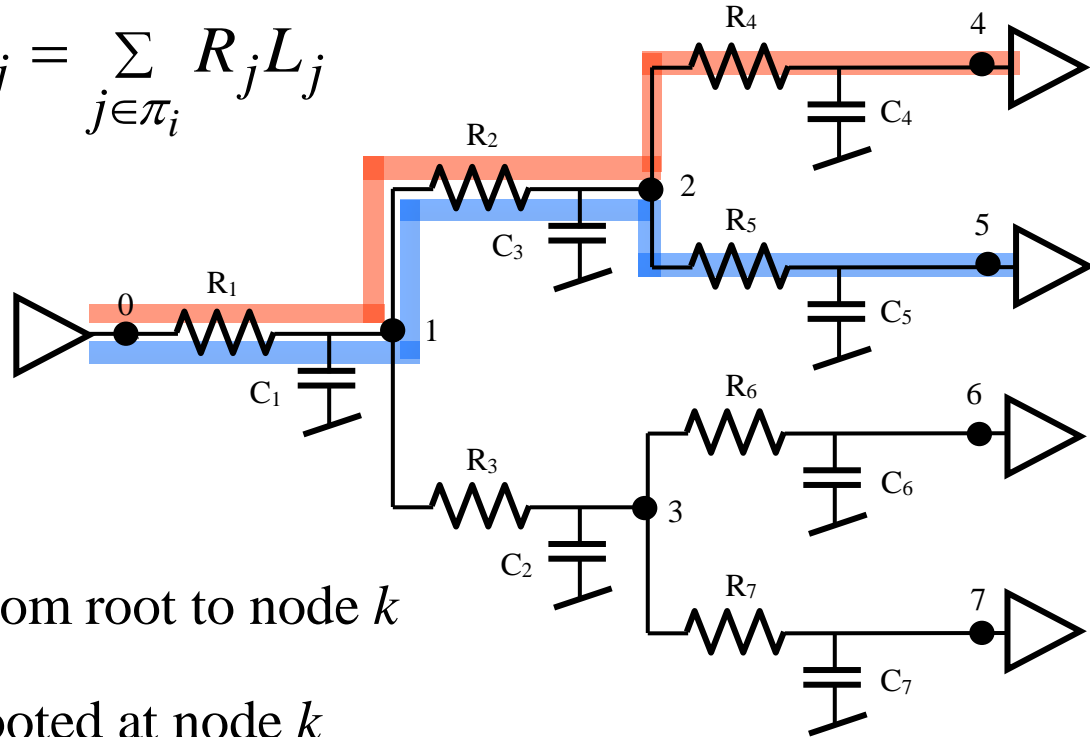
$$d(v, u_i) = \sum_j R_{ji} C_j = \sum_{j \in \pi_i} R_j L_j$$



π_k - nodes along path from root to node k

T_k - nodes of sub-tree rooted at node k

$R_{kl} = \sum_{j \in \pi_k \cap \pi_l} R_j$ - resistance along common paths

$L_k = \sum_{j \in T_k} C_j$ - capacitance of sub-tree

Bottom-Up Solution

$$T'_K = \min \{T_M, T_N\}$$

$$L'_K = L_M + L_N$$

without buffer


$$T_K = T'_K - R_K \left(L'_K + \frac{C_K}{2} \right)$$

$$L_K = L'_K + C_K$$


with buffer

$$T_K = T'_K - D_{\text{buffer}} - R_{\text{buffer}} L'_K - R_K \left(C_{\text{buffer}} + \frac{C_K}{2} \right)$$

$$L_K = C_{\text{buffer}} + C_K$$

 

Scaling Trends

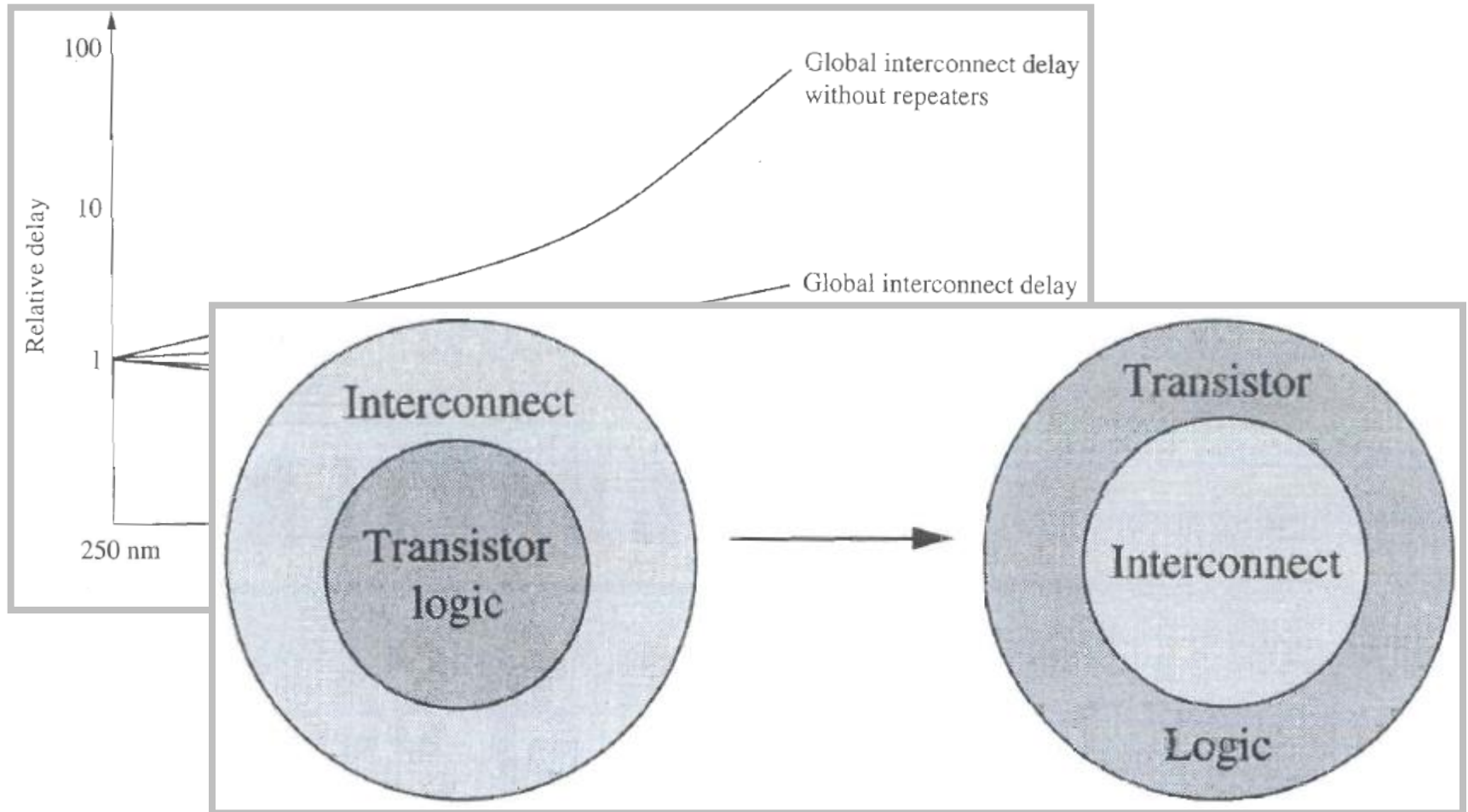

Device Scaling

| Performance parameter | Constant electric field | Constant voltage |
|-----------------------|-------------------------|------------------|
| Threshold voltage | $1/S$ | 1 |
| Current | $1/S$ | S |
| Subthreshold slope | 1 | 1 |
| Capacitance | $1/S$ | $1/S$ |
| On-resistance | 1 | $1/S$ |
| Delay | $1/S$ | $1/S^2$ |
| Power | $1/S^2$ | S |
| Power-delay product | $1/S^3$ | $1/S$ |
| Power density | 1 | S^3 |

Interconnect Scaling

| Interconnect parameters | Ideal scaling | | Quasi-ideal scaling | | Constant resistance | | Constant thickness | |
|--------------------------------|---------------|-------------|---------------------|--------|---------------------|--------|--------------------|--------|
| | Local | Global | Local | Global | Local | Global | Local | Global |
| Length (L_{int}) | $1/S$ | S_c | | | | | | |
| Width (W_{int}) | $1/S$ | $1/S$ | | | | | | |
| Thickness (T_{int}) | $1/S$ | $1/S$ | | | | | | |
| Height (H) | $1/S$ | $1/S$ | | | | | | |
| Spacing (W_{spa}) | $1/S$ | $1/S$ | | | | | | |
| Aspect ratio (AR) | 1 | 1 | | | | | | |
| Resistance | S | $S_c S^2$ | | | | | | |
| Coupling capacitance (C^c) | $1/S$ | S_c | | | | | | |
| Ground capacitance (C^g) | $1/S$ | S_c | | | | | | |
| C^c/C^g | 1 | 1 | | | | | | |
| RC delay | 1 | $S_c^2 S^2$ | | | | | | |