

VLSI System Design

Part I : Introduction

Lecturer : Tsuyoshi Isshiki

Dept. Information and Communications Engineering,

Tokyo Institute of Technology

issiki@ict.e.titech.ac.jp

Lecture Notes, Course Assignments, Grades

- Lecture notes are to be downloaded from OCW/OCWi sites
- Course assignments will be given after each lecture chapter (2-3 lectures per chapter)
- Course grade is based upon the score of each course assignment *only*.
- Each course assignments includes several regular problems and a few “extra credit” problems.
- Regular problems are due **ONE WEEK** after the actual assignment. Late submission will be reflected in the score
- Extra credit problems can be submitted any time before the due date of the final assignment. Scores of extra credit problems will be added to the course grade as bonus points. Students are strongly encouraged to submit at least one extra credit problem.

Course Outline

1. Introduction to VLSI system design

- VLSI design methodology and computer-Aided Design (CAD) tools
- Hardware description language and hardware behavior model

2. Logic synthesis

- Logic minimization
 - Combinational and sequential circuits
 - Two-level logic minimization
 - Multi-level logic minimization
- Technology mapping
 - Implementation technology : PLA, gate-array, standard cell, FPGA
 - Area-optimal mapping
 - Delay-optimal mapping, fan-out optimization


3. High-level synthesis

- High-level design methodology
 - Register-transfer level and behavioral level descriptions
 - Architecture (datapath, register, memory, bus, control logic)
- Operation scheduling
- Resource allocation

4. Advanced topics in system-level design issues


- Description language issues (C-based system description)
- Design verification (simulation, emulation, formal verification)
- Platform-based design (CPU-core, standard bus interface, IPs)

Today' s VLSI : System-on-Chip (SoC)

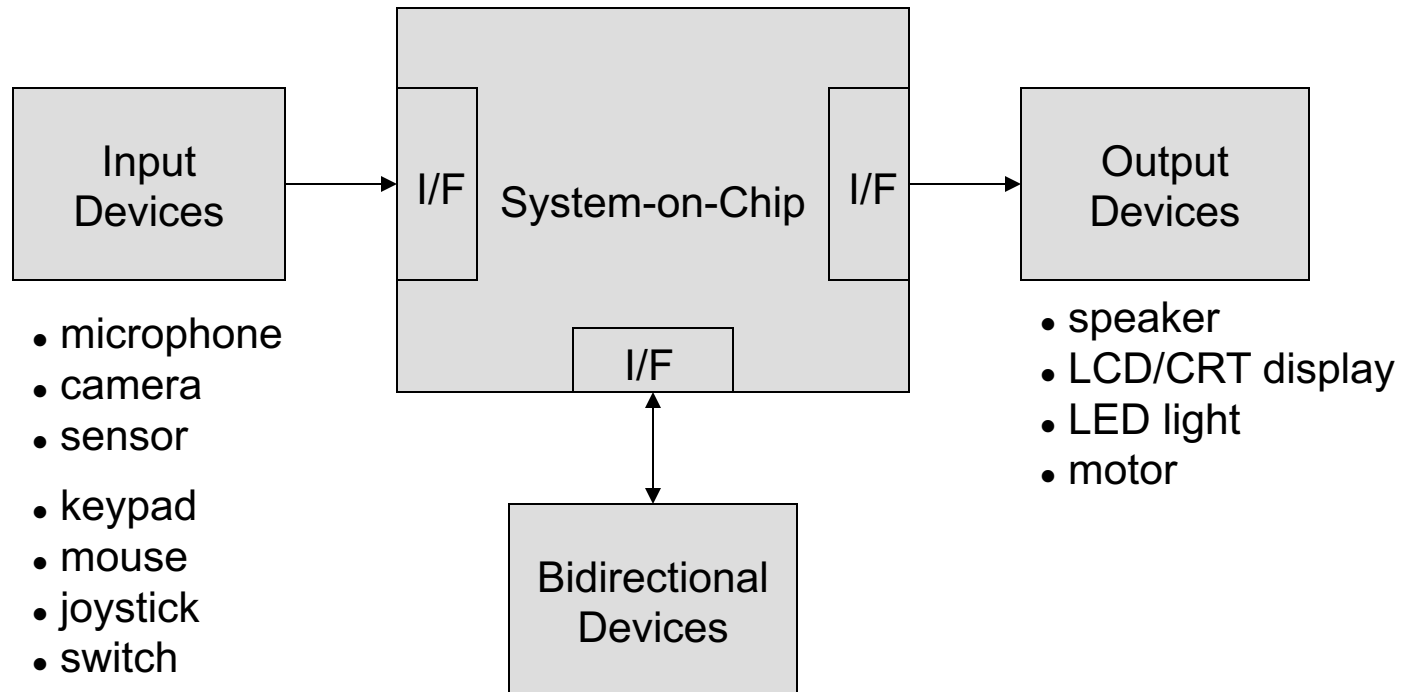


- peripheral bus (IEEE1394, USB, RS232C, PCI, SCSI, AGP, ISA, ATA, ...)
- storage (SRAM, DRAM, FLASH-ROM, disk drive)
- network (Modem, Ethernet, wireless)

SoC – A simplified (logical) view

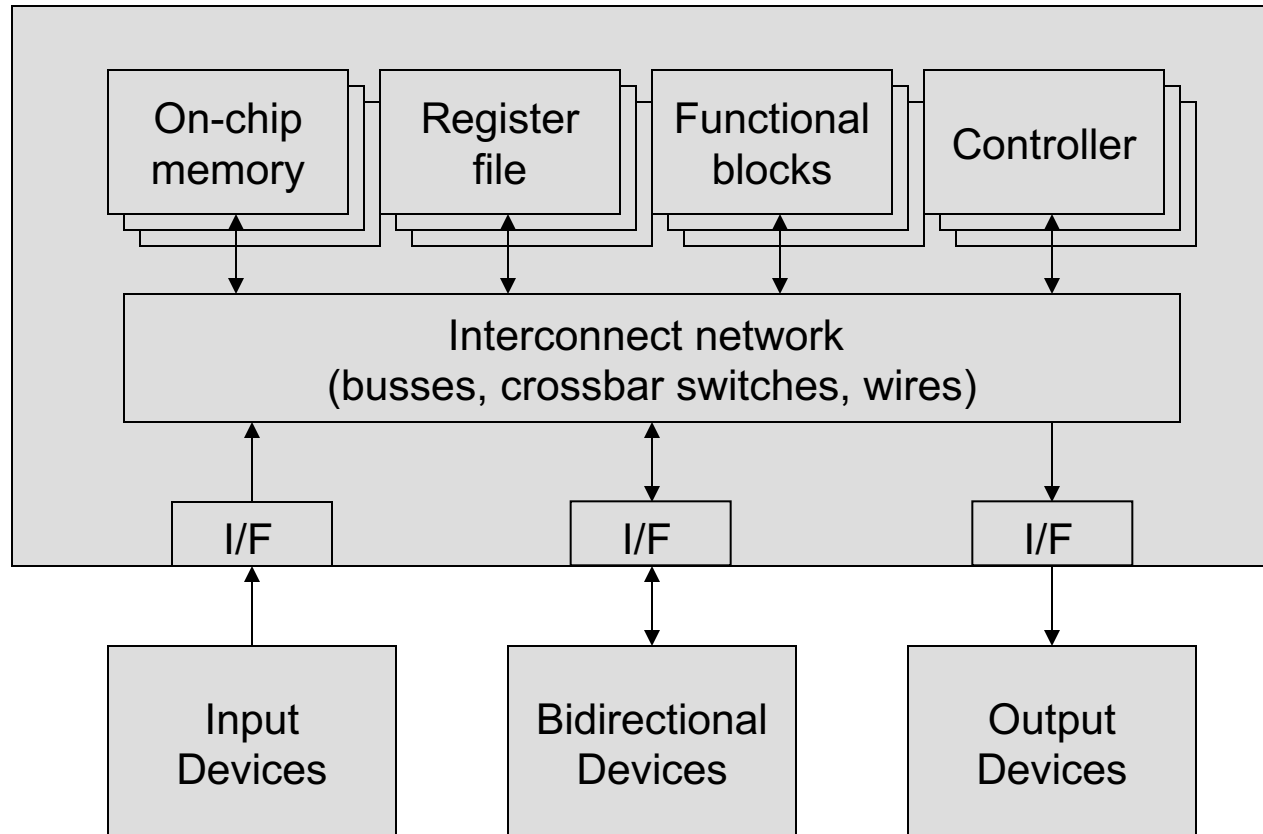

Systematic VLSI Design Flow

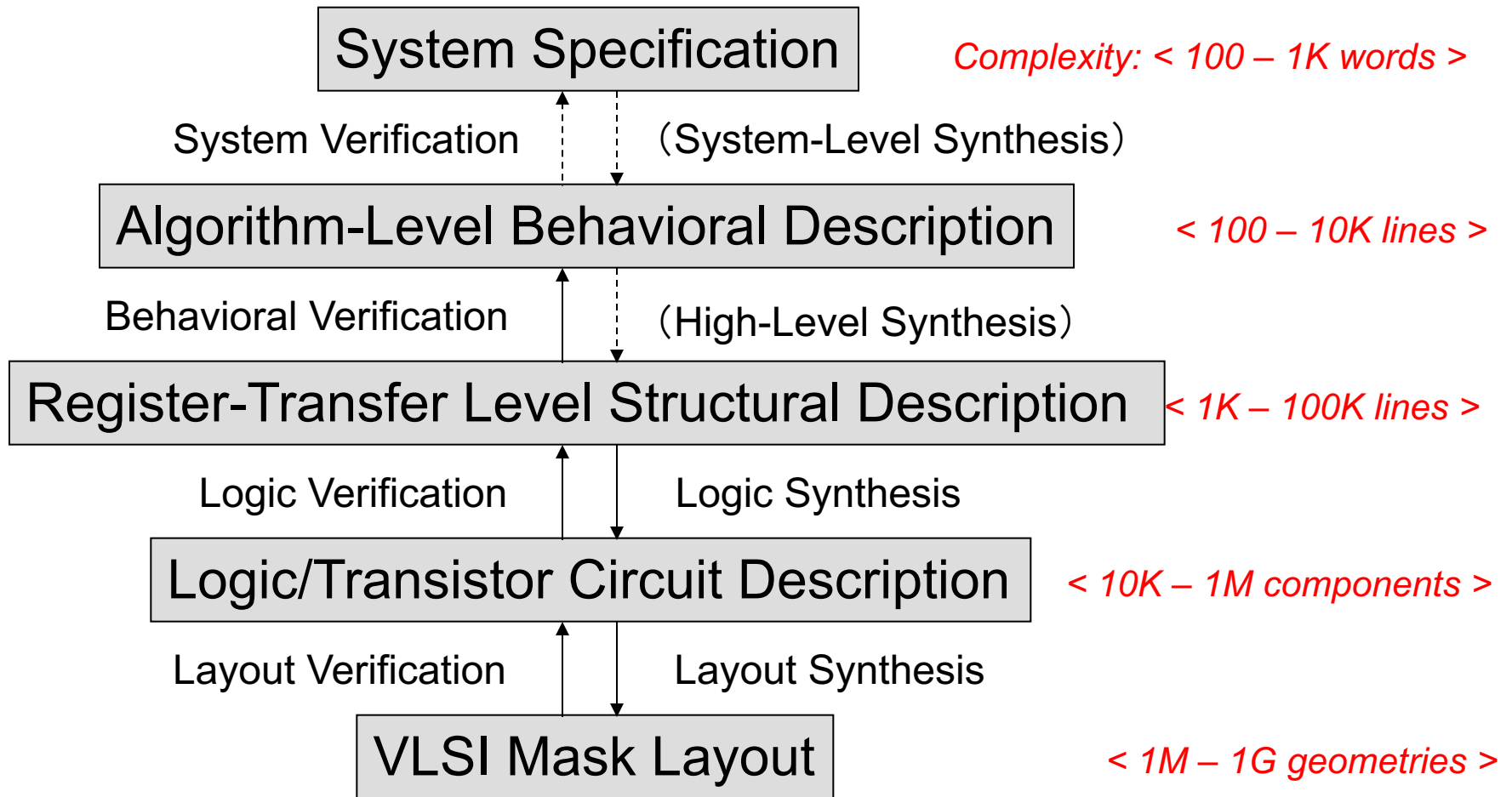


System Specification

System Specification


□ *Human language*
(English, Japanese, etc.)
< 100 – 1K words >

- ✓ System functionality (application)
- ✓ Operating environment (IO interface)
- ✓ Cost (development, manufacture, test)
- ✓ Size/weight (# of chips, board area, box size)
- ✓ Power consumption
- ✓ Flexibility (specification changes, added functionality)


System Synthesis/Verification

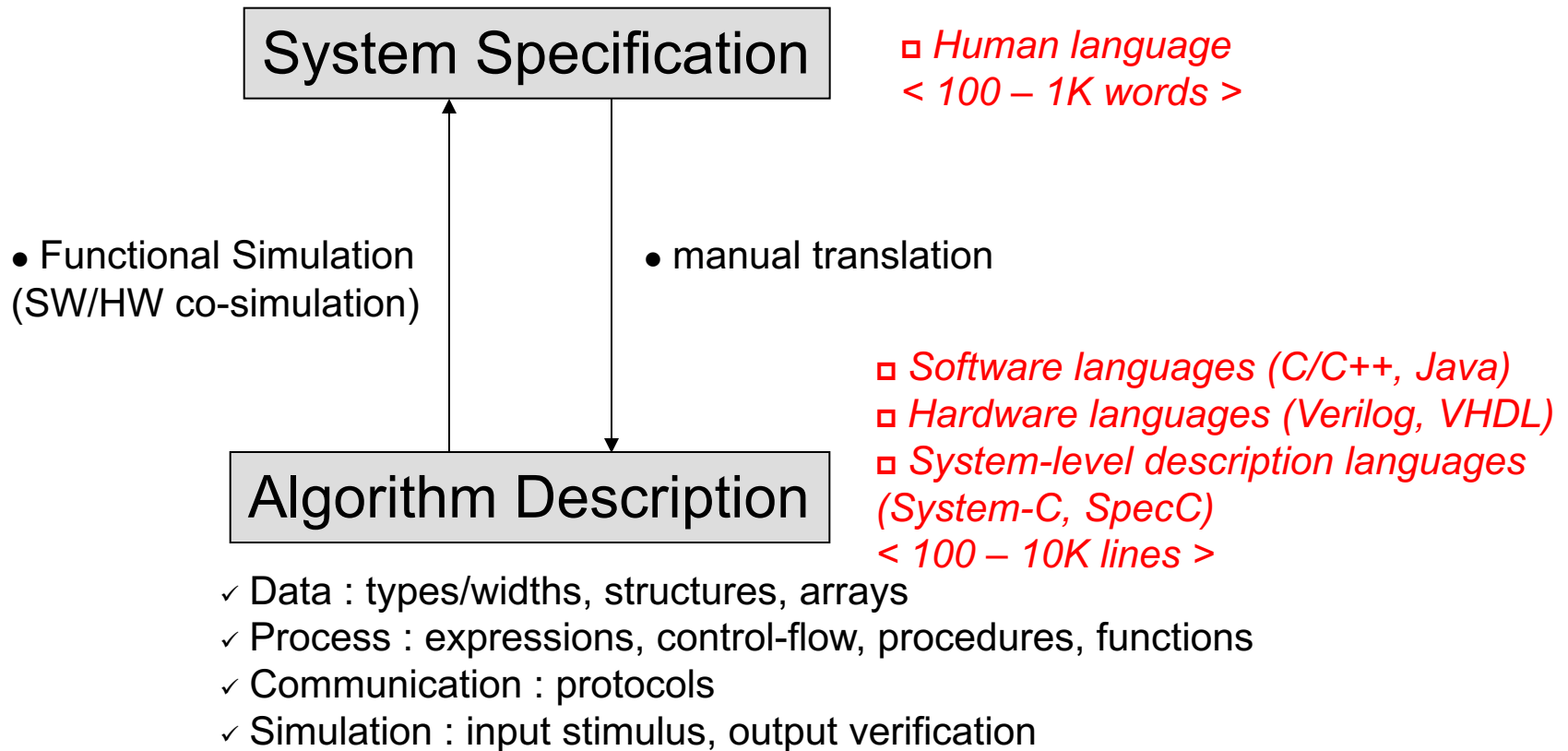


High-Level Synthesis/Verification

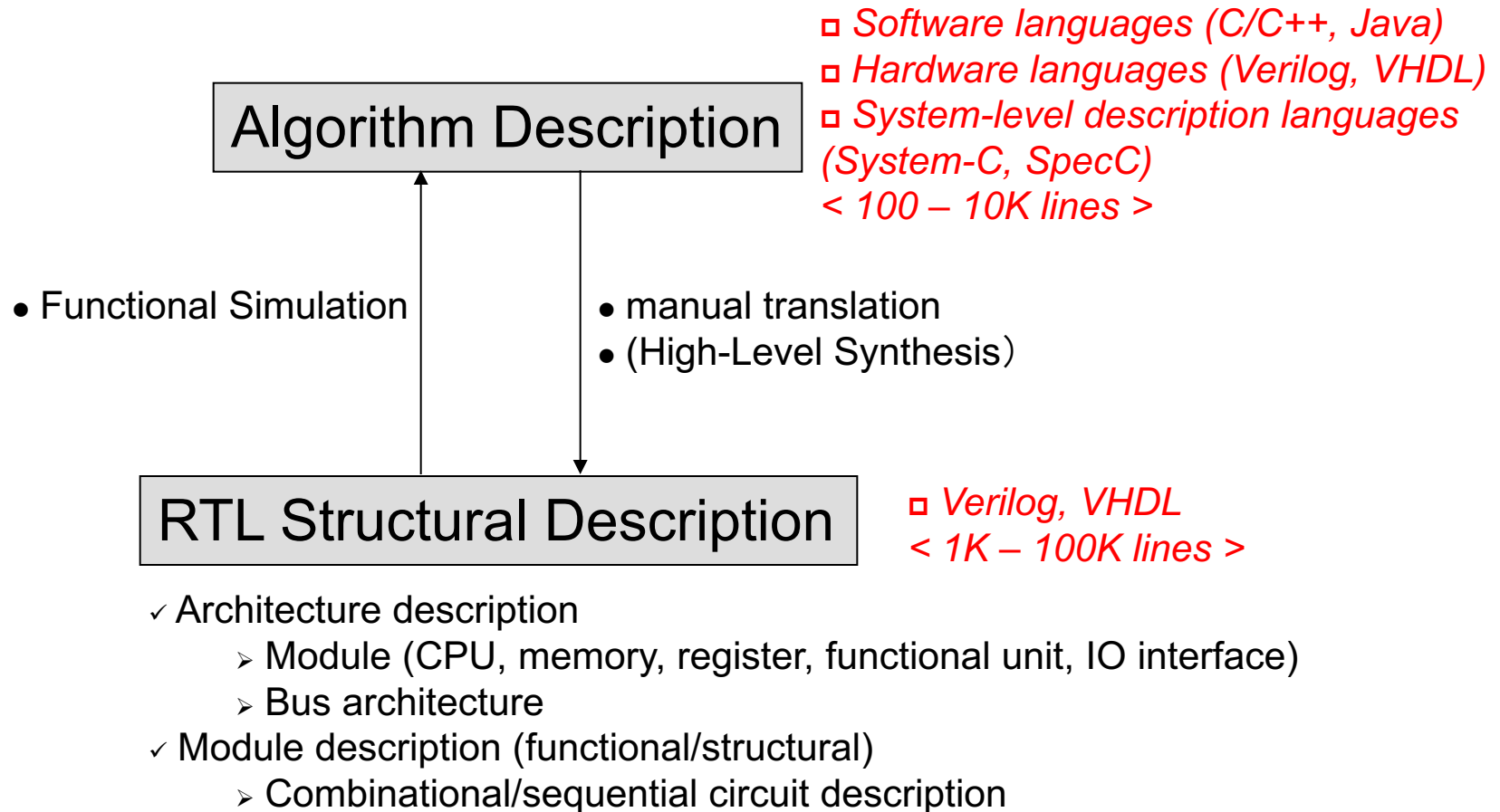


Logic Synthesis/Verification

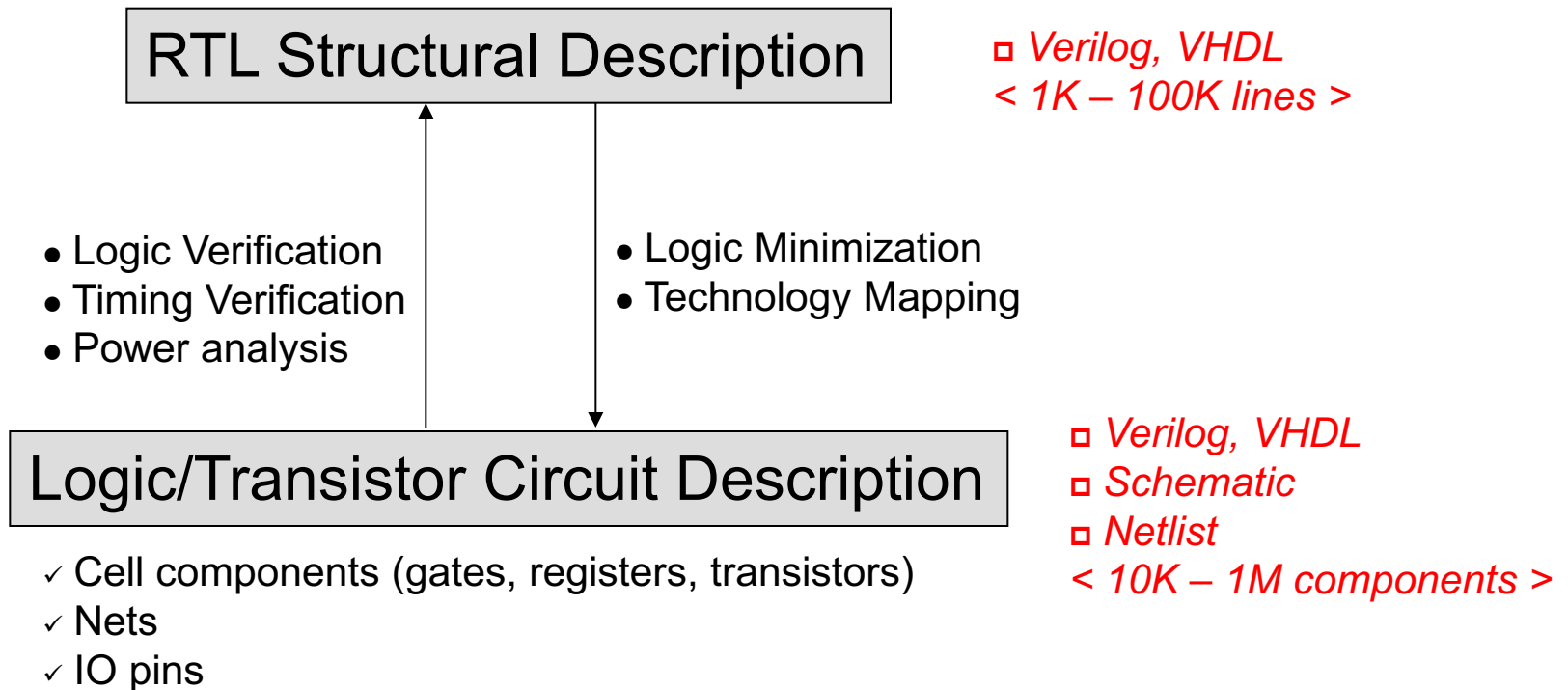

Layout Synthesis/Verification

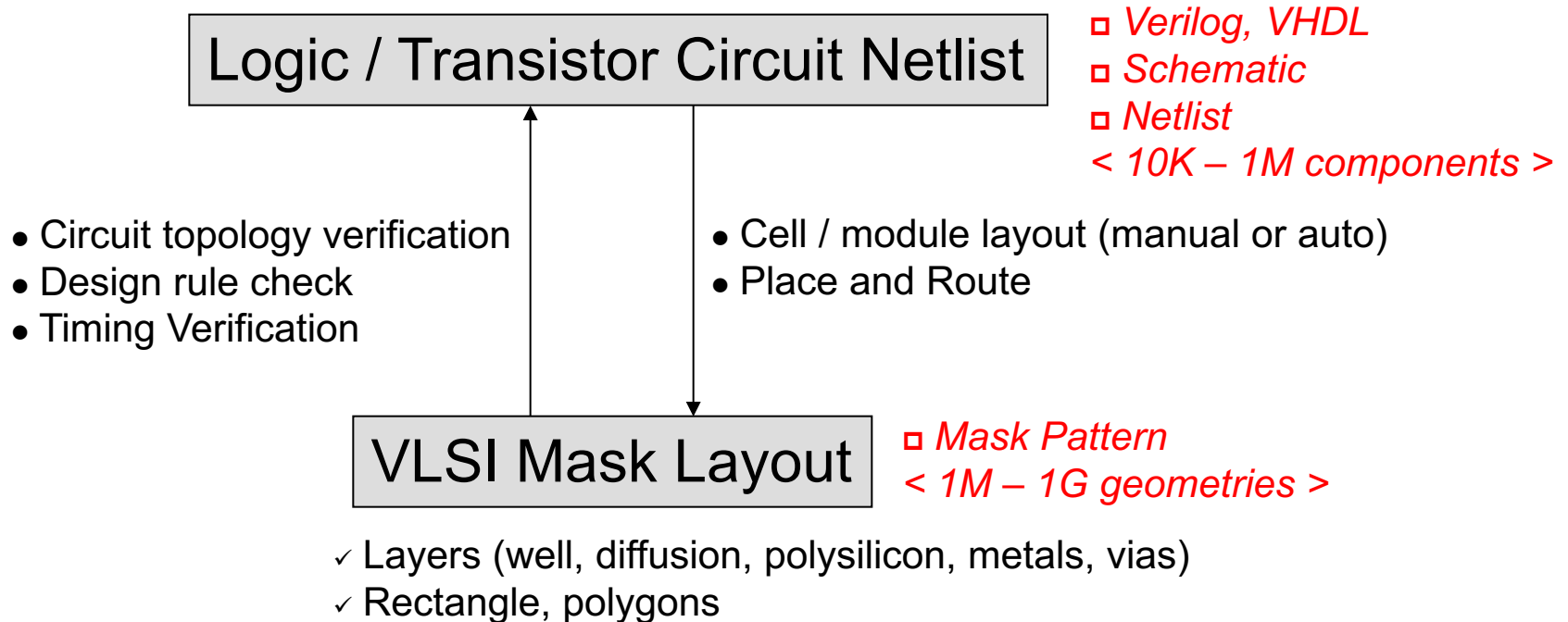

CAD Technology in VLSI Design

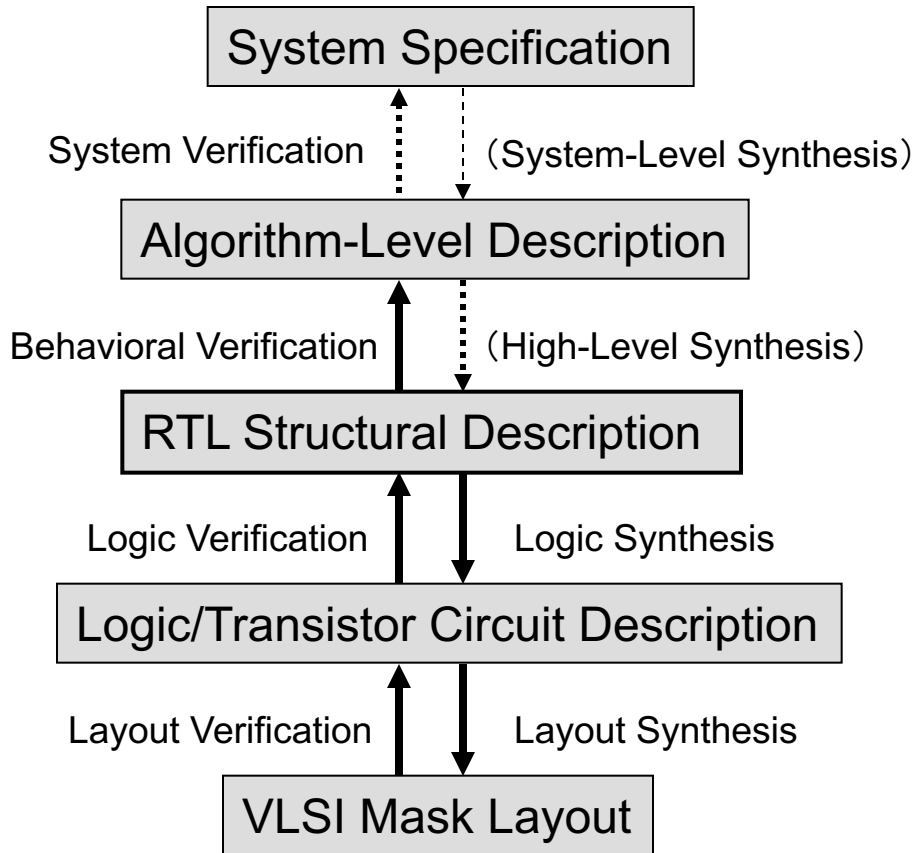

Synthesis tools : transformation of a design description into a more detailed form of description (logic synthesis, layout synthesis)

Verification tools : checking the correctness of the description (simulators, symbolic verification)

- **Logic synthesis** and **layout synthesis** tools have matured enough to be used by most designers
- **High-level synthesis** tools started to appear in real design cases (but many designers still prefer RTL as their design entry)
- **System-level synthesis** tools do not yet exist. (currently an active research area)

Course Outline

1. Introduction to VLSI system design

- VLSI design methodology and computer-Aided Design (CAD) tools
- Hardware description language and hardware behavior model

2. Logic synthesis

- Logic minimization
 - Combinational and sequential circuits
 - Two-level logic minimization
 - Multi-level logic minimization
- Technology mapping
 - Implementation technology : PLA, gate-array, standard cell, FPGA
 - Area-optimal mapping
 - Delay-optimal mapping, fan-out optimization

3. High-level synthesis

- High-level design methodology
 - Register-transfer level and behavioral level descriptions
 - Architecture (datapath, register, memory, bus, control logic)
- Operation scheduling
- Resource allocation

4. Advanced topics in system-level design issues

- Description language issues (C-based system description)
- Design verification (simulation, emulation, formal verification)
- Platform-based design (CPU-core, standard bus interface, IPs)

Modeling the Hardware Behavior Using Hardware Description Language (HDL)

- **Hardware Description Language (HDL)** is designed to describe the behavior of all kinds of digital circuits in text format (to be readable by human).
 - Primary objective of HDLs was to model the hardware and do simulation (logic synthesis was initially not the main objective).
- HDL is similar to software programming languages, BUT the execution model is different:
 - All processes occur simultaneously (concurrency)
 - All processes are either event-triggered or self-timed


Verilog Hardware Model

- *Test vector module* describes the behavior of the environment external to the circuit (usually with self-timed processes)
- *Circuit modules* describes the reactive behavior of the circuit with respect to the environment
- Hardware behavior is described by a set of *concurrent processes* whose information is exchanged via signals.

Concurrent processes

- Not all of the HDL description can be automatically synthesized into gate-level circuits. A *synthesizable code* is composed of a subset of HDL constructs which can be directly translated into logic equations and storage elements.

Synthesizable code

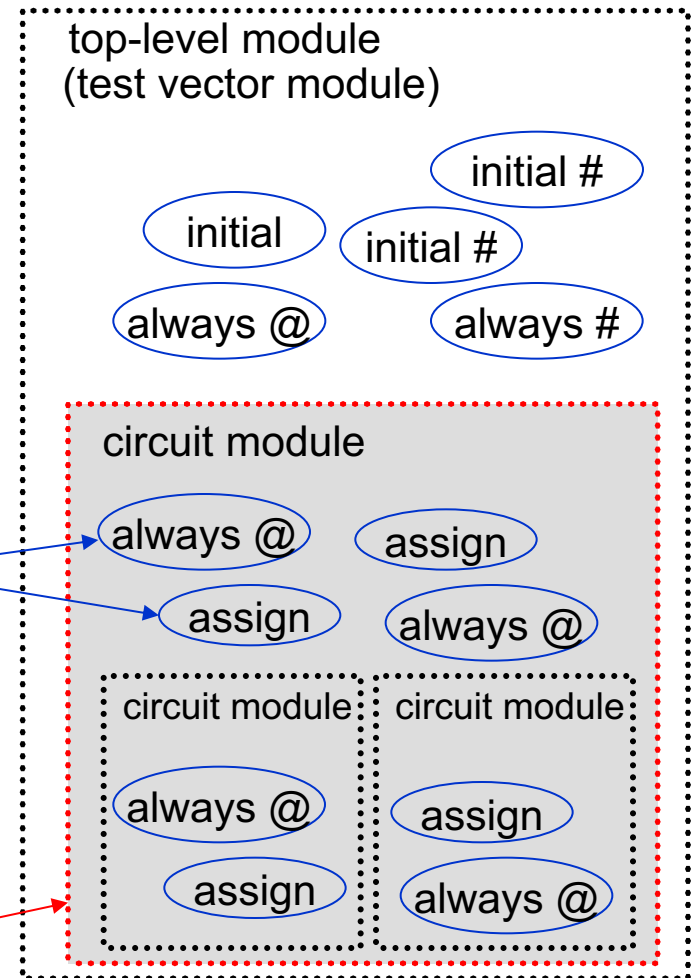

Basic Constructs in Verilog-HDL (1)

- A *module* is the basic unit for circuits to describe hierarchical structure

```
module mux(a,b,sel,c) ;  
input a, b, sel; // input port list  
output c; // output port list  
    Module_description  
endmodule
```

- *Signals* connect the circuit elements and transfer logic values
 - *Register* data type : special type of signal that can store logic value
 - *Net* data type (*wire*) : used for circuit connection (cannot store logic value)

Basic Constructs in Verilog-HDL (2)

- Logic values : **0**, **1**, **x** (undefined), **z** (high impedance)
- Bit-vector signal : signal with multiple bits (unsigned integer)
example : **wire [7:0] dbus; // 8-bit signal**
- Bit-vector constants : **<size>'<base><value>**
 - ✓ size : # of bits (default size is 32 bits, when not specified)
 - ✓ base : **b,B** = binary, **o,O** = octal, **d,D** = decimal, **h,H** = hex
(default base is decimal, when not specified)

example	size	base	value in binary
101	32	decimal	00...001100101
8'hb9	8	hex	10111001
6'b100100	6	binary	100100
6'b111	6	binary	000111
8'z	8	binary	zzzzzzzz


Hierarchy Structure on Verilog (1)

```
module mux(a,b,sel,c);  
input a, b, sel;  
output c;  
    Module_description  
endmodule
```

```
module DFF(clk,d,q);  
input clk, d;  
output q;  
reg q;  
    Module_description  
endmodule
```

module name instance name

 
```
module mux_DFF(clk,a,b,sel,c);  
input clk, a, b, sel;  
output c;  
wire d;  
    mux M0 (a,b,sel,d);  
    DFF D0 (clk,d,c);  
endmodule
```



- **Ports** (**input,output,inout**) are considered as **nets** unless explicitly specified as **registers**.
- Only **nets** (**wire**) can be used to connect module instance ports

Hierarchy Structure on Verilog (2)
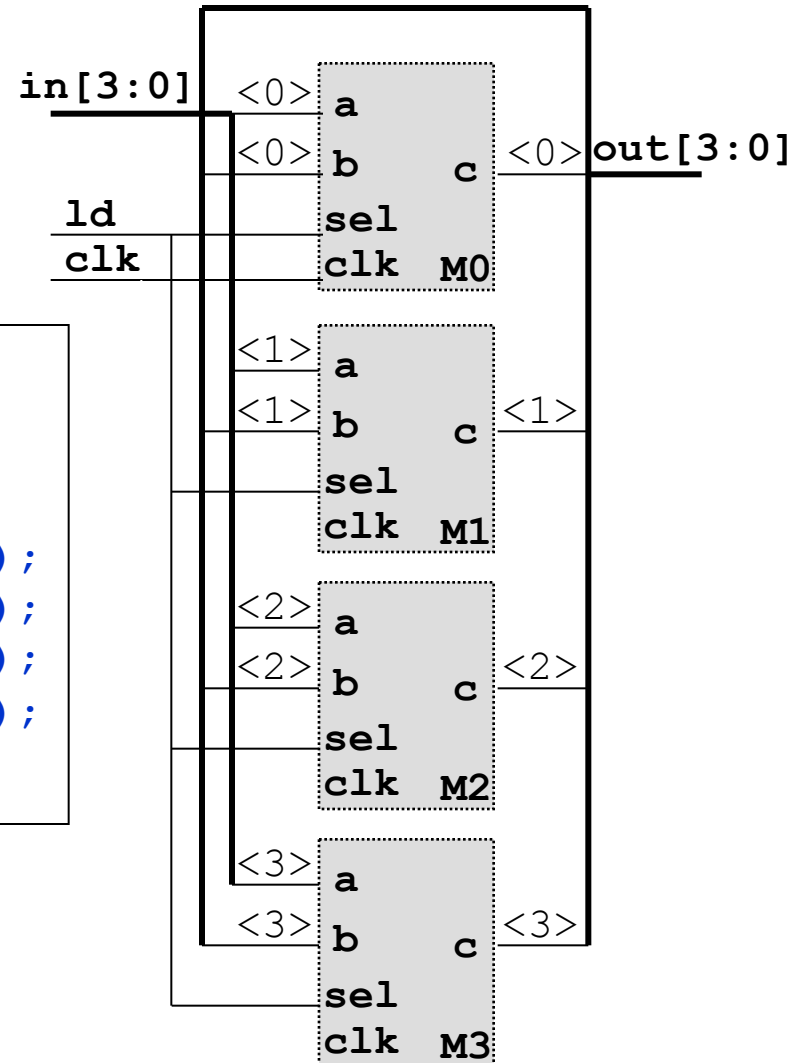
```
module REG4(clk,ld,in,out);  
input clk, ld;  
input [3:0] in;  
output [3:0] out;  
mux_DFF M0 (clk,in[0],out[0],ld,out[0]);  
mux_DFF M1 (clk,in[1],out[1],ld,out[1]);  
mux_DFF M2 (clk,in[2],out[2],ld,out[2]);  
mux_DFF M3 (clk,in[3],out[3],ld,out[3]);  
endmodule
```



Combinational Logic on Verilog (1)

- Event triggered repeated procedure (**always**)

```
reg sum, count; // register data type declaration
always @(a or b or c) begin
    sum = a ^ b ^ c;
    cout = (a & b) | (b & c) | (a & c);
end
```

("&" : AND, "|" : OR, "^" : EXOR)

- **Sensitivity list** (triggers block evaluation)

@(a or b or c) : one of the signals **a**, **b**, **c** changes its value

- ✓ In describing combinational logic, all signals on the right-hand side of the expression needs to be included in the sensitivity list.
- ✓ *Implication : if none of the signals in the sensitivity list changes, output signal does not change; therefore no need to reevaluate the expression.*

- **Statement group**

- ✓ **begin – end** : evaluate multiple statements sequentially
- ✓ **fork – join** : evaluate multiple statements concurrently (*rarely used*)

- **Data types**

- ✓ **reg** : register data type (required for assigned signals inside procedural blocks. *But in this case, this does not represent an actual "register"*)

Combinational Logic on Verilog (2)

- **If-else** statement

```
reg sum, cout;
reg [1:0] a_plus_b;
always @(a or b or c) begin
    a_plus_b = a + b;
    if (a_plus_b == 0) begin
        sum = c;
        cout = 0;
    end
    else if (a_plus_b == 1) begin
        sum = ~c;
        cout = c;
    end
    else begin
        sum = c;
        cout = 1;
    end
end
end
```

arithmetic addition

```
reg sum, cout;
reg [1:0] a_plus_b;
always @(a or b or c) begin
    a_plus_b = a + b;
    sum = c;
    cout = 1;
    if (a_plus_b == 0) begin
        sum = c;
        cout = 0;
    end
    else if (a_plus_b == 1) begin
        sum = ~c;
        cout = c;
    end
end
end
```

Initial assignments

Same behavior

*These assignments
override the initial
assignments*

Combinational Logic on Verilog (3)

- Case statement

```
reg sum, cout;
reg [1:0] a_plus_b;
always @(a or b or c) begin
    a_plus_b = a + b;
    case (a_plus_b)
        0: begin
            sum = c;
            cout = 0;
        end
        1: begin
            sum = ~c;
            cout = c;
        end
        default: begin
            sum = c;
            cout = 1;
        end
    endcase
end
```

```
reg sum, cout;
reg [1:0] a_plus_b;
always @(a or b or c) begin
    a_plus_b = a + b;
    sum = c;
    cout = 1;
    case (a_plus_b)
        0: begin
            sum = c;
            cout = 0;
        end
        1: begin
            sum = ~c;
            cout = c;
        end
    endcase
end
```

Same behavior

Combinational Logic on Verilog (4)

- **Continuous assignment (**assign**)**

```
wire sum; // net data type declaration
```

```
assign sum = a ^ b ^ c;
```

(explicit continuous assignment)

```
wire cout = (a & b) | (b & c) | (a & c);
```

(implicit continuous assignment)

- **Sensitivity list**

- ✓ By default, all signals on the right-hand side of the expression are included in the sensitivity list (if one of the signal changes, assignment is triggered and reevaluated)

- **Data types**

- ✓ **wire** : net data type (required for assigned signals in continuous assignment)

- **Continuous assignment** using conditional expression

```
assign sum = (a == 1) ? ~(b ^ c) : (b ^ c);
```

Combinational Logic on Verilog (5)

- **Function call**

```
function F_sum;  
input a, b, c;  
reg a_plus_b;  
begin  
    a_plus_b = a + b;  
    case (a_plus_b)  
        0: F_sum = c;  
        1: F_sum = ~c;  
        2: F_sum = c;  
    endcase  
end  
endfunction  
  
wire sum = F_sum(a, b, c);
```



- Function call is used to describe complex combinational logic
- Input ports become the sensitivity list (if one of the input changes, the function is reevaluated)
- Function definition must be inside the module definition

Sequential Logic on Verilog (1)

- *Transparent latch* using repeated procedure

```
reg q;  
always @(clk or d) begin  
    if (clk == 1) q = d;  
end
```

  - What is different from combinational logic description?
 - ✓ Case (clk == 0) is not specified.
- Circuit behavior
 - ✓ When (clk == 1), value of d is transferred to q (transparent).
 - ✓ When (clk == 0), value of q is unchanged (regardless of value of d)





Sequential Logic on Verilog (2)

- *D flip-flop* using 2 latches

```
reg q0, q;  
always @(clk or d) begin  
    if(clk == 0) q0 = d;  
    else if(clk == 1) q = q0;  
end
```

- *D flip-flop* using edge sensitivity list
(simpler and more common way to describe D flip-flops)
  
```
reg q;  
always @(posedge clk) begin  
    q = d;  
end
```



Sequential Logic on Verilog (3)

- 3-bit shift register using *blocking procedural assignment*

```
reg [2:0] q;  
always @(posedge clk)  
begin  
    q[2] = q[1];  
    q[1] = q[0];  
    q[0] = d;  
end
```

- *Below description is incorrect!!*

```
reg [2:0] q;  
always @(posedge clk)  
begin  
    q[0] = d;  
    q[1] = q[0];  
    q[2] = q[1];  
end
```

- *Blocking assignment* executes left side assignment *immediately after* the evaluation of the right side of the expression
(It “blocks” the following statements from entering evaluation phase until its left side assignment is completed)

1. $q[2]_{\text{next}} = q[1];$
2. $q[2] = q[2]_{\text{next}};$
3. $q[1]_{\text{next}} = q[0];$
4. $q[1] = q[1]_{\text{next}};$
5. $q[0]_{\text{next}} = d;$
6. $q[0] = q[0]_{\text{next}};$

right side evaluation

left side assignment

1. $q[0]_{\text{next}} = d;$
2. $q[0] = q[0]_{\text{next}};$
3. $q[1]_{\text{next}} = q[0];$
4. $q[1] = q[1]_{\text{next}};$
5. $q[2]_{\text{next}} = q[1];$
6. $q[2] = q[2]_{\text{next}};$

Value of d is eventually assigned to q[2]

Sequential Logic on Verilog (4)

- 3-bit shift register using *non-blocking procedural assignment*

➤ *Below description is correct!!*

```
reg [2:0] q;  
always @(posedge clk)  
begin  
    q[0] <= d;  
    q[1] <= q[0];  
    q[2] <= q[1];  
end
```

1. $q[0]_{\text{next}} = d;$
 2. $q[1]_{\text{next}} = q[0];$
 3. $q[2]_{\text{next}} = q[1];$
 4. $q[0] = q[0]_{\text{next}};$
 5. $q[1] = q[1]_{\text{next}};$
 6. $q[2] = q[2]_{\text{next}};$
- ← right side evaluation


- *Non-blocking assignment* delays the left side assignment until all expressions have completed the right side evaluation.

Sequential Logic on Verilog (5)

- Blocking vs non-blocking procedural assignments
 - *Blocking assignment*
 - Evaluation timing is consistent with software programming (easy to understand)
 - Description becomes simpler in some cases
 - Need to be careful with statement ordering
 - *Non-blocking assignment*
 - Statement ordering is more flexible
 - Description is more closer to actual circuit implementation
 - Behavior is sometimes hard to understand
 - Cannot be used in combinational logic
- Common practice
 - *Use blocking assignment for combinational logic*
 - *Use non-blocking assignment for sequential logic*

Finite State Machine on Verilog

- (1101)-String recognizer : when a sequence {1, 1, 0, 1} is detected at the input, the circuit outputs 1, otherwise outputs 0.

```
module str1101(clk, in, out);  
  input clk, in;  
  output out;  
  reg [1:0] state;  
  reg out;  
  always@(posedge clk) begin  
    state <= 2'b00;  2-bit binary value "00"  
    out <= 0;  
    case(state)  
      2'b00 : if(in == 1) state <= 2'b01;  
      2'b01 : if(in == 1) state <= 2'b10;  
      2'b10 : if(in == 0) state <= 2'b11;  
              else state <= 2'b10;  
      2'b11 : if(in == 1) begin  
                  out <= 1;  
                  state <= 2'b01;  
                end  
    endcase  
  end  
endmodule
```

Memory Model on Verilog


- Synchronous RAM

```
module mem1k_8_sync(clk, ce, we, addr, din, dout);  
  input ce, we; // ce : chip enable, we : write enable  
  input [9:0] addr; // 10-bit address  
  input [7:0] din; // 8-bit data input  
  output [7:0] dout; // 8-bit data output  
  reg [7:0] dout; // dout : reg-type  
  reg [7:0] ram[0:1023]; // 1024 address space  
  always@(posedge clk) begin  
    if(ce) begin  
      if(we) ram[addr] <= din;  
      else   dout <= ram[addr];  
    end  
  end  
end  
endmodule
```

- `@(posedge clk)` : read/write access occurs on clk positive edge
- Read (`we == 0`) : ram[addr] is transferred to dout
- Write (`we == 1`) : din is transferred to ram[addr]

Simulation on Verilog

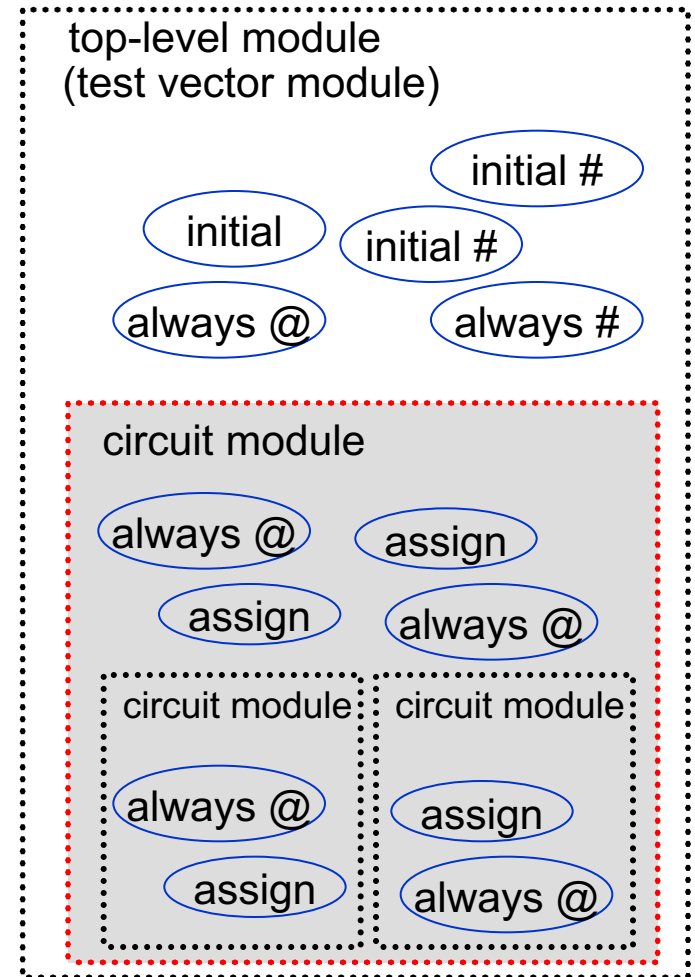- *Test vector module* describes the behavior of the environment external to the circuit (usually with self-timed processes)
- Simulation results can be displayed with wave viewer software, or can be displayed on console



Self-Timed Process on Verilog

- One-time procedure

```
initial begin
    #10 a = 0; b = 0;
    #10 a = 1;
end;
```


Delay
10 time units

- Self-timed repeated procedure


```
always begin
    #10 a = 0; b = 0;
    #10 a = 1;
end;
```

- Concurrent procedures

 
```
initial a = 1;
always begin
    #10 a = 0;
    #10 a = 1;
end;
```



initial

 

always

 

initial


always

Example of Test Vector Module

Example #1 :

```
module test;
reg clk, in;
wire out;
reg [4:0] i;
wire [15:0] seq = 16'h5d6c;
initial begin
    clk = 0;
    for(i=0;i<16;i=i+1)
    begin
        in = seq >> i;
        #50 clk = 1;
        #50 clk = 0;
    end
end
str1101 S0(clk, in, out);
endmodule
```

0101 1101 0110 1100



- Simulation automatically stops when all processes have terminated.

Example #2 :

```
module test;
reg clk, in;
wire out;
reg [4:0] i;
wire [15:0] seq = 16'h5dc6;
initial
    for(i=0;i<16;i=i+1) begin
        in = seq >> i; #100;
    end
always #50 clk = ~clk;
initial begin
    clk = 0;
    wait(i == 16) $finish;
end
str1101 S0(clk, in, out);
endmodule
```

- When there is an endless process, simulation can be explicitly terminated by **\$finish** command

Simulation Output Command

```
module str1101(clk, in, out);
input clk, in;
output out;
reg [1:0] state;
reg out;
always@(posedge clk) begin
    $display($stime, " in(%b) ,out(%b) ,state(%b)",
             in, out, state);
    state <= 2'b00;
    out <= 0;
    case(state)
        2'b00 : if(in == 1) state <= 2'b01;
        2'b01 : if(in == 1) state <= 2'b10;
        2'b10 : if(in == 0) state <= 2'b11;
                else state <= 2'b10;
        2'b11 : if(in == 1) begin
                    out <= 1;
                    state <= 2'b01;
                end
    endcase
end
endmodule
```

Simulation Output Result

```
50  in(0) , out(x) , state(xx)
150 in(0) , out(0) , state(00)
250 in(1) , out(0) , state(00)
350 in(1) , out(0) , state(01)
450 in(0) , out(0) , state(10)
550 in(1) , out(0) , state(11)
650 in(1) , out(1) , state(01)
750 in(0) , out(0) , state(10)
850 in(1) , out(0) , state(11)
950 in(0) , out(1) , state(01)
1050 in(1) , out(0) , state(00)
1150 in(1) , out(0) , state(01)
1250 in(1) , out(0) , state(10)
1350 in(0) , out(0) , state(10)
1450 in(1) , out(0) , state(11)
1550 in(0) , out(1) , state(01)
```

The diagram illustrates state transitions in a simulation. Red dotted boxes group lines of output that share the same 'in' value. Red dotted circles highlight specific 'out' values. Red arrows indicate the sequence of state changes.

- Box 1 (in=1):** Lines 250, 350, 550, 650, 850.
- Box 2 (in=0):** Lines 450, 750, 950, 1350.
- Box 3 (in=1):** Lines 1150, 1250, 1450.
- Box 4 (in=0):** Lines 1550.

Highlighted 'out' values (circles):

- Line 650: out(1)
- Line 950: out(1)
- Line 1550: out(1)

Arrows indicate the flow from the first 'in(1)' box to the first 'out(1)' circle, and from the second 'in(0)' box to the second 'out(1)' circle.

Tips on Simulation and Verification (1)

- State initialization

- In simulation, register values are initially undefined.
- In real circuits, registers can take arbitrary initial values
- In order to force the state to a known desired state, a proper input sequence needs to be fed into the circuit.

Simulation

```
50 in(0), out(x), state(xx)
150 in(0), out(0), state(00)
250 in(1), out(0), state(00)
```

Real circuit

```
50 in(0), out(x), state(10)
150 in(0), out(0), state(11)
250 in(1), out(0), state(00)
```

- Regardless of the initial state, the first two 0s at the input forces the state to go into initial state at the 2nd clock cycle.
- *HOWEVER, many state machine does not have a proper input sequence to force to a known desired state from arbitrary (possibly unreachable) states → add “reset” input*

Tips on Simulation and Verification (2)

- In general, forcing the state to a known desired state is simply done by adding a “reset” signal input

```
module str1101(clk, rst_n, in, out);
    input clk, rst_n, in; // rst_n : asynchronous reset (active low)
    output out;
    reg [1:0] state;
    reg out;
    always@(posedge clk or negedge rst_n) begin
        state <= 2'b00;
        out <= 0;
        if(~rst_n) // if reset is deactivated
            case(state)
                2'b00 : if(in == 1) state <= 2'b01;
                2'b01 : if(in == 1) state <= 2'b10;
                2'b10 : if(in == 0) state <= 2'b11;
                        else state <= 2'b10;
                2'b11 : if(in == 1) begin
                            out <= 1;
                            state <= 2'b01;
                        end
            endcase
    end
endmodule
```

Tips on Simulation and Verification (3)

- In any system, coding the appropriate test vectors is not easy (probably harder than coding the actual circuit)
 - The designer needs to take account all the possible input patterns so as to cover the complete behavior of the circuit
 - For a large system, test vector covering only a small portion of the complete behavior takes very long time to simulate. This results in very low design productivity, and also leaves a large number of “bugs” left undetected.
 - To verify a large system, *Circuit Emulation* technique is often used (the system is implemented on a set of programmable logic devices and run on actual environment).

Verilog Reference on the WEB

- ***On-line Verilog HDL Quick Reference Guide***
by Stuart Sutherland of Sutherland HDL, Inc. -
Portland, Oregon, USA

http://www.emmelmann.org/Library/Tutorials/docs/verilog_ref_guide/vlog_ref_top.html

HDL Summary

- **Hardware Description Languages (HDLs)** are designed to describe the behavior of all kinds of digital circuits in text format (to be readable by human).
- A subset of HDL description can be automatically transformed to gate-level circuit by logic synthesis tools (“synthesizable” RTL code).
- With the current increase in design complexity, doing designs on RTL is becoming too time consuming
 - Although the description is in text format, concurrent behavior of HDL is still hard to track by human, giving more opportunities for errors and making debugging even harder.
 - Software languages are far more easy to track, since everything occurs sequentially.
 - Population of HDL programmers is much smaller than that of software programmers.
 - *Strong need for high-level synthesis tools*

Problem 1.1

Design the following circuits in Verilog.

- Give complete module description for each circuit
 - Explain the behavior
 - (If you have access to Verilog simulator) create simple test vector module and confirm the behavior on simulation
- A) 4-bit ripple-carry adder using full-adder modules
- B) 4-bit counter with enable/reset inputs in register-transfer level description (use arithmetic operators directly on the 4-bit signals)
- increment only when “enable” is 1
 - set the counter to 0 when “reset” is 1
- C) Describe the 4-bit counter in B) using 4-bit ripple-carry adder in A)
- D) Unsigned multiplier (4-bit inputs, 8-bit output) (use whatever architecture such as “shift-and-add” , “array” , “Booth”)

Problem 1.2

Consider the following integer divider module


```
module divide8(clk, start, a, b, ready, q, r);
input clk, start;
input [7:0] a, b;
output ready;
output [7:0] q, r;

reg [7:0] q, r, a0, b0;
reg [3:0] state;
reg ready;

wire [7:0] a1;
assign a1[7:1] = r[6:0];
assign a1[0] = a0[7];

wire sub = (a1 >= b0);

    always@(posedge clk) begin
        if(state < 8) state <= state + 1;
        if(start == 0) begin
            state <= 0; ready <= 0;
            q <= 0; r <= 0;
        end
        else if(state == 0) begin
            a0 <= a; b0 <= b;
        end
        else if(ready == 0) begin
            if(state == 8) ready <= 1;
            r <= (sub)? a1 - b0 : a1;
            q <= (q << 1) + sub;
            a0 <= a0 << 1;
        end
    end
end
endmodule
```

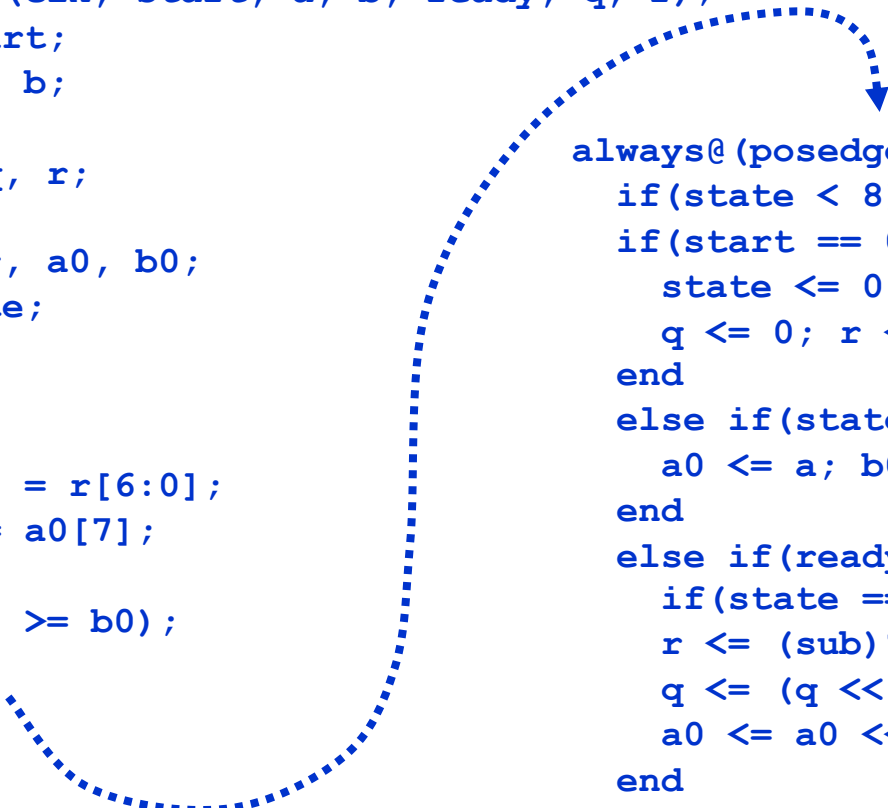A diagram showing a curved arrow pointing from the 'sub' wire to the 'ready' output in the always block.

Problem 1.2

A) Explain the algorithm of this divider.

- How is the division computed?
- What are the roles for each variable?

B) Assume :

- **a** = 8' b01100100 (=100), **b** = 8' b00001001 (=9)
- **start** = 0 for the first clock cycle, and **start** = 1 after that.

Explain the behavior of the circuit at each clock cycle (explain the values of each variable at each clock cycle).

C) Modify this divider module so that it can handle 16-bit inputs.

D) Using the above 16-bit divider module, design a circuit which converts 16-bit binary value into 5-digit decimal value (each decimal digit consumes 4-bit)

Problem 1.3 (*extra credit*)

Design a simple calculator on Verilog with the following specification

- There are 14 keys ('0' , '1' , ..., '9' , '+' , '=' , 'C'). When a key is pushed, a 4-bit signal associated with the key is generated with a proper control signal.
- There is a 4-digit decimal number display which can display 12 types of characters ('0' , '1' , ..., '9' , 'E' , ' '). To control the 4-digit display, the calculator circuit outputs 16-bit signal, each 4-bit group controlling each digit position.
- Entering 'C' resets the calculator. [' ' , ' ' , ' ' , '0'] is displayed.
- If the result is greater than 9999, [' ' , ' ' , ' ' , 'E'] is displayed to indicate error.
- For other specifications, follow the conventions of actual calculator.