

# **VLSI System Design**

## **Part II : Logic Synthesis (1)**

**Lecturer : Tsuyoshi Isshiki**

Dept. Information and Communications Engineering,  
Tokyo Institute of Technology  
[issiki@ict.e.titech.ac.jp](mailto:issiki@ict.e.titech.ac.jp)

# Logic Synthesis

## 1. Logic synthesis types

### a. Combinational logic synthesis

- Two-level logic
- Multi-level logic


### b. Sequential logic (finite state machine) synthesis

- State minimization
- State encoding

## 2. Currently available logic synthesis CAD tool

- Mainly two-level/multi-level logic synthesis
- State code optimization for sequential logic

# Logic Synthesis Flow

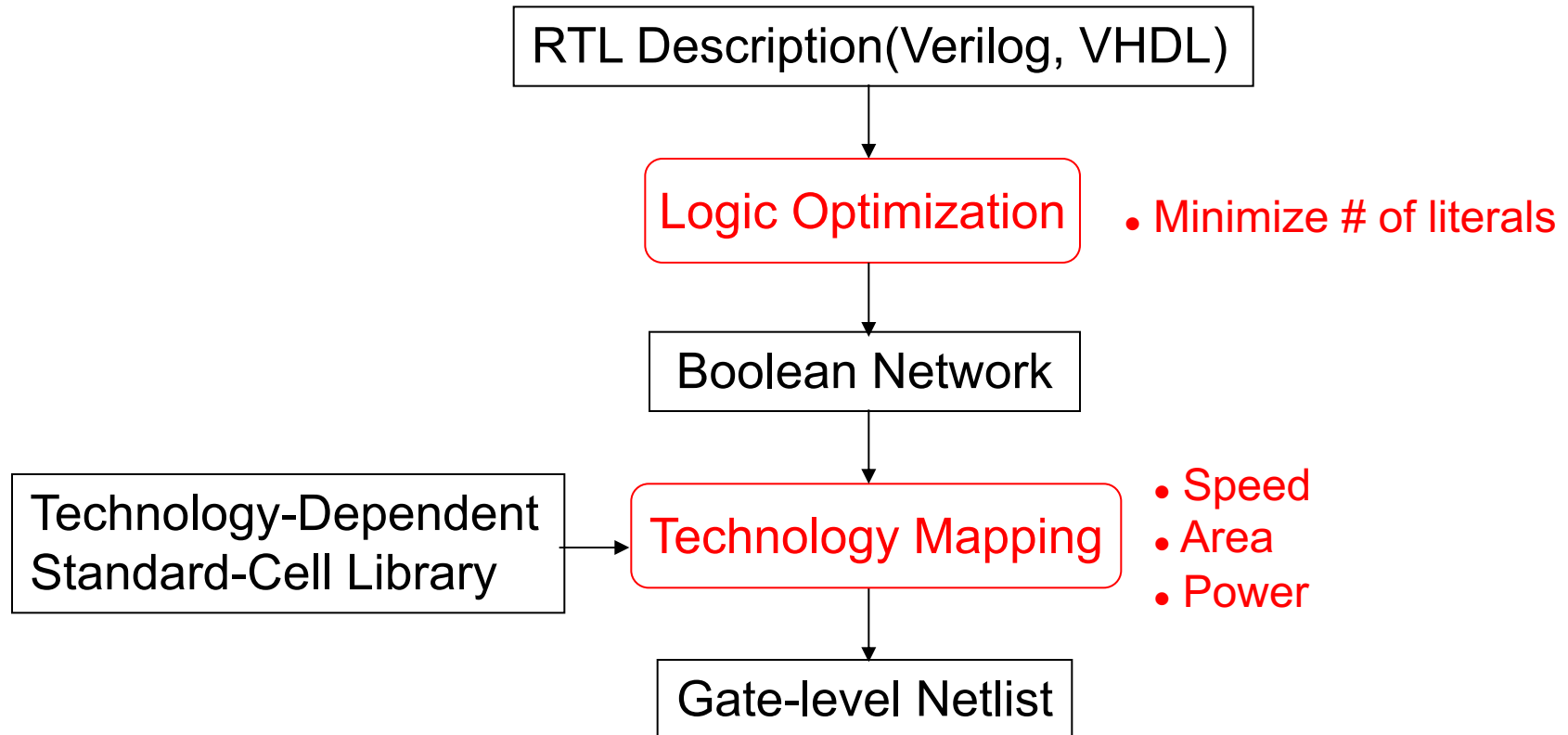

# RTL-to-Logic Translation (1)

## A) **Combinational logic extraction :**

*RTL description is partitioned into combinational logic part and storage elements (DFF, latches)*


```
module str1101(clk, in, out);  
input clk, in;  
output out;  
reg [1:0] state;  
reg out;
```

```
always@(posedge clk) begin  
    state <= 2'b00;  
    out <= 0;  
    case(state)  
        2'b00: if(in == 1) state <= 2'b01;  
        2'b01: if(in == 1) state <= 2'b10;  
        2'b10: if(in == 0) state <= 2'b11;  
               else state <= 2'b10;  
        2'b11: if(in == 1) begin  
                    out <= 1;  
                    state <= 2'b01;  
                end  
    endcase  
end  
endmodule
```

```
reg [1:0] n_state;  
reg n_out;
```

```
always@(in or state) begin  
    n_state = 2'b00;  
    n_out = 0;  
    case(state)  
        2'b00: if(in == 1) n_state = 2'b01;  
        2'b01: if(in == 1) n_state = 2'b10;  
        2'b10: if(in == 0) n_state = 2'b11;  
               else n_state = 2'b10;  
        2'b11: if(in == 1) begin  
                    n_out = 1;  
                    n_state = 2'b01;  
                end  
    endcase  
end
```
 
```
always@(posedge clk) begin  
    state <= n_state; out <= n_out;  
end
```




# RTL-to-Logic Translation (2)
 
## B) *Logic equation transformation :*

*For each output variable, compute the conditions in which the value evaluates as 1, 0, and don't-care (DC).*


```
begin
  n_state = 2'b00;
  n_out = 0;
  case(state)
    2'b00: if(in == 1) n_state = 2'b01;
    2'b01: if(in == 1) n_state = 2'b10;
    2'b10: if(in == 0) n_state = 2'b11;
           else n_state = 2'b10;
    2'b11: if(in == 1) begin
              n_out = 1;
              n_state = 2'b01;
            end
          endcase
end
```



```
if(state == 2'b00 && in == 1 ||
   state == 2'b10 && in == 0 ||
   state == 2'b11 && in == 1)
  n_state[0] = 1;
else n_state[0] = 0;
```

```
if(state == 2'b01 && in == 1 ||
   state == 2'b10)
  n_state[1] = 1;
else n_state[1] = 0;
```
 
```
if(state == 2'b11 && in == 1)
  n_out = 1;
else n_out = 0;
```



```
n_state[0] =
  (~state[0] & ~state[1] & in ||
   ~state[0] & state[1] & ~in ||
   state[0] & state[1] & in);

n_state[1] =
  (state[0] & ~state[1] & in ||
   ~state[0] & state[1]);

n_out = state[0] & state[1] & in;
```

# RTL-to-Logic Translation (3)

## A) *Combinational logic extraction*

```
module str11011(clk, rst, in, out);
input clk, in;
output out;
reg [2:0] state;
reg out;
always@(posedge clk) begin
    state <= 3'b000;
    out <= 0;
    if(rst == 0)
        case(state)
            3'b000: if(in == 1) state <= 3'b001;
            3'b001: if(in == 1) state <= 3'b010;
            3'b010: if(in == 0) state <= 3'b011;
                     else state <= 3'b010;
            3'b011: if(in == 1) state <= 3'b100;
            3'b100: if(in == 1) begin
                        out <= 1;
                        state <= 3'b010;
                    end
            default: begin // don't-care state
                        state <= 3'bx;
                        out <= x;
                    end
        endcase
    endmodule
```



```
.....
reg [2:0] n_state;
reg n_out;

always@(in or rst or state) begin
    n_state = 3'b000;
    n_out = 0;
    if(rst == 0)
        case(state)
            3'b000: if(in == 1) n_state = 3'b001;
            3'b001: if(in == 1) n_state = 3'b010;
            3'b010: if(in == 0) n_state = 3'b011;
                     else n_state = 3'b010;
            3'b011: if(in == 1) n_state = 3'b100;
            3'b100: if(in == 1) begin
                        n_out = 1;
                        n_state = 3'b010;
                    end
            default: begin // don't-care state
                        n_state = 3'x;
                        out = x;
                    end
        endcase
    end
```


```
always@(posedge clk) begin
    state <= n_state; out <= n_out;
end
```

.....

# RTL-to-Logic Translation (4)
 
## ***B) Logic equation transformation :***

```
begin
  n_state = 3'b000;
  n_out = 0;
  if(rst == 0)
    case(state)
      3'b000: if(in == 1) n_state = 3'b001;
      3'b001: if(in == 1) n_state = 3'b010;
      3'b010: if(in == 0) n_state = 3'b011;
               else n_state = 3'b010;
      3'b011: if(in == 1) n_state = 3'b100;
      3'b100: if(in == 1) begin
                  n_out = 1;
                  n_state = 3'b010;
                end
      default: begin // don't-care state
                  n_state = 3'x;
                  out = x;
                end
    endcase
  end
```



```
if(state == 3'b000 && in == 1 ||
   state == 3'b010 && in == 0)
  n_state[0] = 1;
else_if(state == 3'b101 ||
   state == 3'b110 ||
   state == 3'b111)
  n_state[0] = x;
else_n_state[0] = 0;
```


```
if(state == 3'b001 && in == 1 ||
   state == 3'b010 ||
   state == 3'b100 && in == 1)
  n_state[1] = 1;
else_if(state == 3'b101 ||
   state == 3'b110 ||
   state == 3'b111)
  n_state[1] = x;
else_n_state[1] = 0;
```

```
if(state == 3'b011 && in == 1)
  n_state[2] = 1;
else_if(state == 3'b101 ||
   state == 3'b110 ||
   state == 3'b111)
  n_state[2] = x;
else_n_state[2] = 0;
```


```
if(state == 3'b100 && in == 1)
  n_out = 1;
else_if(state == 3'b101 ||
   state == 3'b110 ||
   state == 3'b111)
  n_out = x;
else_n_out = 0;
```
 
# Boolean Function Implementation Using Two-Level Logic


- The study of logic synthesis started from two-level logic
- Optimized two-level logic is often the starting point for multi-level logic synthesis.
- Several types of two-level logic
  - **Sum-of-product** (1<sup>st</sup> level : AND, 2<sup>nd</sup> level : OR)
  - **NAND-NAND** (has the same structure as sum-of-product)
  - **Product-of-sum** (1<sup>st</sup> level : OR, 2<sup>nd</sup> level : AND)
  - **NOR-NOR** (has the same structure as product-of-sum)




sum-of-product

 

NAND-NAND

 

product-of-sum

 


NOR-NOR

*All four circuits implement the same function*


 
# Programmable Logic Array

- A programmable logic array is a device which can implement arbitrary Boolean function in sum-of-product form with  $N$  inputs,  $M$  outputs, and  $R$  products (cubes).
- Minimizing the number of products  $R$  results in smaller area ( $N$  and  $M$  are fixed for a given function)





# Boolean Function Terminologies (1)

1. Boolean function  $f$  with  $N$  inputs and  $M$  outputs is a mapping  $f: \{0, 1\}^N \rightarrow \{0, 1, X\}^M$ . ( $X$ : don't-care)
2. If mapping to don't-care values does not exist, the function is said to be *completely specified*. Otherwise it is said to be *incompletely specified*.
3. If  $M = 1$ , it is called a *single-output function*. Otherwise it is called a *multiple-output function*.
4. For each output  $f_m$  of function  $f$ :
  - *ON-set* is defined as the set of input values  $x$  such that  $f_m(x) = 1$
  - *OFF-set* is defined as the set of input values  $x$  such that  $f_m(x) = 0$
  - *DC-set* is defined as the set of input values  $x$  such that  $f_m(x) = X$
5. A *literal* is a Boolean variable or its complement.
6. A *cube* is a conjunction of literals (a product term).
7. A *cover* is a set of cubes (interpreted as sum-of-product term).

# Boolean Function Terminologies (2)

8. A **bit vector notation** of a cube describes the polarity of each literal (0 : complemented literal, 1 : uncomplemented literal) for each variable in the Boolean function. If a variable does not appear in the cube, it is denoted as '-' (also don't-care)  
Ex.  $x_3 \bar{x}_2 x_1 \bar{x}_0 \rightarrow 1010$        $x_3 x_2 \bar{x}_0 \rightarrow 11-0$
9. A cube is called a **k-cube** if there are  $k$  elements of '-' (don't-care) in the bit vector notation.
10. A **minterm** is a cube that contains all variables in the Boolean function. Each minterm belongs to either the ON-set, OFF-set or the DC-set of a particular output of the function. A minterm is a 0-cube.

```
if(state == 3'b000 && in == 1 ||  
    state == 3'b010 && in == 0)  
    n_state[0] = 1;  
else_if(state == 3'b101 ||  
        state == 3'b110 ||  
        state == 3'b111)  
    n_state[0] = x;  
else n_state[0] = 0;
```

  


function  $f_{n\_state[0]}(state[2], state[1], state[0], in)$


# Boolean Function Terminologies (3)

 11. The input variable space  $\{0, 1\}^N$  can be modeled as a **binary  $N$ -dimensional hypercube**

- Each vertex in the hypercube represents a minterm.
- $k$ -cube is represented by a binary  $k$ -dimensional hypercube
- $k$ -dimensional hypercube is sometimes referred to as “binary  $k$ -cube”





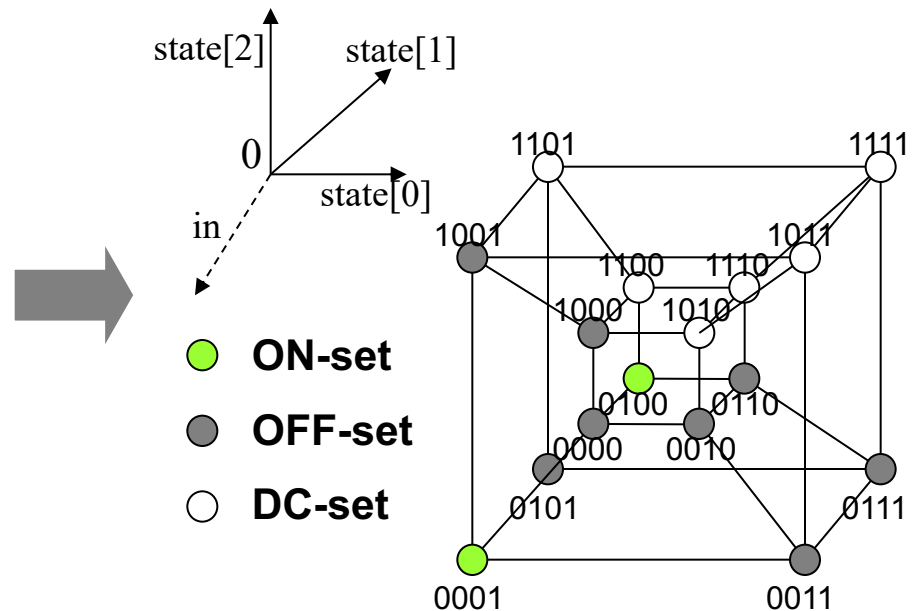
function  $f_{n\_state[0]}(state[2], state[1], state[0], in)$



# Boolean Function Terminologies (4)
   
## 12. Analogy of Boolean algebra to Class calculus (*Set Theory*)




- logic variable  $\rightarrow$  set
- logic negation  $\rightarrow$  complement set
- logical 1  $\rightarrow$  universal set
- logical 0  $\rightarrow$  null set ( $\phi$ )
- logical AND  $\rightarrow$  set intersection ( $a \cdot b \rightarrow a \cap b$ )
- logical OR  $\rightarrow$  set union ( $a + b \rightarrow a \cup b$ )



# Boolean Function Terminology (4)

  
 
## 13. Partial order and containment

- Partial order of logic variables :  $f \leq g \Leftrightarrow (\text{if } f = 1, \text{ then } g = 1) \Leftrightarrow f \cdot g = f$ 
  - Interpretation in set theory  $\rightarrow$  containment of sets :  $f \subseteq g$
- Partial order of logic expression (cubes and covers) :
  - $a b c \leq a b \rightarrow a b c \subseteq a b$
  - $b c \leq a b + \bar{a} c \rightarrow b c \subseteq a b + \bar{a} c$
  - $a \bar{c} + b c \leq a b + \bar{a} c + a \bar{b} \bar{c} \rightarrow a \bar{c} + b c \subseteq a b + \bar{a} c + a \bar{b} \bar{c}$
- ✓ Terminologies for set theory (intersection, union, containment) is often applied to logic expressions.



# Boolean Function Terminology (5)

  14. An **implicant** for a particular output of a function is a cube which contains minterms only in the ON-set and DC-set. (*In other words, a cube which does not intersect with the OFF-set*)
15. A **prime implicant** (or simply, **prime**) is an implicant that is not contained by any other implicant, and intersects with the ON-set.
16. An **essential prime implicant** (or **essential prime**) is a prime that contains one or more minterms which are not contained by other primes.
17. A **legal cover** for a function is a set of implicants which contains the ON-set and does not intersect with OFF-set (may intersect with DC-set).



Implicants :  $a\bar{b}\bar{c}$ ,  $\bar{a}\bar{b}c$ ,  
 $a\bar{b}c$ ,  $a\bar{b}\bar{c}$ ,  $\bar{a}b\bar{c}$ ,  
 $a\bar{b}$ ,  $\bar{a}\bar{b}$ ,  $a\bar{c}$ ,  $\bar{b}\bar{c}$

Primes :  $\bar{a}\bar{b}$ ,  $a\bar{c}$ ,  $\bar{b}\bar{c}$

Essential primes :  $\bar{a}\bar{b}$ ,  $a\bar{c}$

Legal cover :  $\bar{a}\bar{b} + a\bar{c}$

# Two-Level Logic Optimization

- Input : Boolean function representation using
  - Truth table *or*
  - Set of cubes in the ON-, OFF- and DC-sets.
    - ✓ *Since the union of the ON-, OFF- and DC-sets is the universal set, specifying two sets (ex. ON-set and DC-set) is sufficient for describing a Boolean function.*
    - ✓ *For a completely specified function, only the ON-set is needed.*
- Output : optimized Boolean function in terms of number of cubes (or sometimes number of literals)
- Algorithm :
  - A) Enumerate all prime implicants of the target function
  - B) Select a minimum set of prime implicants which are required to contain the ON-set of the target function.



# Preparation : Cube Reduction

- For a pair of cubes  $A$  and  $B$ , if there exists an cube  $C$  such that  $A + B = C$ , then  $A$  and  $B$  are said to be **adjacent** and are **reducible** to  $C$ .
- On the bit-vector representations, adjacency of a pair of implicants can be determined by comparing elements in each position : if only one position is different, and if all '-' positions are same, then the implicant pair is adjacent.

	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	
<i>a b c <math>\bar{d}</math></i>	1	1	1	0	
<i>a b c d</i>	1	1	1	1	
<i>a b c</i>	1	1	1	-	<b>reducible</b>
<i>a b <math>\bar{c}</math></i>	1	1	0	-	
<i>a b c</i>	1	1	1	-	<i>don't-cares at the same position</i>
<i>a b</i>	1	1	-	-	<b>reducible</b>

# Single-Output 2-Level Logic Minimization Using Quine-McCluskey Method (1)

## 1. Prime implicant extraction

- A) From the truth table, delete minterms in OFF-set.  
(0-cube table : contains only minterm implicants)
- B)  $k=0$ .
- C) Let  $N$  be the # of rows in  $k$ -cube table.  
If  $N=0$ , then terminate.
- D) for( $i = 0$ ;  $i < N$ ;  $i ++$ )  
for( $j = i + 1$ ;  $j < N$ ;  $j ++$ )  
If rows  $i$  and  $j$  are adjacent,
  - mark these 2 rows with ‘ \* ’
  - add a reduced cube to  $(k+1)$ -cube table
  - Output part of the reduced cube is 1 if it intersects with the ON-set. Otherwise (if it is fully contained in the DC-set), it is x.
- E)  $k=k+1$ . Go to C) .
- F) Rows whose output is 1 and without ‘ \* ’ marked are the prime implicants.

truth table

$x[3:0]$	$f[1]$
0000	0
0001	1
0010	0
0011	0
0100	0
0101	1
0110	0
0111	x
1000	1
1001	0
1010	1
1011	0
1100	1
1101	1
1110	1
1111	0

0-cube table

$x[3:0]$	$f[1]$
0001	1 *
0101	1 *
0111	x *
1000	1 *
1010	1 *
1100	1 *
1101	1 *
1110	1 *

1-cube table

$x[3:0]$	$f[1]$
0-01	1
01-1	1
-101	1
10-0	1 *
1-00	1 *
1-10	1 *
110-	1
11-0	1 *

2-cube table

$x[3:0]$	$f[1]$
1--0	1

# Single-Output 2-Level Logic Minimization Using Quine-McCluskey Method (2)

**0-cube table**

$x[3:0]$   $f[1]$   
-----

0001 1 \*  
0101 1 \*  
0111 x \*  
1000 1 \*  
1010 1 \*  
1100 1 \*  
1101 1 \*  
1110 1 \*

**1-cube table**

$x[3:0]$   $f[1]$   
-----


0-01 1  
01-1 1  
-101 1  
10-0 1 \*  
1-00 1 \*  
1-10 1 \*  
110- 1  
11-0 1 \*

**2-cube table**

$x[3:0]$   $f[1]$   
-----

1--0 1  
1--0 1

 *identical cubes are  
generated here.  
(delete the 2<sup>nd</sup> cube  
from the list)*



# Single-Output 2-Level Logic Minimization Using Quine-McCluskey Method (3)

## 2. Prime implicant table generation

- Assign ON-set minterms to each row
- Assign prime implicants to each column
- For each minterm row, mark an 'x' at the column whose prime implicant contains this minterm

## 3. Prime implicant cover extraction containing all ON-set minterm

(*minimumunate covering problem : NP-complete*)

- Delete dominated prime (column) and dominating minterm (row)
- Extract essential primes and delete all minterms (rows) which are contained in these essential primes.
- Arbitrary select a prime and delete all minterms which are contained in this prime.

prime implicant

$x[3:0]$	$f[1]$	0	0	-	1	1
		-	1	1	1	-
		0	-	0	0	-
		1	1	1	-	0
0001	1	x	x	x		
0101	1	x	x	x		
1000	1					x
1010	1					x
1100	1				x	x
1101	1			x	x	
1110	1					x

ON-set minterm

*Techniques to reduce the problem complexity (can be applied in any order)*

# Single-Output 2-Level Logic Minimization Using Quine-McCluskey Method (4)

## 3.A Elimination of dominating minterms

- **Prime set for a minterm**

A set of primes which contain the minterm

Ex: prime set for 0101 is {0-01, 01-1, -101}

- **Dominating minterm :**

On a pair of minterms, if the prime set of one of the minterm contains that of the other, the former minterm is said to be the *dominating minterm* of the latter.

- Prime set is the set of candidate for covering the particular minterm.  
*Dominating* minterms can be eliminated from the problem since the prime which covers some *dominated* minterm always covers the corresponding *dominating* minterm.

		0	0	-	1	1
		-	1	1	1	-
		0	-	0	0	-
x[3:0]	f[1]	1	1	1	-	0
0001	1	x				
0101	1	x	x	x		
1000	1					x
1010	1					x
1100	1				x	x
1101	1			x	x	
1110	1					x

- Row **0101** is the dominating minterm of row **0001**.
- Row **1100** is the dominating minterm of rows **1000**, **1010** and **1110**.

# Single-Output 2-Level Logic Minimization Using Quine-McCluskey Method (5)

## 3.A Elimination of dominated primes

- Minterm set for a prime**

A set of minterms which are contained by the prime

**Ex:** minterm set for 0-01 is {0001, 0101}

- Dominated prime :**


On a pair of primes, if the minterm set of one of the prime contains that of the other, the latter prime is said to be the *dominated prime* of the former.

- *Dominated* primes can be eliminated from the problem since the entire minterm set of a *dominated* prime is always covered by the *dominating* prime.

		0	0	-	1	1
		-	1	1	1	-
		0	-	0	0	-
		1	1	1	-	0
x[3:0]	f[1]					
0001	1	x				
0101	1	x	x	x		
1000	1					x
1010	1					x
1100	1				x	x
1101	1			x	x	
1110	1					x

- Column **01-1** is the dominated prime of column **0-01** and **-101**.
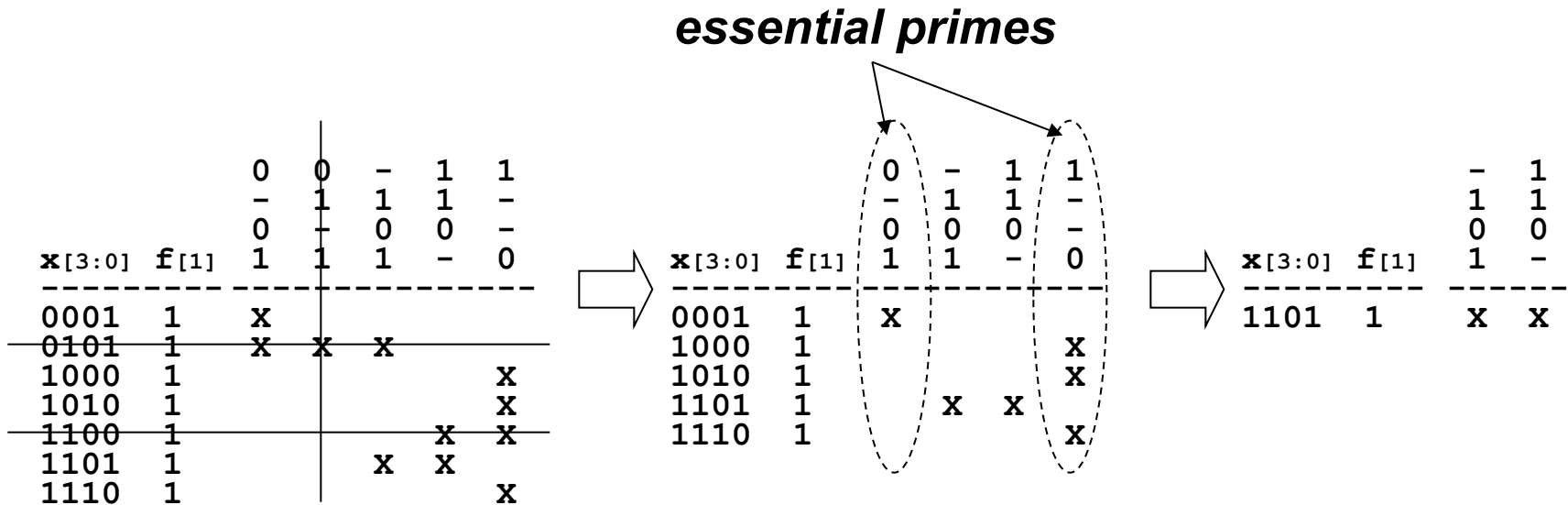
# Single-Output 2-Level Logic Minimization Using Quine-McCluskey Method (6)



## 3.B Extraction of essential primes

- An **essential prime implicant** (or **essential prime**) is a prime that has at least one ON-set minterm which are not contained in any other primes. Such minterms are called **essential minterms**.

# Single-Output 2-Level Logic Minimization Using Quine-McCluskey Method (7)

select an arbitrary prime

$x[3:0]$	$f[1]$		
1101	1	-	1
		1	1
		0	0
		1	-
		x	x

No minterm left to cover  
**TERMINATE**

$x[3:0]$	$f[1]$	
		1
		1
		0
		-

obtained prime cover

$x[3:0]$	$f[1]$	0 - 0 1	0 1 - 1	- 1 0 1	1 1 0 -	1 - - 0
0001	1	x				
0101	1	x	x	x		
1000	1					x
1010	1					x
1100	1				x	x
1101	1			x	x	x
1110	1					x

## 3.C Arbitrary selection of remaining primes


- If 3.A (*elimination of dominating minterms and dominated primes*) and 3.B (*essential prime extraction*) cannot further be applied, select an arbitrary remaining prime and delete the rows (minterms) which is contained in this prime. Try 3.A and 3.B again.
- If all minterms have been covered, then **TERMINATE**.
- In order to obtain an optimal cover, do all combinations of the arbitrary prime selection.



# Multiple-Output 2-Level Logic Minimization Using Quine-McCluskey Method (1)

## 1. Prime Implicant Extraction

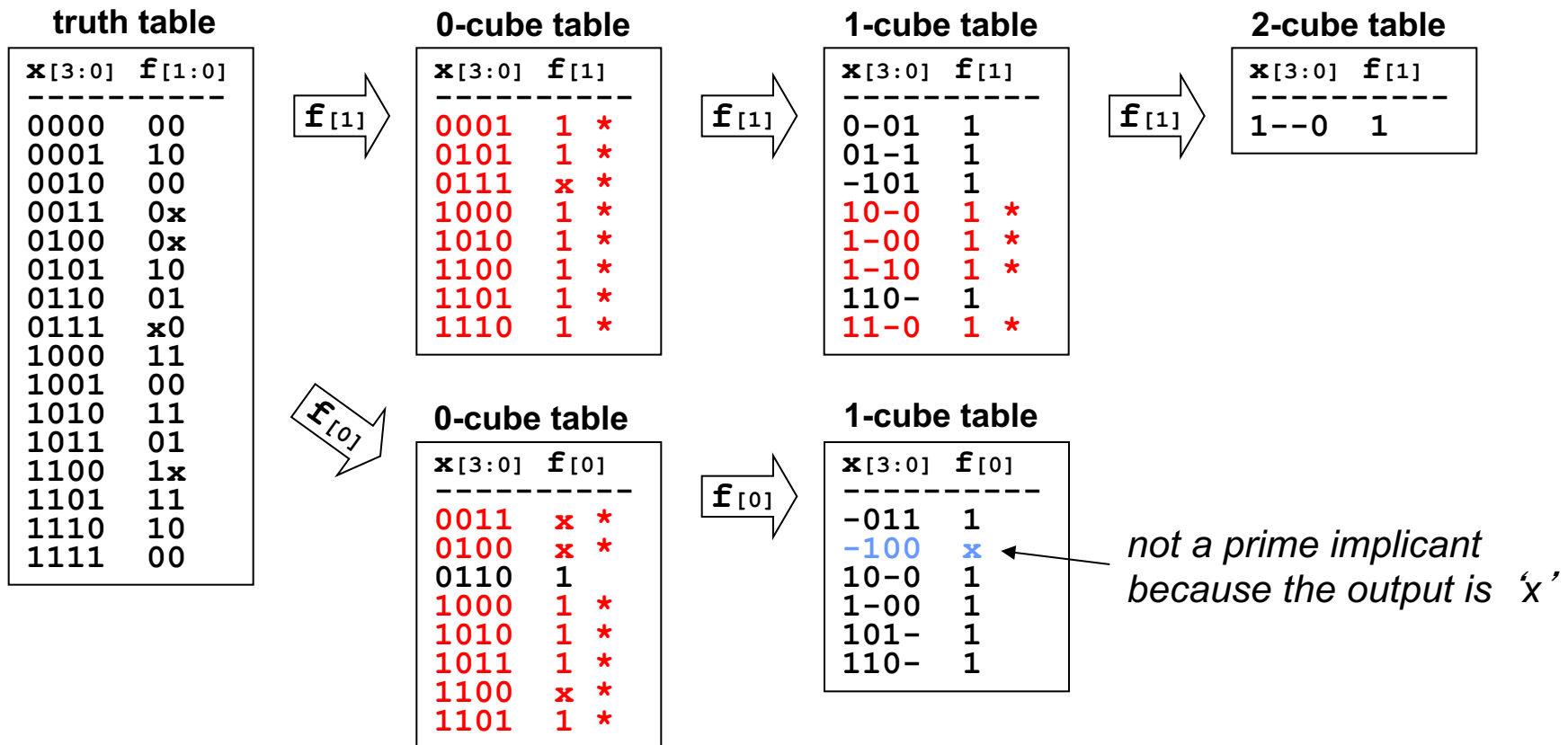A) Extract the prime implicants for each output separately.



# Multiple-Output 2-Level Logic Minimization Using Quine-McCluskey Method (2)

## 2. Prime Implicant List Merging

- ✧  $m^{\text{th}}$  prime implicant list corresponds to the prime implicant list for the  $m^{\text{th}}$  output
- ✧  $m^{\text{th}}$  outputs in  $m^{\text{th}}$  prime implicant list are all 1s by definition

A) For each prime  $p$  in the all prime implicant lists

- $m^{\text{th}}$  output is 1 if there exists a prime in the  $m^{\text{th}}$  prime implicant list which contains  $p$ .
- $m^{\text{th}}$  output is 0 otherwise.

➤ *This allows implicants other than the primes to be included in the candidate for minterm covering.*

prime implicant list

$x[3:0]$	$f[1:0]$
0-01	10
01-1	10
-101	10
110-	11
1--0	10
0110	01
-011	01
10-0	11
1-00	11
101-	01
110-	11

*these are identical primes  
delete one of them from the list*

# Multiple-Output 2-Level Logic Minimization Using Quine-McCluskey Method (3)

## 3. Prime implicant table generation

- A) Assign ON-set minterms to each row *for each output*
- B) Assign prime implicants to each column
- C) For each minterm row,
  - mark an 'I' at the column whose output part of the corresponding prime implicant is 0 for the corresponding output of this minterm
  - Otherwise, mark an 'X' at the column whose prime implicant contains this minterm

		0	0	-	1	1	0	-	1	1	1
		-	1	1	1	-	1	0	0	-	0
		0	-	0	0	-	1	1	-	0	1
x[3:0]	f[1:0]	1	1	1	-	0	0	1	0	0	-
0001	1-	x									
0101	1-	x	x	x							
1000	1-					x			x	x	
1010	1-					x			x		
1100	1-				x	x				x	
1101	1-			x	x						
1110	1-					x					
0110	-1						x				
1000	-1								x	x	
1010	-1								x		x
1011	-1						x				
1101	-1				x						

*These primes cannot be used for covering because they intersect with the OFF-set of the corresponding output*

# Multiple-Output 2-Level Logic Minimization Using Quine-McCluskey Method (4)

## 4. Prime implicant cover extraction containing all ON-set minterms

(same as the single-output case)

$x[3:0]$	$f[1:0]$	0 - 0 1	0 1 - 1	- 1 0 1	1 1 - 0	1 - 1 0	0 1 1 0	- 1 1 1	0 1 - 0	1 - 0 0	1 0 1 -
0001	1-	X									
0101	1-	X	X	X							
1000	1-					X			X	X	
1010	1-					X			X		
1100	1-				X	X				X	
1101	1-			X	X						
1110	1-				X						
0110	-1						X				
1000	-1							X	X		
1010	-1										X
1011	-1							X			X
1101	-1				X						X

$x[3:0]$	$f[1:0]$	0 - 0 1	1 1 0 -	1 - 0 0	0 1 - 0	1 0 - 0	1 - 0 0	1 0 1 -
0001	1-	X						
1101	1-		X	X				
1110	1-				X			
0110	-1					X		
1000	-1						X	X
1010	-1						X	
1011	-1							X
1101	-1			X				X

$x[3:0]$	$f[1:0]$	0 - 0 1	1 1 0 -	1 - 0 0	0 1 1 0	1 0 - 0	1 0 1 -
0001	1-	X					
1110	1-			X			
0110	-1				X		
1000	-1					X	
1011	-1						X
1101	-1		X				

# Improving Quine-McCluskey Method (Espresso-EXACT, UC Berkeley)

- **Problems**

- Need to specify all minterms
- Need a large number of cube reducibility tests.
  - Only a small portion will pass the test to generate reduced cubes.
  - Identical primes may be generated multiple times.
- Size of the prime implicant table is large since each row corresponds to minterms

- **Improvements**

- Extract all the prime implicants directly without enumerating minterms.
- Generate a *reduced prime implicant table* and solve the minimum covering problem on this smaller table.

# Direct Extraction of Prime Implicants (Preperation 1)

- **Corollary 1** : Let  $P$  be a cover for a *completely specified* function  $f$ . For any implicant  $c$  of  $f$ , there exists  $c' \in P$  such that  $c \subseteq c'$  if and only if  $P$  includes all primes of  $f$ .
- **Theorem 1** : Let  $P_f$  and  $P_g$  be the covers for *completely specified* functions  $f$ , and  $g$ , respectively. And let  $P_{fg}$  be  $P_f \cdot P_g$  that is expanded in sum-of-product form. If  $P_f$  and  $P_g$  include all primes for  $f$  and  $g$ , respectively, then  $P_{fg}$  includes all primes of function  $f \cdot g$ .
- **Proof** :
  - By definition,  $P_{fg}$  is a cover whose cube elements are the non-zero conjunctions of a cube in  $P_f$  and cube in  $P_g$ ;  

$$P_{fg} = \{c_f \cdot c_g \mid c_f \in P_f, c_g \in P_g, c_f \cdot c_g \neq 0\}.$$
  - Any implicant of the function  $f \cdot g$  is also an implicant for both  $f$  and  $g$  (if  $f \cdot g$  is true, then both  $f$  and  $g$  must be true as well). Thus for any implicant  $c$  of  $f \cdot g$ , there exists  $c_f \in P_f$  and  $c_g \in P_g$  such that  $c \subseteq c_f$  and  $c \subseteq c_g$ . Therefore  $c \subseteq c_f \cdot c_g \in P_{fg}$ .


# Direct Extraction of Prime Implicants (Preperation 2)

- **Theorem 2:** Let  $P$  be a cover for a *completely specified* function  $f$ , and  $P'$  be the cover for the complement of  $f$  (denoted as  $\bar{f}$ ) which is obtained by applying De-Morgan's Law to  $P$  and then expanding it to sum-of-product form.  $P'$  includes all primes of  $\bar{f}$ .

(Let us call this the **Negate-And-Expand Method**)

- **Proof :**
  - Let  $P = c_0 + c_1 + \dots + c_n$  ( $c_i$  is a cube)
  - By De-Morgan's Law :  $\bar{P} = \overline{c_0 + c_1 + \dots + c_n} = \bar{c}_0 \cdot \bar{c}_1 \cdot \dots \cdot \bar{c}_n$  ---- (1)
  - A complement of a cube becomes a cover composed of single-literal cubes. Each single-literal cube is the prime of this cover.  
Ex.  $\overline{x_0 \cdot \bar{x}_1 \cdot x_2} = \bar{x}_0 + x_1 + \bar{x}_2$
  - Since each term in eq(1) becomes a cover composed of primes for that cover, expanding these terms into sum-of-product form results in a cover composed of all primes of  $\bar{f}$ . (according to Theorem 1)

# Negate-And-Expand Method

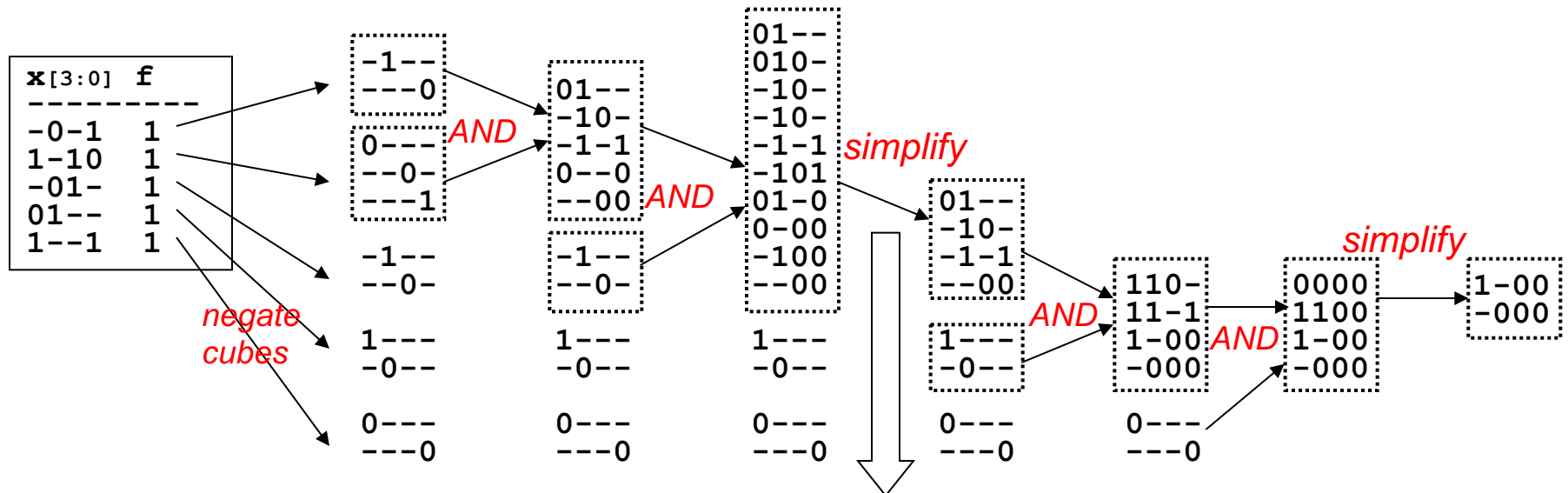

## Single Cube Containment Minimality

For each cube in the list, if some other cube contains it, then delete this cube from the list.

Ex:

$01--$  contains  $010-$  (delete  $010-$ )

$-1-1$  contains  $-101$  (delete  $-101$ )


$01--$	*	← delete
$010-$	*	
$-10-$	*	← delete
$-10-$	*	
$-1-1$	*	
$-101$	*	
$01-0$	*	
$0-00$	*	
$-100$	*	
$---00$	*	


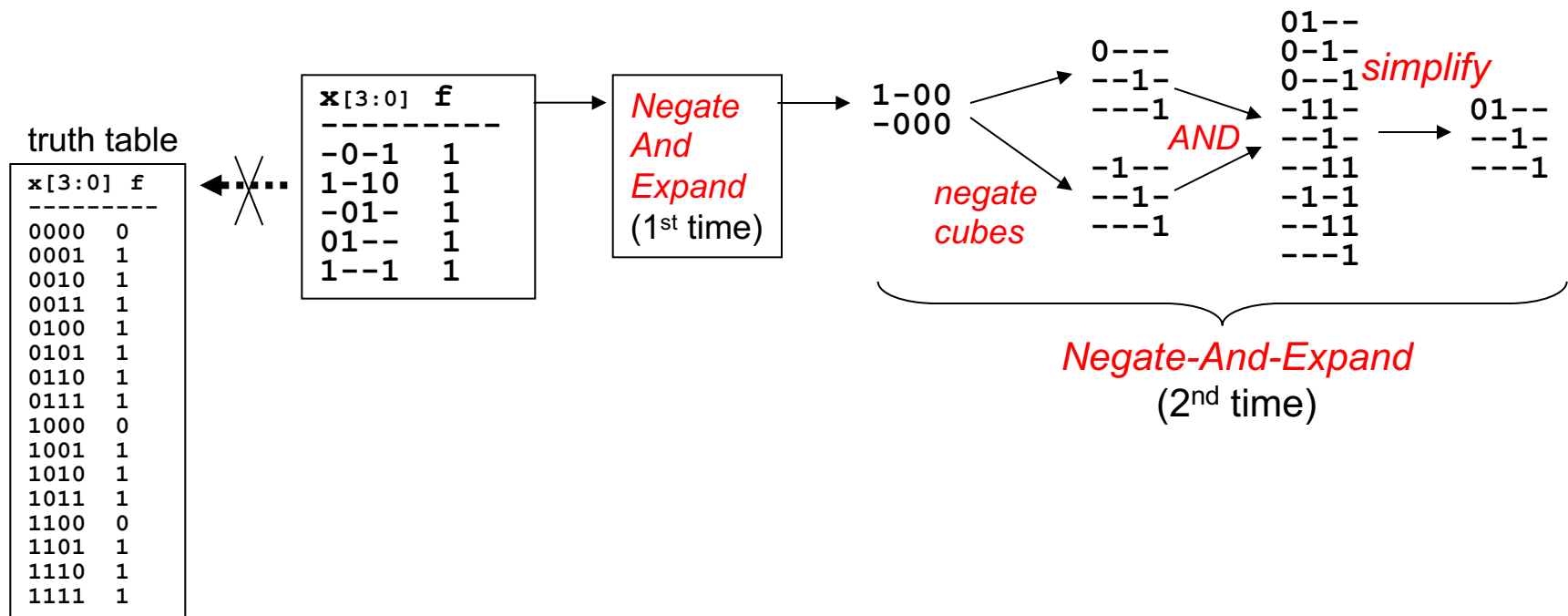
# Direct Extraction of Prime Implicants for Completely Specified Functions


- By applying *Negate-And-Expand* twice on a cover for a *completely specified* function  $f$ , the obtained cover becomes the entire set of primes for  $f$ .

Ex.  $f = x_0 \bar{x}_2 + \bar{x}_0 x_1 x_3 + x_1 \bar{x}_2 + x_2 \bar{x}_3 + x_0 x_3$


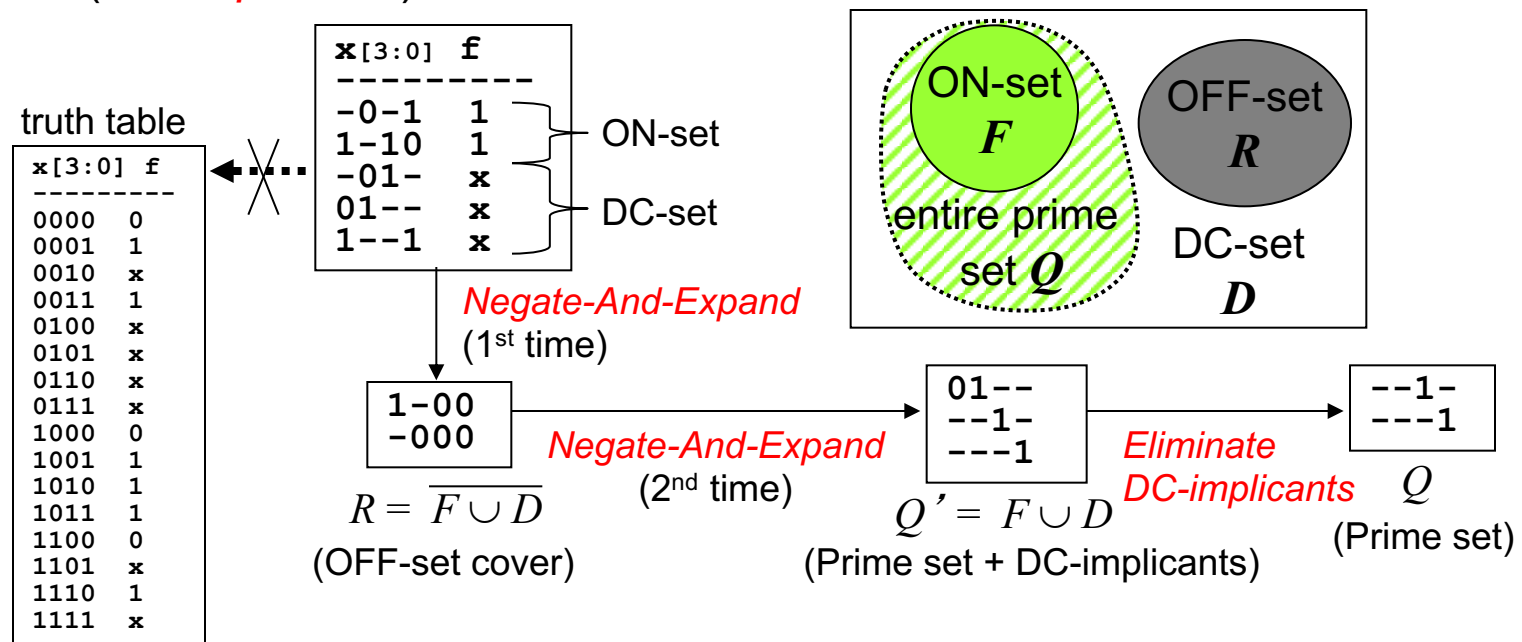
# Direct Extraction of Prime Implicants for *Incompletely Specified Functions*

- For an incompletely specified function  $f$ , apply the Negate-And-Expand operations twice on the cover containing both the ON-set and DC-set. The obtained cover includes all primes of  $f$  and possibly other implicants which do not intersect with the ON-set. (*DC-implicants*)



# Function Negation Methods (1)

- Computation time of *Negate-And-Expand* operation can become very long when there are a large degree of redundancy in the cover representation of the function (i.e. a large number of small cubes).
- While the 2<sup>nd</sup> negation requires *Negate-And-Expand* operation in order to obtain the entire prime set, the obtained cover after the 1<sup>st</sup> negation (OFF-set cover) does not have to be the entire prime set for the negated function.
- *Shannon Expansion* method can be used for the 1<sup>st</sup> negation to obtain the OFF-set cover.
- The cover obtained by Shannon Expansion does not include all primes for the negated function, but its redundancy is relatively low. Also, the computational complexity is significantly lower than Negate-And-Expand Method.

# Shannon Expansion

- $f_{x_i}$  : cofactor of  $f$  with respect to factor  $x_i$

$$f_{x_i} = f(x_0, \dots, x_{i-1}, 1, x_{i+1}, \dots, x_{n-1}), \quad f_{\bar{x}_i} = f(x_0, \dots, x_{i-1}, 0, x_{i+1}, \dots, x_{n-1})$$

$$\text{Ex : } f = a \bar{b} \bar{c} + a c \bar{d} + \bar{b} c d$$

$$f_a = \bar{b} \bar{c} + c \bar{d} + \bar{b} c d, \quad f_{\bar{a}} = \bar{b} c d, \quad f_{ac} = \bar{d} + \bar{b} d$$

- Shannon expansion :  $f = x_i f_{x_i} + \bar{x}_i f_{\bar{x}_i}$
- Shannon expansion negation :  $\bar{f} = x_i \bar{f}_{x_i} + \bar{x}_i \bar{f}_{\bar{x}_i}$
- Recursive Shannon expansion negation :

$$\text{Ex : } f = a \bar{b} \bar{c} + a b c + \bar{b} c$$


$$\bar{f} = a \bar{f}_a + \bar{a} \bar{f}_{\bar{a}} = a (\bar{b} \bar{c} + b c + \bar{b} c) + \bar{a} (\bar{b} \bar{c})$$

$$\bar{f}_a = b \bar{f}_{ab} + \bar{b} \bar{f}_{a\bar{b}} = b (\bar{c}) + \bar{b} (\bar{c} + c) = b \bar{c}$$

$$\bar{f}_{\bar{a}} = b \bar{f}_{\bar{a}b} + \bar{b} \bar{f}_{\bar{a}\bar{b}} = b (0) + \bar{b} (\bar{c}) = b + \bar{b} \bar{c}$$

$$\bar{f} = a \bar{f}_a + \bar{a} \bar{f}_{\bar{a}} = a (b \bar{c}) + \bar{a} (b + \bar{b} \bar{c}) = a b \bar{c} + \bar{a} b + \bar{a} \bar{b} \bar{c}$$

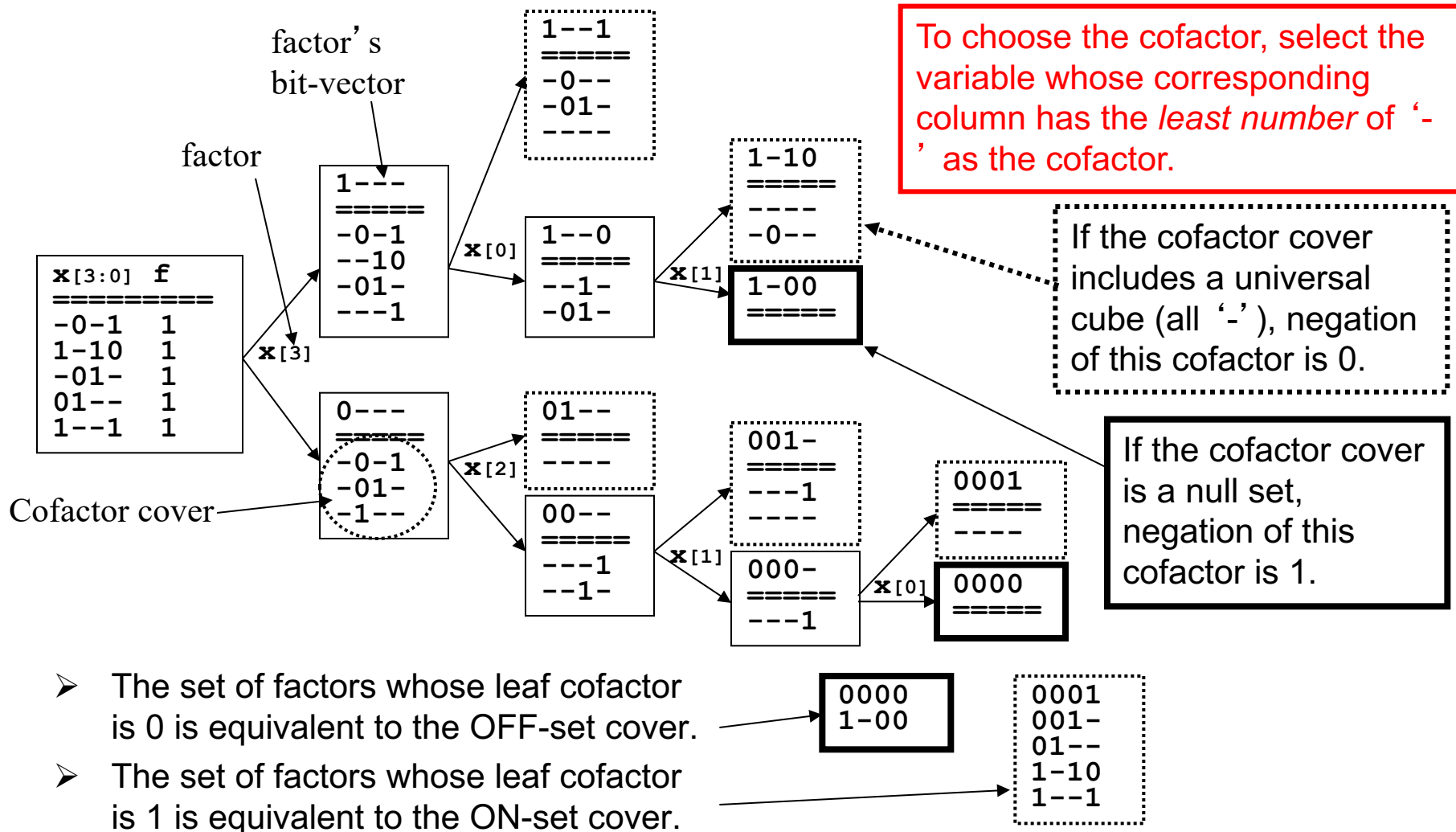
# Function Negation by Shannon Expansion (1)



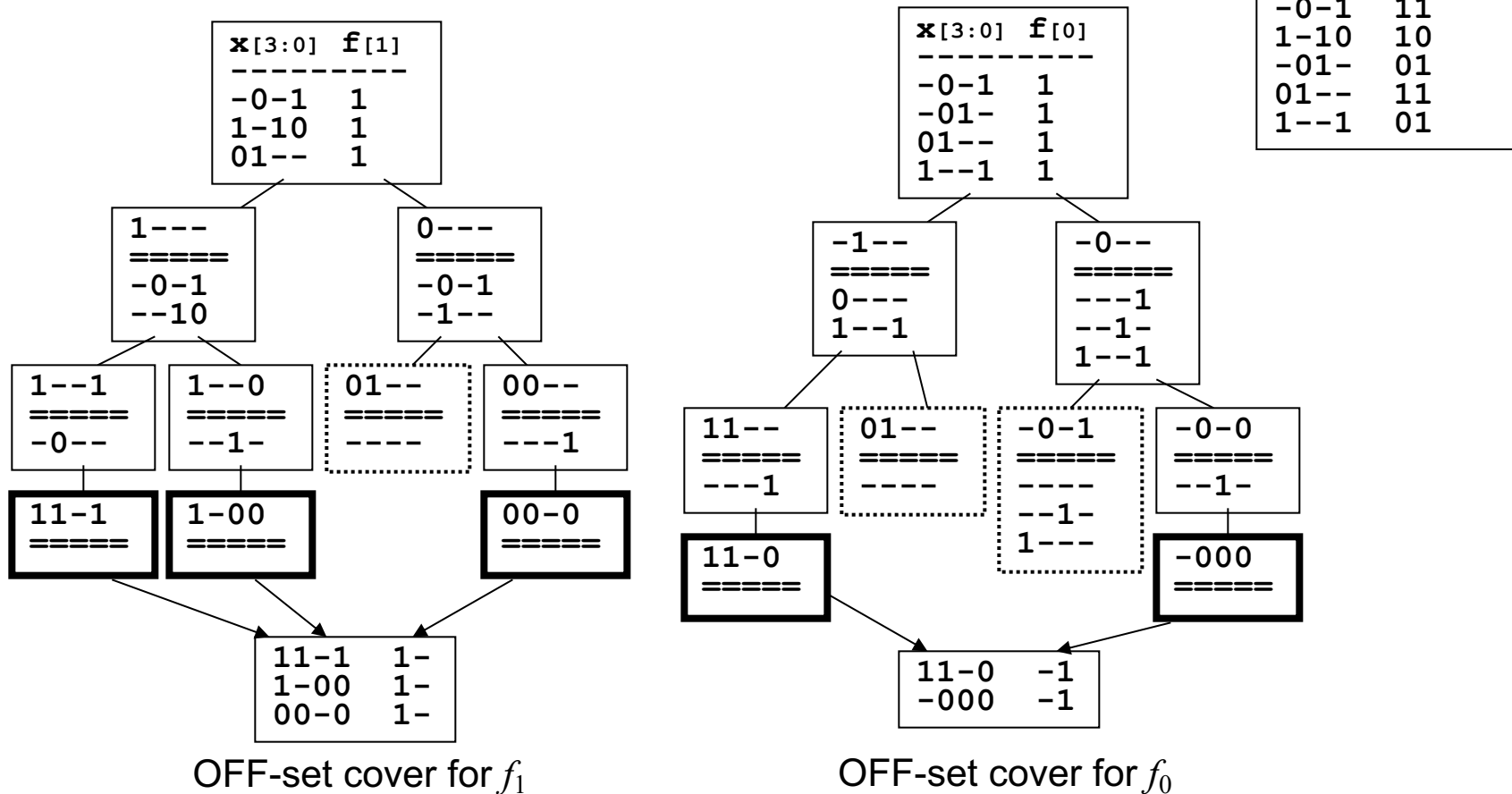
# Shannon Expansion on Multiple-Output Function

$$f_1 = x_0x_2 + x_0x_1x_3 + x_2x_3$$

$$f_0 = x_0\bar{x}_2 + x_1\bar{x}_2 + x_2\bar{x}_3 + x_0x_3$$



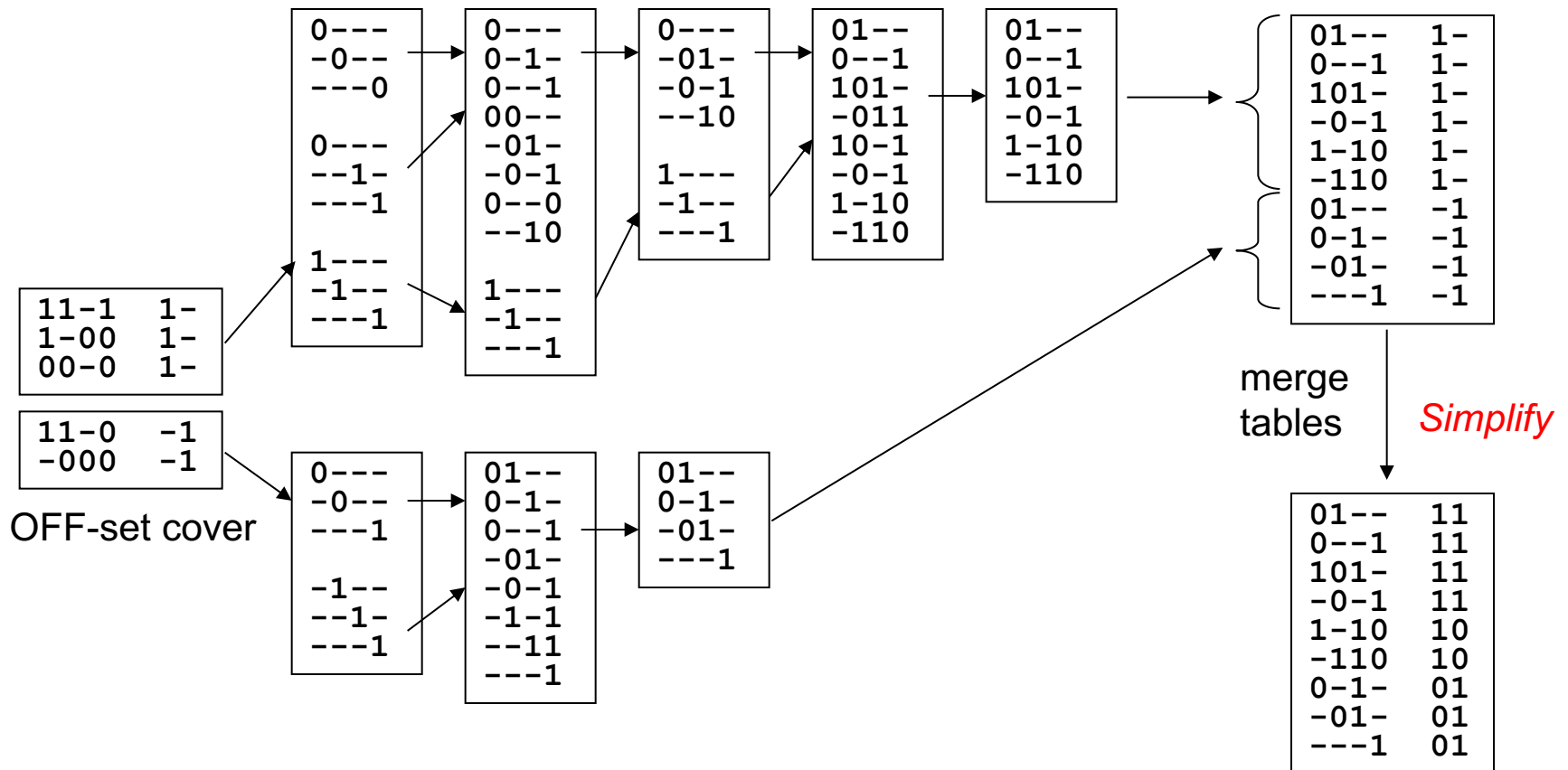
# Negate-And-Expand Method for Multiple-Output Functions


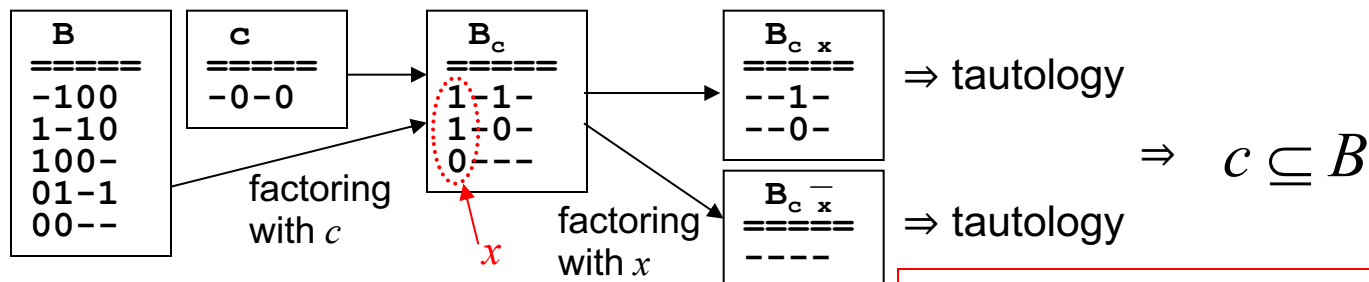
# Reduced Prime Implicant Table Generation (1)

- Essential prime set  $E_r = \{c \mid c \in Q, F \not\subseteq Q - c\}$  :
  - $c$  is an essential prime if the prime set excluding  $c$  (" $Q - c$ " denotes the set  $Q$  whose element  $c$  is eliminated) does not contain the ON-set cover  $F$ . (therefore  $c$  is *essential* for covering  $F$ )
  - Checking  $F \cap c \not\subseteq Q - c$  (instead of  $F \not\subseteq Q - c$ ) is sufficient.
- Containment check
  - $A \subseteq B \Leftrightarrow c \subseteq B$  for  $\forall c \in A$  ( $A, B$  : cover,  $c$  : cube)
    - ✓ In order for a cover to be contained in another (partial order), all cube included in the former needs to be contained in the latter.
  - $c \subseteq B \Leftrightarrow B_c \equiv 1$  ( $B_c$  : cofactor of  $B$  with respect to cube  $c$ )
  - $B \equiv 1 \Leftrightarrow B_x \equiv 1 \wedge B_{\bar{x}} \equiv 1$  (tautology check by recursion)



**Recall:**  $c \subseteq B \Rightarrow c \cdot B = c$



# Reduced Prime Implicant Table Generation (2)

- Relatively redundant prime set  $R_r = Q - E_r$
- Totally redundant prime set  $R_t = \{c \mid c \in R_r, c \subseteq E_r\}$
- Partially redundant prime set  $R_p = R_r - R_t$
- On obtaining a minimal prime set which covers the ON-set  $F$ 
  - ✓  $E_r$  is always included
  - ✓  $R_t$  is never included
  - ✓  $R_p$  is the portion of the total prime set which is considered in the minimum covering problem.
- Each element of  $R_p$  corresponds to the columns of the reduced prime implicant table.
- Minterm set  $M_p$  which needs to be covered (rows of the reduced prime implicant table)
  - ✓  $M_p = \overline{E_r} \cap R_p$
  - ✓  $m \cap E_r = \phi (m \in M_p)$

# Reduced Prime Implicant Table Generation (3)

- Computation of minterm set  $M_p$  (*actually, each row may represent a collection of minterms*)
  - For each cube  $c \in R_p$ , consider the set  $R' = R_p - c$ .
  - Recursively divide  $c$  into smaller cubes at its don't-care variables
    - Ex.  $0-1- \rightarrow (001-, 011-) \rightarrow ((0010, 0011), (0110, 0111))$
  - On each divided cubes  $c'$ :
    - If  $c' \subseteq E_r$ , then  $c'$  is not included in  $M_p$ .
    - If there exists a cube  $d \in R'$  such that  $c' \subseteq d$ , then all minterms included in  $c'$  is covered by the prime  $d$ . If so, add  $c'$  to the row and mark 'X' to all columns which contain  $c'$ . (Note that there may be several cubes which contain  $c'$ )

If one of the two conditions above is satisfied, then  $c'$  does not have to be divided anymore.

# Reduced Prime Implicant Table Generation (4)

$E_r$
01--
10--

$c = 0-1- \rightarrow$   $001- \subseteq -01- \in R'$   
 $011- \subseteq 01-- \in E_r$

$R'$
-01-
-101
1-01

	0	-	-	1
	-	0	1	-
	1	1	0	0
	-	-	1	1
001-	x	x		

$R_p$
0-1-
-01-
-101
1-01

$c = -01- \rightarrow$   $001- \subseteq 0-1- \in R'$   
 $101- \subseteq 10-- \in E_r$

$R'$
0-1-
-101
1-01

	0	-	-	1
	-	0	1	-
	1	1	0	0
	-	-	1	1
001-	x	x		

$c = -101 \rightarrow$   $0101 \subseteq 01-- \in E_r$   
 $1101 \subseteq 1-01 \in R'$

$R'$
0-1-
-01-
1-01


	0	-	-	1
	-	0	1	-
	1	1	0	0
	-	-	1	1
001-	x	x		
1101			x	x

$c = 1-01 \rightarrow$   $1001 \subseteq 10-- \in E_r$   
 $1101 \subseteq -101 \in R'$


$R'$
0-1-
-01-
-101

	0	-	-	1
	-	0	1	-
	1	1	0	0
	-	-	1	1
001-	x	x		
1101			x	x
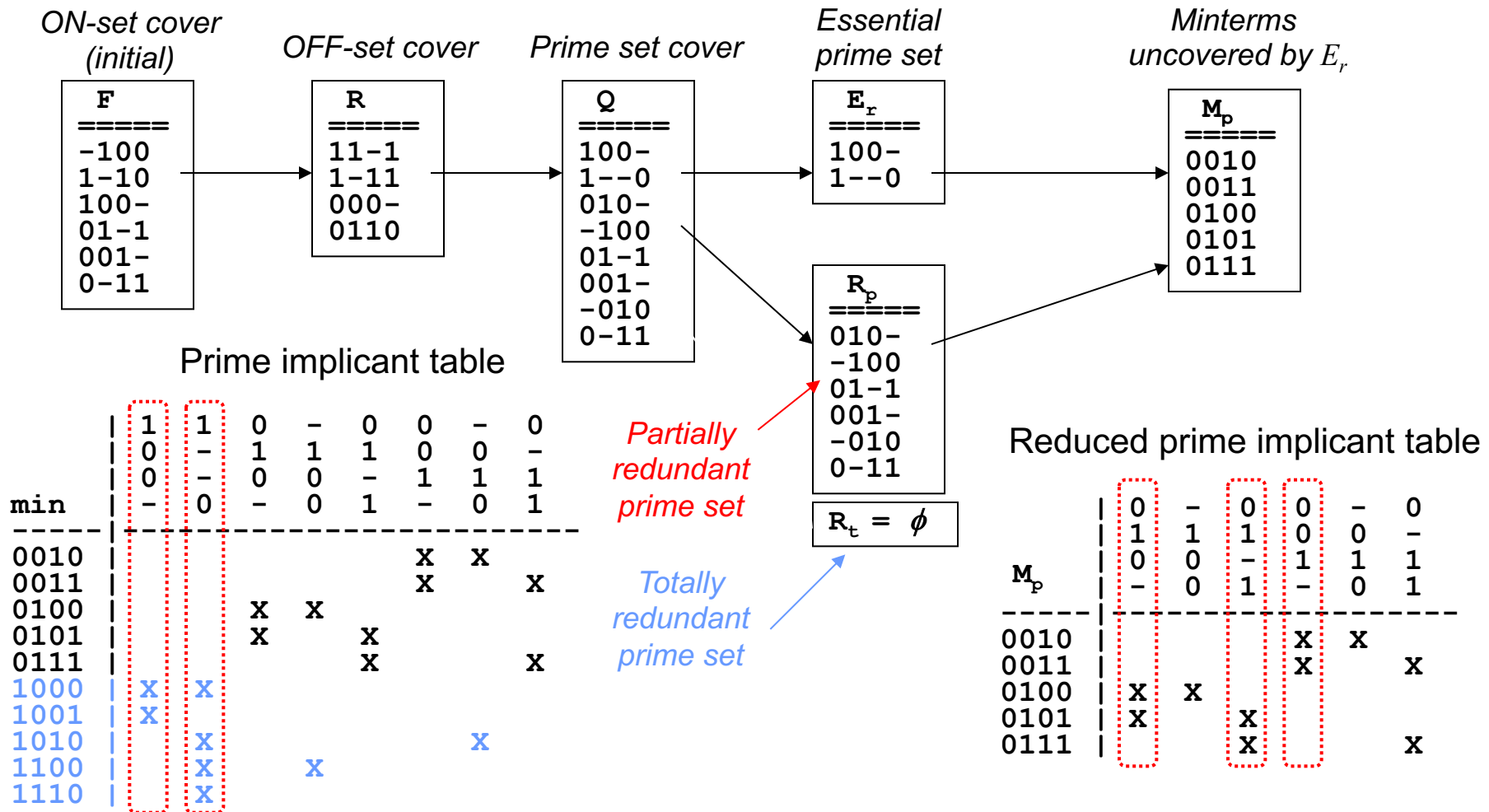
# Reduced Prime Implicant Table Generation (5)


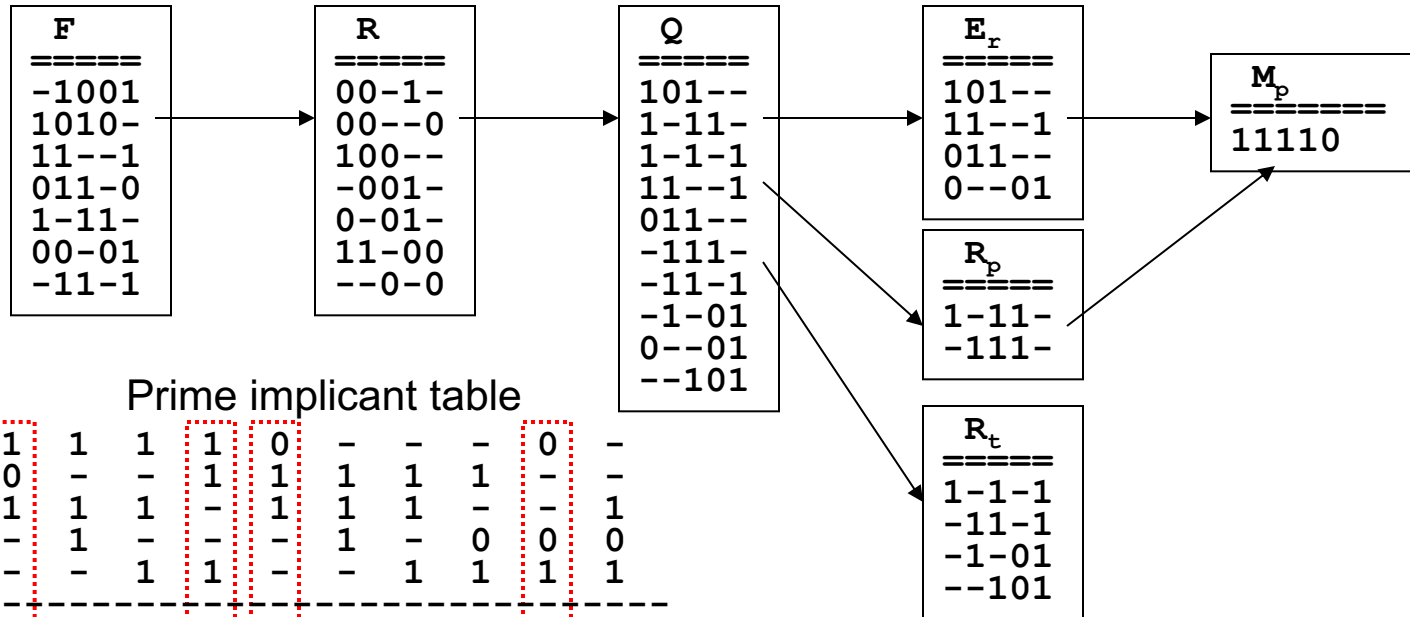
# Reduced Prime Implicant Table Generation (6)



Prime implicant table

min	1	1	1	1	0	-	-	-	0	-
00001	1	-	-	1	1	1	1	1	-	-
00101	1	1	1	-	1	1	1	-	-	1
01001	-	1	-	-	-	1	-	0	0	0
01100	-	-	1	1	-	-	1	1	1	1
01101										
01110										
01111										
10100	x									
10101	x									
10110	x	x								
10111	x	x	x							
11001										
11011										
11101										
11110		x								
11111		x	x							

Reduced prime implicant table

$M_p$	1	-
11110	x	x

# Summary on Two-Level Logic Optimization

- Two-level logic optimization is first proposed by Quine and McCluskey, and since then has been studied widely.
- Based on Quine-McCluskey method, improvements have been made in prime extraction, prime table generation, covering techniques to reduce the computation time.
- Even though the computational complexity is NP-complete (due to prime covering problem), near-optimal solution can be obtained in short time.
- There are heuristic algorithms which solve the prime extraction/prime covering problems iteratively.