

# Problem 4.1

Consider the NAND2-tree in Fig.1.

- A) Using the cell library shown in Fig.2 (next page : note that NOR2 gate is added), give an area optimal technology mapping. Also show the intermediate covering results on the subtrees rooted at each node.
- For simplicity, you don't have to consider the “powered” cells, since area optimal covering will always use the smaller “unpowered” cells only.
- B) For the same problem, give a delay optimal technology mapping with the same cell library.
- Assume that a load of 2 to 6 is connected to the output of the root (node 11) and derive the mapping solutions for each of the load value.
  - For each different mapping solutions derived, compute the slack times at each mapped cell, and apply area recovery if possible.

 


Fig.1 Target NAND2-tree

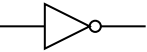
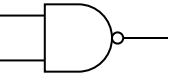
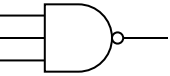
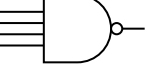
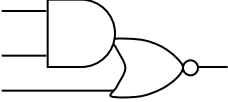

symbol	cell name	area	gate load	switching delay	output transition coef
	INV	2	3	12	4
	INVP	3	6	12	2
	NAND2	3	3	25	6
	NAND2P	5	6	25	3
	NAND3	4	2	40	8
	NAND3P	7	4	40	4
	NAND4	5	2	60	8
	NAND4P	9	4	60	4
	AOI21	4	3	60	8
	AOI21P	7	6	60	4
	NOR2	3	3	25	6
	NOR2P	5	6	25	3

Fig.2 : Cell library. Assume that all input pins have the same load and switch delay for each cell in this library

# Problem 4.2

Consider the fan-out network in Fig.3.

- An inverter with cell switching delay  $S_r = 12$  and output transition coefficient  $T_r = 4$  is driving the 8 loads whose required times are indicated by  $R_i$  and input gate loads indicated by  $L_i$  ( $i = 0, 1, \dots, 7$ ).
- A) Construct a fan-out tree by Two-Level Tree algorithm using the buffer cell  $b_1$  shown in Fig.4.
- B) Construct a fan-out tree by Combinational Merging algorithm using the buffer cell  $b_1$  and  $b_2$  shown in Fig.4.

 


Fig.3 Fan-out network

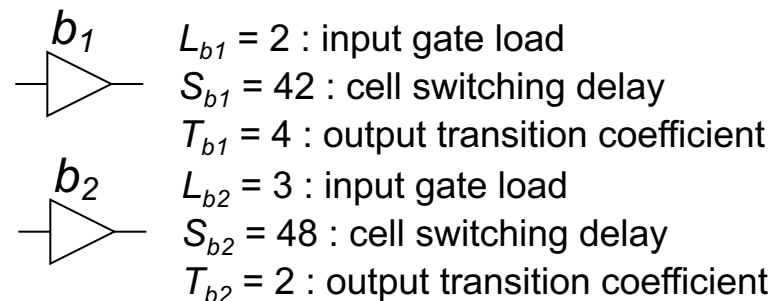


Fig.4 Buffer cell  $b_1$  and cell  $b_2$