

Parallel and Reconfigurable VLSI Computing (8)

RTL Design: Tiny Processor

Hiroki Nakahara

Tokyo Institute of Technology

The lecture is based on a part of "CPUの創り方",
(in Japanese)



Outline

- Processor Specification
- Behavior Design of Tiny Processor
- RTL Design
- Example


Processor Specification

Stored Program Computer

- Operate according to "program" stored in memory
 - Run various applications on the same hardware
- Its idea can be traced back to the 1936 theoretical concept of a universal Turing machine
- Von Neumann was aware of the paper, and he impressed it on his collaborators as well

von Neumann Architecture

 - It also known as the von Neumann model and Princeton architecture
- Based on the 1945 description by the mathematician and physicist John von Neumann and others in the First Draft of a Report on the EDVAC




4bit Tiny Processor

- Operation and data: 4bit (8bit word length)
- 4bit PC (Program Counter)
 - Up to 16 steps (ROM Size) and reset to all zero "0000"
- Two registers A and B
- Carry flag (CF) only by addition
 - Used for a jump operation
- I/O: Only 4bit input and output
- Arithmetic operation: Only 4bit addition

Instruction

- Format

 

- "00001001" denotes MOV A,1001 as assembly code
 - $(0001001)_b$ is a machine code, and it can be written by a hexadecimal value
 - "MOV" is a mnemonic (Instruction)
 - "1001" is immediate value

Instruction Set

- MOV A,IMM $A \leftarrow \text{IMM}$
- MOV B,IMM $B \leftarrow \text{IMM}$
- MOV A,B $A \leftarrow B$
- MOV B,A $B \leftarrow A$
- ADD A,IMM $A \leftarrow A + \text{IMM}$, and $\text{CF} \leftarrow \text{Carry bit}$
- ADD B,IMM $B \leftarrow B + \text{IMM}$, and $\text{CF} \leftarrow \text{Carry bit}$
- IN A $A \leftarrow \text{INPUT (GPIO)}$
- IN B $B \leftarrow \text{INPUT (GPIO)}$
- OUT IMM $\text{OUTPUT(GPIO)} \leftarrow \text{IMM}$
- OUT B $\text{OUTPUT(GPIO)} \leftarrow B$
- JMP IMM $\text{PC} \leftarrow \text{IMM}$
- JNC IMM IF $\text{CF} == 0$ THEN $\text{PC} \leftarrow \text{IMM}$ ELSE $\text{PC} \leftarrow \text{PC} + 1$

A: Register A


B: Register B

PC: Program Counter


IMM: Immediate value

CF: Carry Flag


Data Path (Architecture)

 


Add Operation (ADD A, IMM)

 


MOV Operation (MOV A,B)

 


MOV Operation (MOV A,IMM)

 


Read Input Operation (IN A)

 


Write Output Operation (Out IMM)

 


Program Memory (ROM)

 


Instruction Decoder

 

Overall Architecture

 

JUMP Operation (JMP IMM)

 


Truth Table for an Instruction Decoder


	Inst[3:0]	CF	wr_en[3:0]	jump_en	sel_idx[1:0]
MOV A,IMM	0000	X	1001	0	11
MOV B,IMM	0001	X	1010	0	11
MOV A,B	0010	X	1001	0	01
MOV B,A	0011	X	1010	0	00
ADD A,IMM	0100	X	1001	0	00
ADD B,IMM	0101	X	1010	0	01
IN A	0110	X	1001	0	10
IN B	0111	X	1010	0	10
OUT IMM	1000	X	1100	0	11
OUT B	1001	X	1100	0	01
JMP IMM	1010	X	1000	1	11
JNC IMM	1011	0	1000	1	11
JNC IMM	1011	1	1000	0	11

Behavior Design of Tiny Processor


Time Multiplexing of the Processor

 


1. Read ROM

 


2. Decode Instruction

 


3. Select Register

 

4. Execute an ALU

 

 5. Write Back to Registers (Also, update a PC)



C/C++ Source Code

- see, http://https://github.com/HirokiNakahara/FPGA_lecture/blob/master/Lec8_Tiny_Processor/fourbit_tiny_processor.c

The screenshot shows the GitHub repository page for HirokiNakahara/FPGA_lecture. The repository has 9 commits, 1 branch, 0 releases, 1 contributor, and is licensed under MIT. The commit history shows the following files and their creation times:

File	Commit Message	Time
Lec7_Practical_RTL_design	Create fir_pipe_1.v	5 days ago
Lec8_Tiny_Processor	Create fourbit_tiny_processor.c	12 minutes ago
LICENSE	Initial commit	5 days ago
README.md	Update README.md	5 days ago

The README.md file contains the following text:

FPGA_lecture


Source Codes for a lecture entitled "Parallel and Reconfigurable VLSI Computing" in Tokyo Tech.

The lecture slides can be downloaded at the Tokyo Tech.

Tokyo Tech Open Course Ware (OCW) for my FPGA lecture: <http://www.ocw.titech.ac.jp/index.php?module=General&action=T0300&GakubuCD=2&GakkaCD=321818&KeiCD=18&course=18&KougiCD=201818041&Nendo=2018&lang=EN&vid=05>

Case Study: LED Controller

```
0x81, // OUT 0001
0x82, // OUT 0010
0x84, // OUT 0100
0x88, // OUT 1000
0x84, // OUT 0100
0x82, // OUT 0010
0xA0, // JMP to 0000
0x00, // Followings are NOP
0x00,
0x00,
0x00,
0x00,
0x00,
0x00,
0x00,
0x00,
0x00,
0x00,
0x00,
```

 
A screenshot of a terminal window titled 'nakahara@nakSurfLap: /mnt/hgfs/Documents/ResearchDocuments/program/fourbit_computer'. The terminal displays a series of assembly instructions for a four-bit computer, including steps like 'STEP183: PC=B ROM=84 INST=8 IMM=4', 'NextPC=C, REGA=D, REGB=0, OUT=4', and 'STEP184: PC=C ROM=41 INST=4 IMM=1'. The instructions involve setting registers, performing arithmetic, and outputting values. The terminal window is part of a VMware Workstation 14 Player interface, with the Ubuntu 1604 LTS logo visible in the top left corner.

```
nakahara@nakSurfLap: /mnt/hgfs/Documents/ResearchDocuments/program/fourbit_computer
STEP183: PC=B ROM=84 INST=8 IMM=4
sel_ldx=8 wr_en=4
NextPC=C, REGA=D, REGB=0, OUT=4
STEP184: PC=C ROM=41 INST=4 IMM=1
sel_ldx=1 wr_en=1
NextPC=D, REGA=E, REGB=0, OUT=4
STEP185: PC=D ROM=8A INST=8 IMM=a
sel_ldx=8 wr_en=8
NextPC=A, REGA=E, REGB=0, OUT=4
STEP186: PC=A ROM=80 INST=8 IMM=0
sel_ldx=8 wr_en=4
NextPC=B, REGA=E, REGB=0, OUT=0
STEP187: PC=B ROM=84 INST=8 IMM=4
sel_ldx=8 wr_en=4
NextPC=C, REGA=E, REGB=0, OUT=4
STEP188: PC=C ROM=41 INST=4 IMM=1
sel_ldx=1 wr_en=1
NextPC=D, REGA=F, REGB=0, OUT=4
STEP189: PC=D ROM=8A INST=8 IMM=a
sel_ldx=8 wr_en=8
NextPC=A, REGA=F, REGB=0, OUT=4
STEP190: PC=A ROM=80 INST=8 IMM=0
sel_ldx=8 wr_en=4
NextPC=B, REGA=F, REGB=0, OUT=0
STEP191: PC=B ROM=84 INST=8 IMM=4
sel_ldx=8 wr_en=4
NextPC=C, REGA=F, REGB=0, OUT=4
STEP192: PC=C ROM=41 INST=4 IMM=1
sel_ldx=1 wr_en=1
NextPC=D, REGA=0, REGB=0, OUT=4
STEP193: PC=D ROM=8A INST=8 IMM=a
sel_ldx=8 wr_en=8
NextPC=E, REGA=0, REGB=0, OUT=4
STEP194: PC=E ROM=88 INST=8 IMM=8
sel_ldx=8 wr_en=4
NextPC=F, REGA=0, REGB=0, OUT=8
nakahara@nakSurfLap: /mnt/hgfs/Documents/ResearchDocuments/program/fourbit_computer$
```



Execute a C behavior code on your PC

RTL Design

Insert Virtual Register

 

Design an FSM

  

RTL Source Code

- see, https://github.com/HirokiNakahara/FPGA_lecture/blob/master/Lec8_Tiny_Processor/
 - RTL: fourbit_tiny_processor.v
 - Testbench: testbench_tiny_processor.v

The screenshot shows the GitHub repository page for HirokiNakahara/FPGA_lecture. The repository is described as "Source Codes for a lecture entitled 'Parallel and Reconfigurable VLSI Computing' in Tokyo Tech." It has 9 commits, 1 branch, 0 releases, and 1 contributor. The repository is licensed under MIT. The commit history shows the following:

Commit	Author	Message	Time
ffea135	HirokiNakahara	Create fourbit_tiny_processor.c	12 minutes ago
		Create fir_pipe_1.v	5 days ago
		Create fourbit_tiny_processor.c	12 minutes ago
		Initial commit	5 days ago
		Update README.md	5 days ago

The README.md file contains the following text:

FPGA_lecture

Source Codes for a lecture entitled "Parallel and Reconfigurable VLSI Computing" in Tokyo Tech.

The lecture slides can be downloaded at the Tokyo Tech.

Tokyo Tech Open Course Ware (OCW) for my FPGA lecture: <http://www.ocw.titech.ac.jp/index.php?module=General&action=T0300&GakubuCD=2&GakkaCD=321818&KeiCD=18&course=18&KougiCD=201818041&Nendo=2018&lang=EN&vid=05>


RTL Code for Reading ROM

```

60     case( state)
61     3'b000:begin // read ROM
62         state <= 3'b001;
63         {INST, IMM} <= ROM( PC);
64     end
        ⋮

98     function [7:0]ROM( input [3:0]address);
99     begin
100         case( address)
101         4'b0000: ROM = 8'h81;
102         4'b0001: ROM = 8'h82;
103         4'b0010: ROM = 8'h84;
104         4'b0011: ROM = 8'h88;
105         4'b0100: ROM = 8'h84;
106         4'b0101: ROM = 8'h82;
107         4'b0110: ROM = 8'hA0;
108         4'b0111: ROM = 8'h00;
109         4'b1000: ROM = 8'h00;
110         4'b1001: ROM = 8'h00;
111         4'b1010: ROM = 8'h00;
112         4'b1011: ROM = 8'h00;
113         4'b1100: ROM = 8'h00;
114         4'b1101: ROM = 8'h00;
115         4'b1110: ROM = 8'h00;
116         4'b1111: ROM = 8'h00;
117     endcase
118 end
119 endfunction

```

 

RTL for an Instruction Decoder

```

65 3'b001:begin // decode inst
66     state <= 3'b010;
67     {wr_en, jump_en, sel_idx} <= INST_DEC( INST, CF);
68 end


```

⋮

```


140 function [6:0]INST_DEC( input [3:0]inst, input CF);
141 begin "case" accept a don't care "x"
142     casex( {inst, CF})
143         5'b0000_x: INST_DEC = 7'b1001_0_11;
144         5'b0001_x: INST_DEC = 7'b1010_0_11;
145         5'b0010_x: INST_DEC = 7'b1001_0_01;
146         5'b0011_x: INST_DEC = 7'b1010_0_00;
147         5'b0100_x: INST_DEC = 7'b1001_0_00;
148         5'b0101_x: INST_DEC = 7'b1001_0_01;
149         5'b0110_x: INST_DEC = 7'b1001_0_10;
150         5'b0111_x: INST_DEC = 7'b1010_0_10;
151         5'b1000_x: INST_DEC = 7'b1100_0_11;
152         5'b1001_x: INST_DEC = 7'b1100_0_01;
153         5'b1010_x: INST_DEC = 7'b1000_1_11;
154         5'b1011_0: INST_DEC = 7'b1000_1_11;
155         5'b1011_1: INST_DEC = 7'b1000_0_11;
156         default: INST_DEC = 7'b0000_0_00;
157     endcase
158 end
159 endfunction

```

 

RTL for a Register Selector

 
```
69 3'b010:begin // select reg
70   state <= 3'b011;
71   sel_val <= sel_idx == 2'b00 ? REGA :
72               sel_idx == 2'b01 ? REGB :
73               sel_idx == 2'b10 ? gpio_in :
74               4'b0000;
75 end
```



RTL for an ALU (4-bit Adder with CF)

```
76 3'b011:begin // execute
77   state <= 3'b100;
78   add_result <= tmp_add_result[3:0];
79   CF <= tmp_add_result[4];
80 end
```
 
```
160
161 assign tmp_add_result = sel_val + IMM;
162
```




RTL for a Write Back to Register

```


81 3'b100:begin // write back regs
82     state <= 3'b000;
83     if( wr_en[0] == 1'b1) REGA <= add_result;
84     if( wr_en[1] == 1'b1) REGB <= add_result;
85     if( wr_en[2] == 1'b1) gpio_out <= add_result;
86     if( jump_en == 1'b1)
87         PC <= add_result;
88     else
89         PC <= PC + 1'b1;
90 end

```

 

Behavior Simulation

- See, testbench_tiny_processor.v

 

Wrapper of a Topmodule

- see, github. Source: topmodule_fourbit_tiny_processor.v

```
23 module topmodule_fourbit_tiny_processor(  
24     input sysclk,  
25     input [0:0] btn,  
26     output [3:0] led  
27 );  
28  
29     reg [24:0] count; // 1sec ~ 8ns (125MHz) * 125,000,000  
30  
31     always@( posedge sysclk or posedge btn[0])begin  
32         if( btn[0] == 1'b1) begin  
33             count <= 25'b0;  
34         end else begin  
35             count <= count + 1'b1;  
36         end  
37     end  
38  
39     fourbit_tiny_processor tiny_processor_inst(  
40         .clock( count[24]),  
41         .reset_p( btn[0]),  
42         .gpio_in( 4'b0000),  
43         .gpio_out( led)  
44     );  
45  
46 endmodule
```

Example

3min Timer

0x87, // OUT 0111

LED: ○●●●

0x41, // ADD A,0001

0xB1, // JNC 0001

0x41, // ADD A,001

0xB3, // JNC 0011

0x86, // OUT 0110

LED: ○●●○

0x41, // ADD A,0001

0xB6, // JNC 0110

0x41, // ADD A,0001

0xB8, // JNC 1000

0x80, // OUT 0000

0x84, // OUT 0100




0x41, // ADD 0001

0xBA, // JNC 1010

0x88, // OUT 1000

LED: ○●○○

0xAF, // JMP 1111

   

Conclusion

- Tiny Processor by RTL Design
 - Specification
 - Block Diagram Design
 - C/C++ Behavior Design
 - FSM Design
 - RTL Design & Verification
 - FPGA Implementation
- Software Example
 - LED Controller
 - 3min Timer

Exercise

- (Mandatory) Implement the tiny processor on the Zybo board
- (Optional 1) Extend the memory size to 32 words
- (Optional 2) Add a subtractor as a new operation
- (Optional 3) Develop an assembler for the tiny processor

Send a report to OCW-i

Deadline is 19th, July, 2019 JST PM 13:20

(At the beginning of the lecture)